



Southern Technical University
Basrah Technical Institute
Department of Electrical Techniques



AC Electrical Circuits

First Year

2022-2023

Chapter (10) Alternating Current and Voltage

10-1 Generation of AC Voltage:

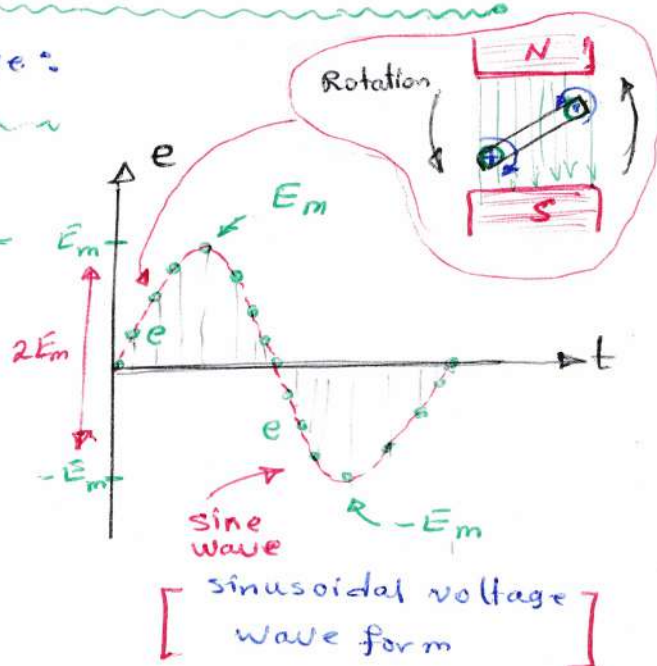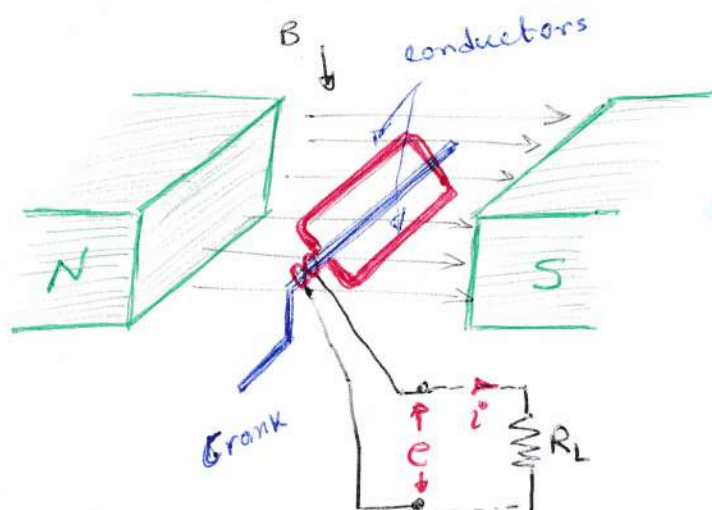

- * A sinusoidal voltage waveform is generated at the terminals of a conducting loop rotated in a magnetic field.
- * Peak of voltage is produced when the conductors are moving perpendicular to the field.
- * Zero of voltage when the conductors are moving parallel to the field.

emf induced

$$e = \frac{\Delta \phi}{\Delta t} = B \cdot \frac{\Delta A}{\Delta t}$$

$$e = B \cdot l \cdot \frac{\Delta d'}{\Delta t}$$

$$\Delta d' = \Delta d \sin \alpha$$

$$e = B l \frac{\Delta d}{\Delta t} \sin \alpha \quad \text{velocity}$$


$$e = B l v \sin \alpha$$

$$e = E_m \sin \alpha$$

emf induced

max. emf induced magnitude peak value

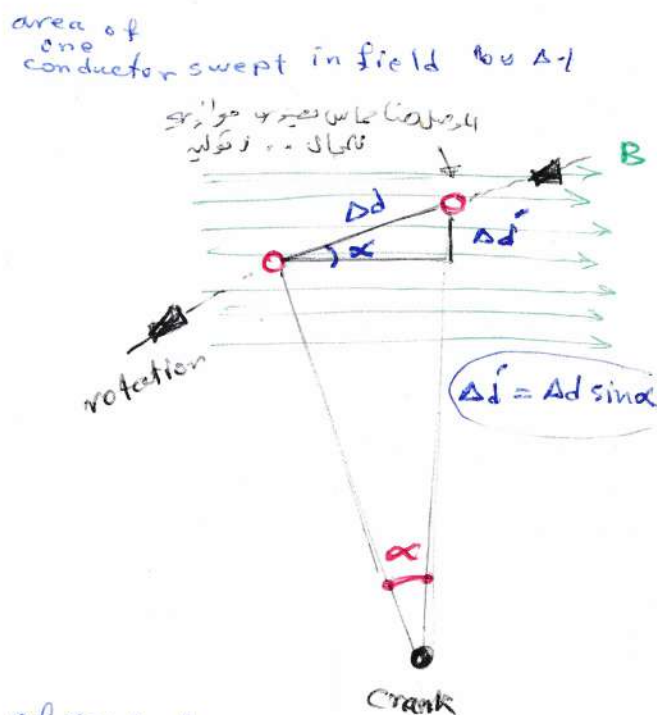angle of conductor with the field. (phases).



Example
 In the hand-cranked generator l of each conductor is 25 cm, $r = 5$ cm, $B = 0.1$ T, $\text{rpm} = 100$
 Calculate E_m , e ($\alpha = 45^\circ, 90^\circ, 135^\circ, 225^\circ$).

Solution:

$$E_m = B l v = B l \frac{\Delta d}{\Delta t}$$

$$\Delta d = 2\pi r \times \overset{\text{r.p.m}}{100} = 2\pi \times 5 \times 10^{-2} \times 100 = 10\pi \text{ m}$$

$$\Delta t = 1 \text{ min} = 60 \text{ sec}$$

$$\therefore E_m = 0.1 \times 0.25 \times \frac{10\pi \text{ m}}{60 \text{ sec}} = 26.2 \text{ mV}$$

$$e = E_m \sin \alpha$$

for $\alpha = 45^\circ \Rightarrow e = 26.2 \sin 45 = 18.5 \text{ mV}$

$\alpha = 90^\circ \Rightarrow e = 26.2 \sin 90 = 26.2 \text{ mV}$

$\alpha = 135^\circ \Rightarrow e = 18.5 \text{ mV}$

$\alpha = 225^\circ \Rightarrow e = -18.5 \text{ mV}$


10-2 : Frequency, phase angle and wavelength.

- * time of one cycle = T
- * frequency $f = \frac{1}{T}$
 number of cycles in 1 sec

$$f = 1 \text{ Hz} = 1 \text{ cycle/sec}$$

* Angular velocity $\omega = \frac{2\pi}{T} = 2\pi f$ radians/sec
 \uparrow
 for one revolution in sec

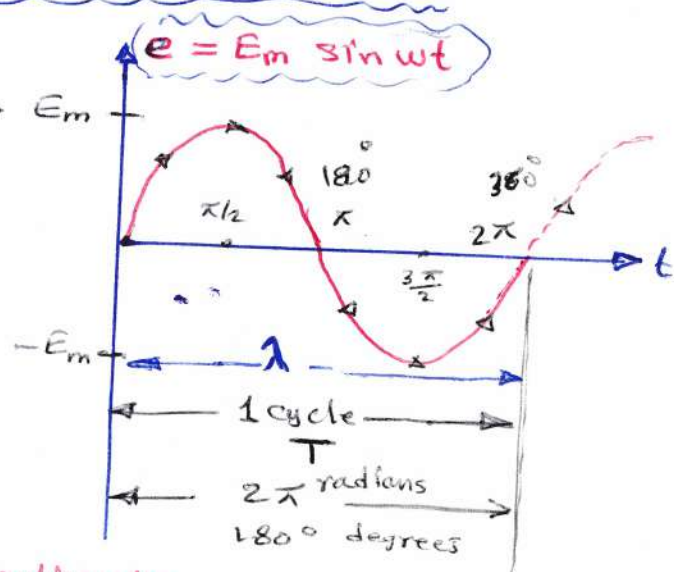* phase angle α at any time = $\omega t = 2\pi f t$ radians.



* Wavelength $\lambda = \frac{c}{f} = cT$

in(m) velocity of light m/s time period in sec.

$c = 3 \times 10^8 \text{ m/s}$

Example: An ac waveform with frequency $f = 1.5 \text{ kHz}$ has a peak value of $E_m = 3.3 \text{ volt}$. Find the time period T and the wavelength λ and e at $t_1 = 0.65 \mu\text{s}$, $t_2 = 1.2 \text{ ms}$

solution:

$$T = \frac{1}{f} = \frac{1}{1.5 \times 10^3} = 0.66 \text{ m sec}$$



$$\lambda = \frac{c}{f} = \frac{3 \times 10^8}{1.5 \times 10^3} = 2 \times 10^5 = 200 \text{ km}$$

$$\omega = 2\pi f = 2\pi \times 1.5 \times 10^3 = 3\pi \times 10^3 \text{ rad/sec.}$$

$$e_1 = E_m \sin \omega t_1 = 3.3 \sin(3\pi \times 10^3 \times 0.65 \times 10^{-6}) = 20.2 \text{ mV}$$

$$e_2 = E_m \sin \omega t_2 = 3.3 \sin(3\pi \times 10^3 \times 1.2 \times 10^{-3}) = -3.1 \text{ volt}$$

10-3: resistive load with AC supply

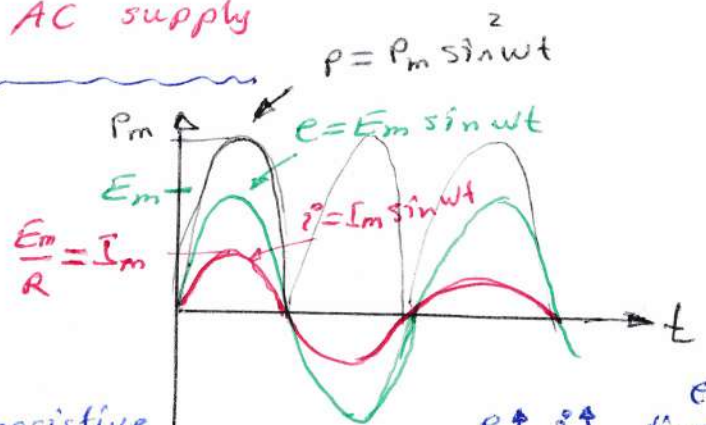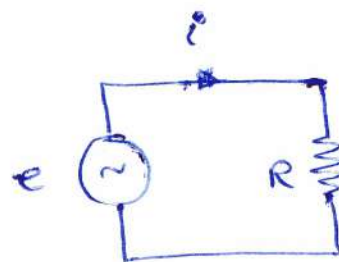


The AC current i in purely resistive circuit is in phase with the ac voltage.

$$i = \frac{e}{R} = \frac{E_m}{R} \sin \omega t = I_m \sin \omega t$$

$$p = e i = i^2 R = \frac{e^2}{R} = I_m^2 R \sin^2 \omega t = P_m \sin^2 \omega t$$

$$P_m = I_m^2 R = \frac{V_m^2}{R} = I_m V_m$$

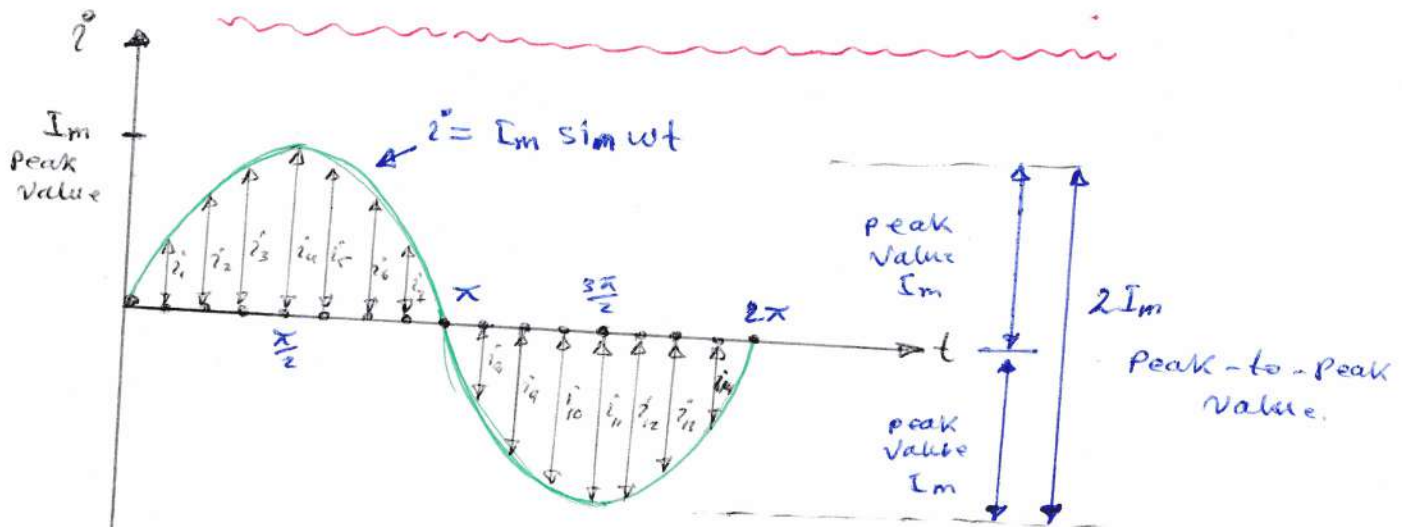10-4: Peak, Average and RMS values of Sine waves



$$I_{av_1} = \frac{i_1 + i_2 + \dots + i_7}{7} \quad \text{for positive half cycle.}$$

$$I_{av_1} = \frac{I_m}{7} \{ \sin \omega t_1 + \sin \omega t_2 + \dots + \sin \omega t_7 \} \approx 0.637 I_m$$

$$I_{av_2} = \frac{i_8 + i_9 + \dots + i_{14}}{7} \quad \text{for negative half cycle}$$

$$\approx -0.637 I_m$$

$$\therefore I_{av} = I_{av_1} + I_{av_2} = 0 \quad \text{Zero. (Average value)}$$

$$\text{or } I_{av} = \frac{1}{2\pi} \int_0^{2\pi} I_m \sin \omega t \, dt = 0$$

\therefore Average value of 1 cycle of sinus wave i or $e = 0$

* **Effective value (rms)** (It is used in ohm's Law)


$$\text{dc equivalent value} \rightarrow I_{rms} = \frac{I_m}{\sqrt{2}} = 0.707 I_m$$

$$\text{dc equivalent value} \rightarrow V_{rms} = \frac{V_m}{\sqrt{2}} = 0.707 V_m$$

$$\text{ac - power dissipation} = I_{rms}^2 R = \frac{1}{2} I_m^2 R$$

$$\therefore P = \frac{1}{2} P_m$$

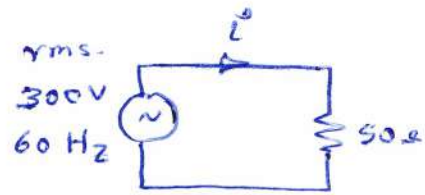Example A 300 V sinusoidal ac supply is applied to 50 Ω resistor. Determine!



- E_m & I_m
- rms current I
- average current for half-cycle
- average current for 1-complete cycle.
- power dissipation.
- instantaneous power at phase angle $\pi/2$

Solution:

$$\text{a) } E_m = \sqrt{2} E = 1.414 * 300 = 424 \text{ Volt.}$$

$$I_m = \frac{E_m}{R} = \frac{424}{50} = 8.48 \text{ A}$$

$$\text{b) rms } I = \frac{I_m}{\sqrt{2}} = \frac{8.48}{\sqrt{2}} = 6 \text{ A} \quad \text{or } I = \frac{E}{R} = \frac{300}{50} = 6 \text{ A}$$

$$\text{c) } I_{\text{av of half cycle}} = 0.637 I_m = 0.637 * 8.48 = 5.4 \text{ A}$$

$$\text{d) } I_{\text{av of 1 complete cycle}} = 0$$


$$\text{e) } P = I^2 * R = 6^2 * 50 = 1.8 \text{ kW.} = \frac{1}{2} P_m = \frac{1}{2} I_m^2 R$$

$$\begin{aligned} \text{f) } P &= I_m^2 R \sin^2 \omega t = I_m^2 R \sin^2 \alpha \\ &= (8.48)^2 * 50 * \sin^2(\pi/2) \\ &= 3.5 \text{ kW.} \end{aligned}$$

Note: *with AC Voltages and currents, all quantities are assumed to be rms quantities unless otherwise indicated.

* For analysis use all quantities in rms or in peak values. (don't mix).

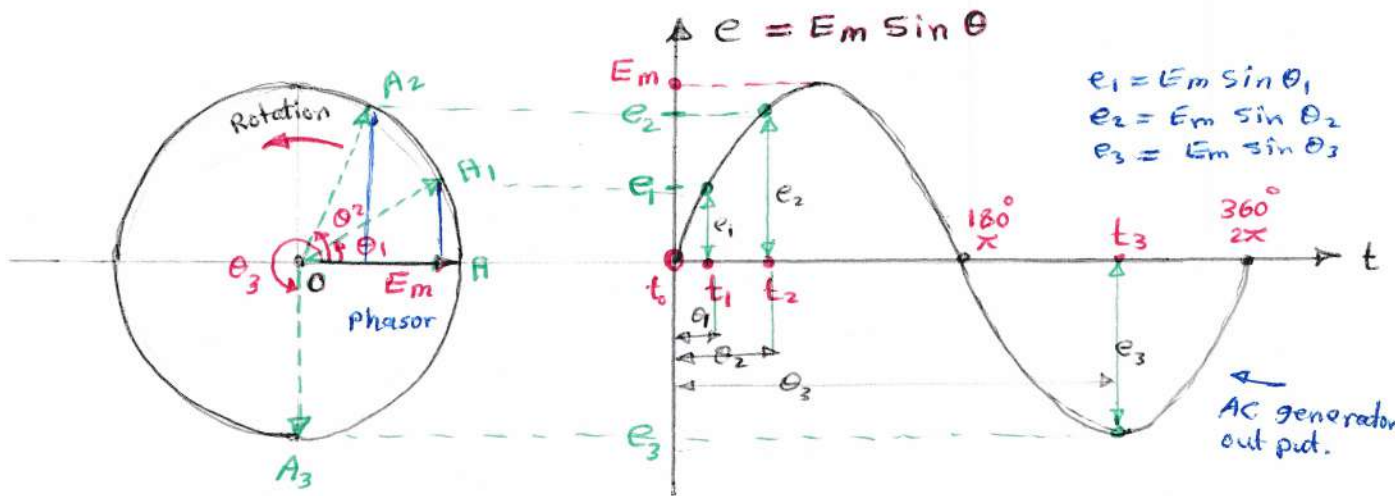Chapter (11) : Phasors and complex numbers



Phasor representation of a sinwave:

At any angle θ , $OA \sin \theta$ is the instantaneous value of the sine wave.





scalar : number of unites (magnitude), (volume, resistance, ...)

vectors : number of unites and direction, (velocity, force, ...)

phasors : vectors rotates by angular velocity ω .

(AC current, AC voltage).

Addition and subtraction of phasors:

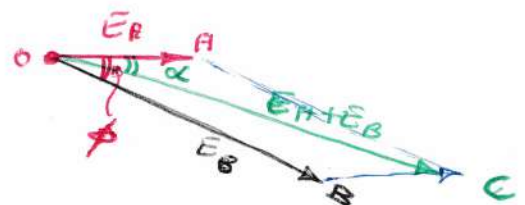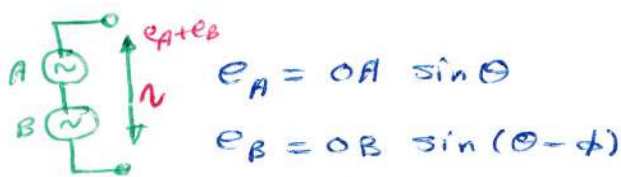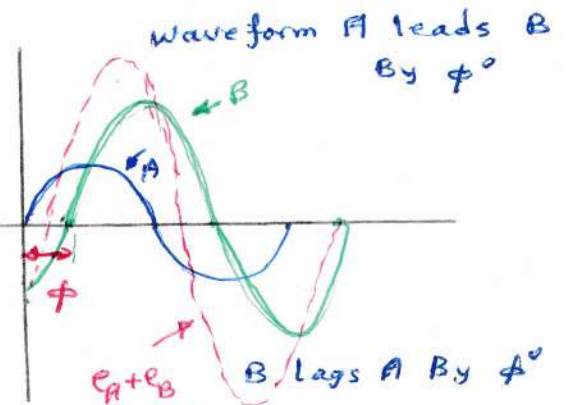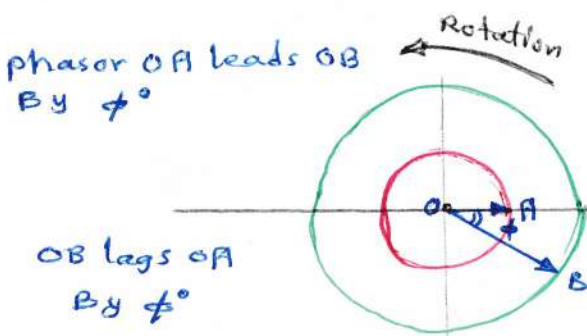


Example

$v_1 = 120 \sin \theta$, $v_2 = 75 \sin(\theta - 30^\circ)$
 find the resultant of (a) $v_1 + v_2$ (b) $v_1 - v_2$

solution

(a)

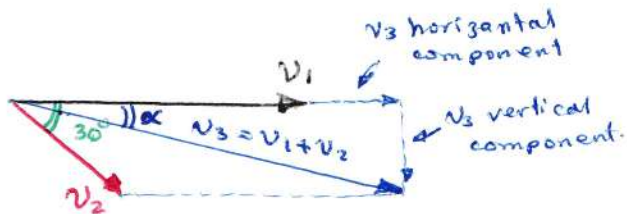

$$v_3 = v_1 + v_2$$

horizontal component of $v_1 = 120 \cos 0 = 120$

$$= \quad = \quad \text{of } v_2 = 75 \cos 30 = 65$$

$$= \quad = \quad \text{of } v_3 = 120 + 65 = 185$$

vertical component of $v_1 = 120 \sin 0 = 0$

$$= \quad = \quad = \quad v_2 = \quad - 75 \sin 30 = -37.5$$

$$= \quad = \quad = \quad v_3 = \quad 0 - 37.5 = -37.5$$

$$v_3 = \sqrt{(185)^2 + (37.5)^2} = 188.8$$

$$\alpha = \tan^{-1} \frac{v_3 \text{ vertical component}}{v_3 \text{ horizontal component}} = \tan^{-1} \frac{-37.5}{185} = -11.5^\circ$$

$$\therefore v_3 = 188.8 \sin(\theta - 11.5^\circ)$$

(b)

$$v_3 = v_1 - v_2$$

horizontal component of $v_1 = 120$

$$= \quad = \quad = \quad -v_2 = 75 \cos(180 - 30)$$

$$= -65$$

$$= \quad = \quad \text{of } v_3 = 120 - 65 = 55$$


vertical component of $v_1 = 120 \sin 0 = 0$

$$= \quad = \quad = \quad -v_2 = 75 \sin(180 - 30) = 37.5$$

$$v_3 = \sqrt{(55)^2 + (37.5)^2} = 66.6$$

$$\phi = \tan^{-1} \frac{37.5}{55} = 34.3^\circ$$
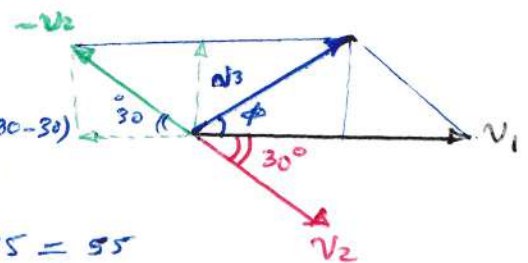
$$\therefore v_3 = 66.6 \sin(\theta + 34.3^\circ)$$




Example




Graphically find $V_t = V_1 + V_2 - V_3$

where: $V_1 = 50 \sin \theta$, $V_2 = 30 \sin(\theta + 25^\circ)$

$V_3 = 25 \sin(\theta - 90^\circ)$.

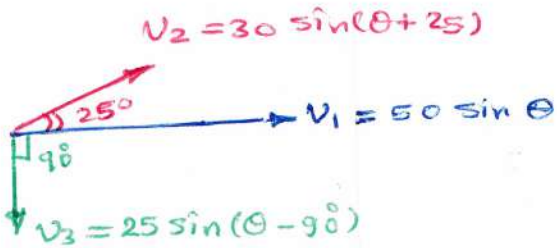

$$V_t = 86 \sin(\theta + 26^\circ)$$

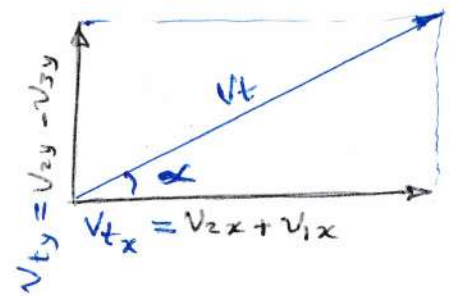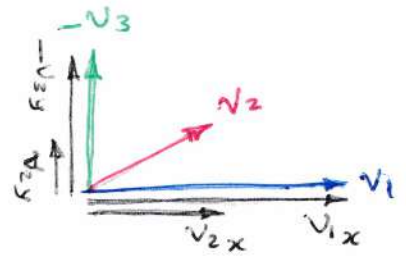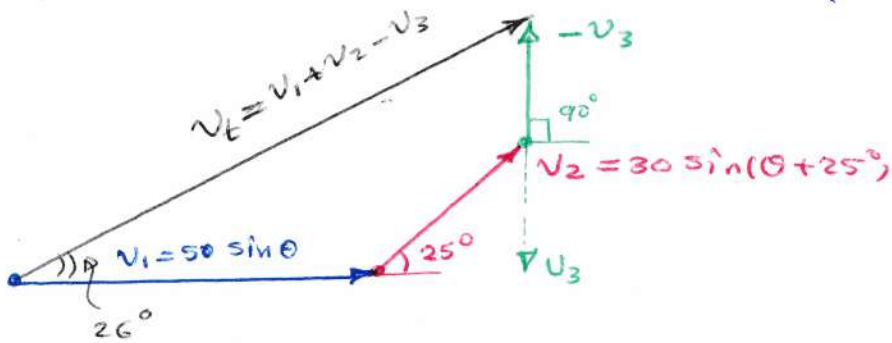

$$\alpha = \tan^{-1} \frac{V_{ty}}{V_{tx}}$$

Polar and Rectangular Form, The j operator

$$e = E_m \sin \theta$$

$$= E_m \angle \theta$$

magnitide angle

$$= E_m [\cos(\theta) + j \sin(\theta)]$$

Real part Imaginary part

$$i = I_m \sin(\theta + \alpha)$$

$$= I_m \angle \theta + \alpha$$

polar form

$$= I_m [\cos(\theta + \alpha) + j \sin(\theta + \alpha)]$$

j operator


imaginary number
↓
sinusoidal quantity

$$j = \sqrt{-1} \equiv 90^\circ$$

$$j^2 = -1 \equiv 180^\circ$$

$$j j x = \sqrt{-1} \sqrt{-1} x = -x$$

$$j b = E_m \sin \theta$$

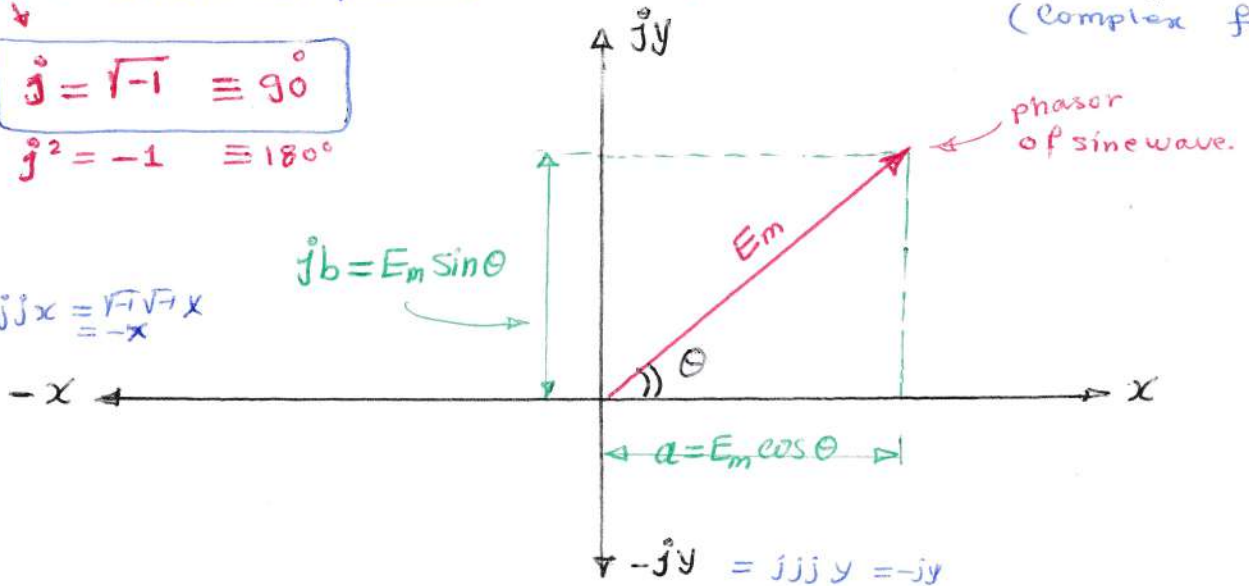




Example:

$$12 \sin(30) \quad , \quad 40 \sin(105) \quad , \quad 270 \sin(1.7\pi)$$

$$\textcircled{1} \quad 12 \sin(30) = 12 \angle 30^\circ = 12 \cos(30) + j 12 \sin 30 = 10.4 + j 6$$

$$\textcircled{2} \quad 40 \sin(105) = 40 \angle 105^\circ = 40 \cos(105) + j \sin(105) + 40 = -10.4 + j 38.6$$
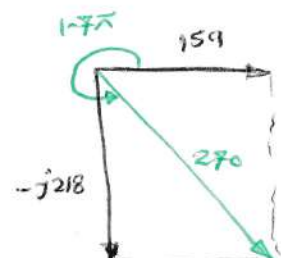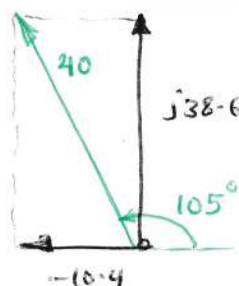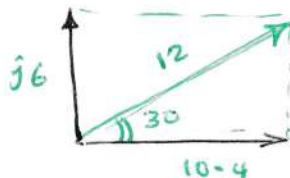
$$\textcircled{3} \quad 270 \sin(1.7\pi) = 270 \angle 1.7\pi = 270 \cos(1.7\pi) + j 270 \sin(1.7\pi) = 159 - j 218$$



* Mathematics of rectangular (complex) form and polar form

$$j = \sqrt{-1} \quad ; \quad j^2 = \sqrt{-1} \sqrt{-1} = -1 \quad ; \quad j^3 = -j \quad , \quad j^4 = 1$$

$$\frac{1}{j} = \frac{1}{j} \times \frac{j}{j} = -j$$

① complex form

Let $f = a + jb$, $h = c + jd$

$$\otimes f + h = (a + jb) + (c + jd) = (a + c) + j(b + d)$$

$$\otimes f - h = (a + jb) - (c + jd) = (a - c) + j(b - d)$$

$$\otimes f \times h = (a + jb) \times (c + jd) = ac + jbc + jad - bc = (ac - bd) + j(bc + ad)$$

$$\otimes \frac{f}{h} = \frac{a + jb}{c + jd} = \frac{a + jb}{c + jd} \times \frac{c - jd}{c - jd} = \frac{(ac + bd) + j(bc - ad)}{c^2 + d^2}$$

↑
conjugate of denominator

$$= \frac{ac + bd}{c^2 + d^2} + j \frac{bc - ad}{c^2 + d^2}$$

② polar form

Let $m = E_1 \angle \theta_1$, $n = E_2 \angle \theta_2$

$$\ast m \times n = E_1 \angle \theta_1 \times E_2 \angle \theta_2 = E_1 E_2 \angle \theta_1 + \theta_2$$

$$\ast \frac{m}{n} = \frac{E_1 \angle \theta_1}{E_2 \angle \theta_2} = \frac{E_1}{E_2} \angle \theta_1 - \theta_2$$


Note: * addition and subtraction are easy in complex form

* multiplication and division are simpler in polar form

chapter (12)


Inductance and capacitance in AC circuits

1) AC supply with pure resistance:

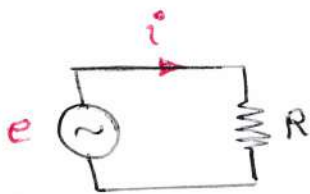

$$e = E_m \sin \omega t$$
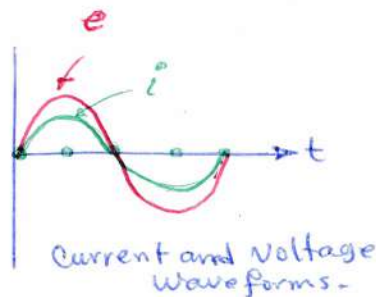
$$i = \frac{e}{R} = \frac{E_m}{R} \sin \omega t = I_m \sin(\omega t)$$




phasor diagram
e in phase with i



$$G = \frac{1}{R} \quad \text{siemens.}$$


2) AC supply with pure inductive load:

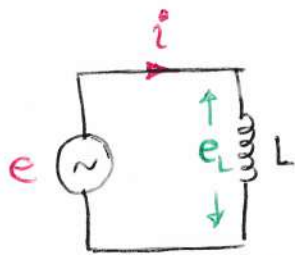

$$e = E_m \sin \omega t$$


$$e_L = L \frac{\Delta i}{\Delta t} = \omega L \cos(\omega t - \pi/2)$$

$$i = I_m \sin(\omega t - \pi/2)$$

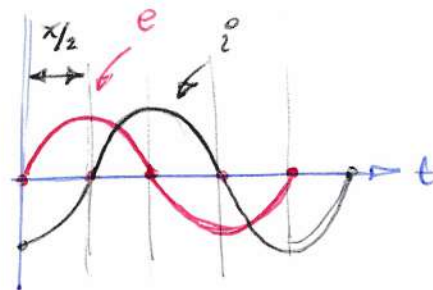

phasor diagram

i Lag e by $\frac{\pi}{2}$

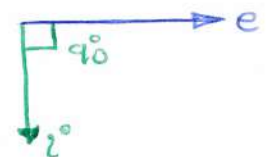




$$X_L = \frac{E_{rms}}{I_{rms}} = \omega L = 2\pi fL$$

Ω (inductive reactance)

$$B_L = \frac{1}{X_L} \quad \text{(siemens)}$$

(inductive susceptance.)

3) AC supply with pure capacitive load:

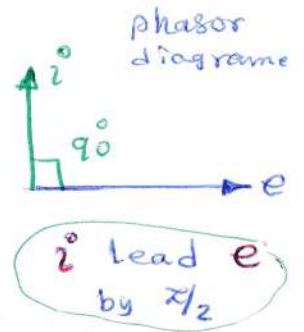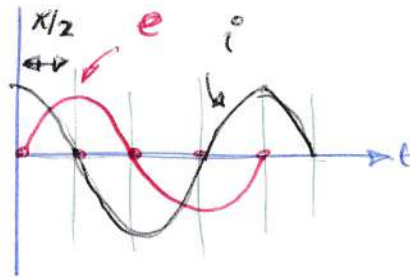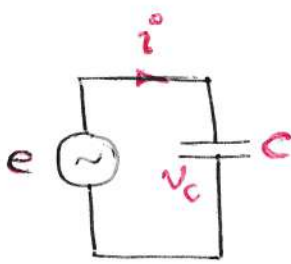

$$e = E_m \sin \omega t$$

$$i = C \frac{\Delta V_c}{\Delta t} = E_m (\omega C) \cos \omega t = E_m \omega C \sin(\omega t + \pi/2)$$

$$i = I_m \sin(\omega t + \pi/2)$$

$$X_c = \frac{E_{rms}}{I_{rms}} = \frac{1}{\omega C} = \frac{1}{2\pi f C} \quad \Omega \quad \text{capacitive reactance}$$

$$B_c = \frac{1}{X_c} = 2\pi f C \quad (\text{siemens}) \quad \text{capacitive susceptance}$$

Memory aid




Example

find X_L , I

inductive reactance $X_L = 2\pi f L$

$$X_L = 2\pi \times 60 \times 500 \text{ mH} \approx 188.5 \Omega$$
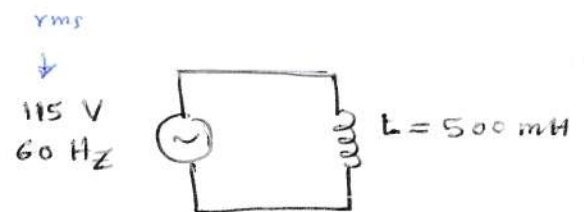
$$I = \frac{E}{X_L} = \frac{115}{188.5} = 610 \text{ mA (rms)}$$




Example

find $L = ?$

$$X_L = \frac{E}{I} = \frac{50}{7.96 \text{ mA}} = 6.28 \text{ k}\Omega$$
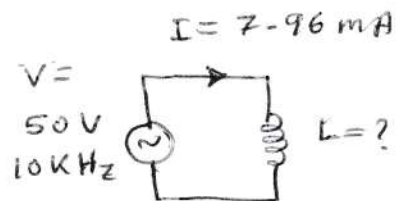
$$X_L = 2\pi f L \quad \rightarrow \quad L = \frac{X_L}{2\pi f} \approx 100 \text{ mH}$$




Example find X_c and I

$$X_c = \frac{1}{2\pi f c} = \frac{1}{2\pi \times 60 \times 50 \times 10^{-6}}$$

$$= 53.1 \Omega$$

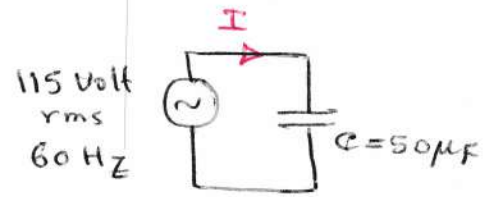
$$I = \frac{E}{X_c} = \frac{115}{53.1} = 2.2 \text{ A}$$



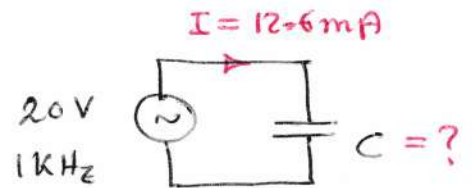
Example: find C

$$X_c = \frac{E}{I} = \frac{20}{12.6} = 1.59 \text{ k}\Omega$$



$$C = \frac{1}{2\pi f X_c} = \frac{1}{2\pi \times 1000 \times 1590} = 0.1 \mu\text{F}$$



4) Series RL in AC circuits:

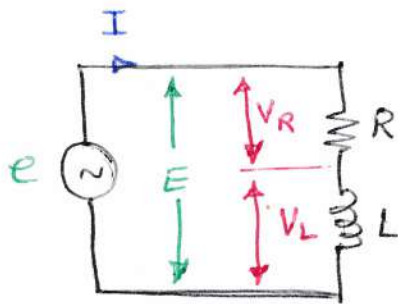

Series RL circuit.

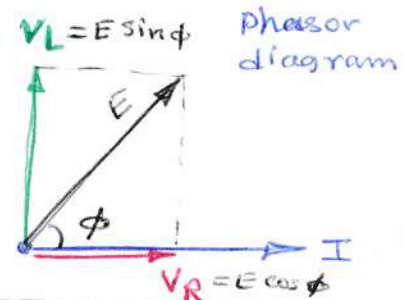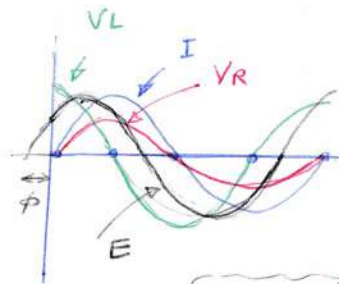


$$E = \sqrt{V_R^2 + V_L^2} \quad \tan^{-1}(V_L/V_R)$$

$$E = V_R + j V_L \quad E = |E| \angle \phi$$

$$\frac{E}{I} = \frac{V_R}{I} + j \frac{V_L}{I}$$

$$\boxed{Z = R + j X_L} \quad \text{Impedance } \Omega$$

$$Z = |Z| \angle \phi$$

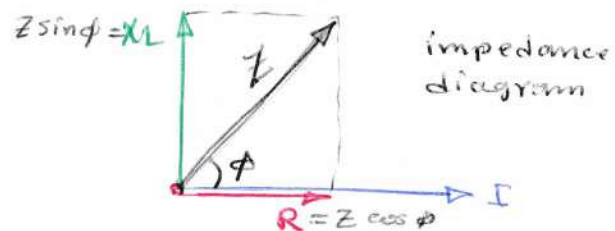


$$Z = \sqrt{R^2 + X_L^2} \quad \tan^{-1}(X_L/R)$$

$$Y = \frac{1}{Z} \quad (\text{SYPmens}) \text{ admittance.}$$

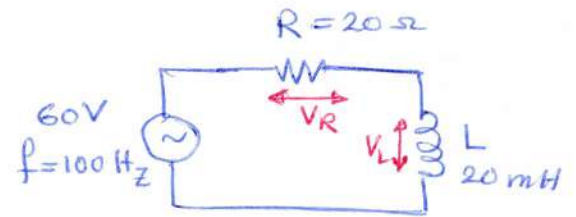Example

Calculate the inductor voltage & resistor voltage and the phase angle of current w.r.t. supply voltage.



$$X_L = 2\pi fL = 2\pi \times 100 \times 20 \times 10^{-3} = 12.57 \Omega$$

$$|Z| = \sqrt{R^2 + X_L^2} = \sqrt{(20)^2 + (12.57)^2} = 23.6 \Omega$$

$$\phi = \tan^{-1} \frac{X_L}{R} = \tan^{-1} \frac{12.57}{20} = 32.1^\circ$$

$$Z = R + jX_L = 20 + j12.57$$

$$Z = |Z| \angle \phi = 23.6 \angle 32.1^\circ$$

$$|I| = \frac{E}{|Z|} = \frac{60 \text{ V}}{23.6} = 2.54 \text{ A}$$

$$V_R = E \cos \phi = 60 \cos(32.1^\circ)$$


$$= 50.8 = I \times R$$

$$V_L = E \sin \phi = 60 \sin(32.1^\circ)$$

$$= 31.9 = I \times X_L$$


$$E = V_R + jV_L = 50.8 + j31.9$$

$$E = |E| \angle \phi = 60 \angle 32.1^\circ$$

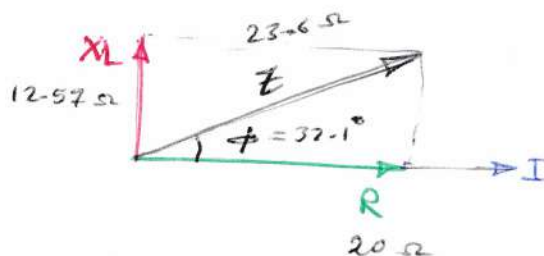

$$R = Z \cos \phi$$


$$X_L = Z \sin \phi$$

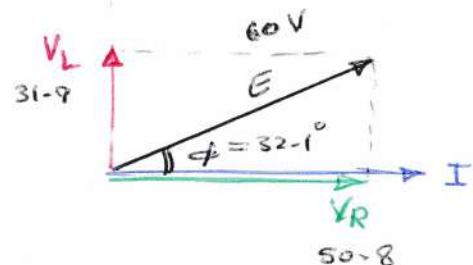


$$\phi = \tan^{-1} \left(\frac{X_L}{R} \right)$$

$$\phi = \tan^{-1} \left(\frac{V_L}{V_R} \right)$$


5) Series RC in AC circuits:

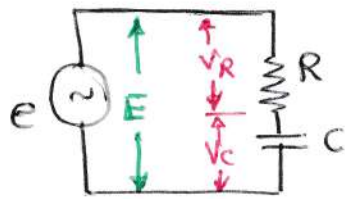

Series RC circuit

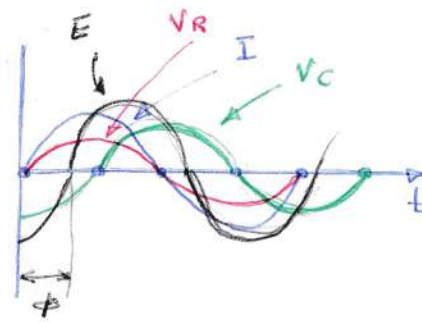

phasor diagram

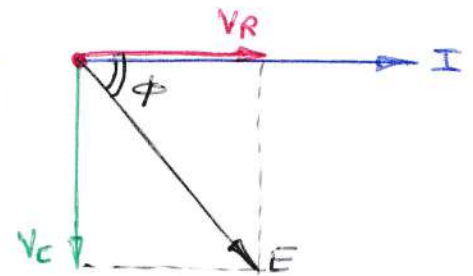


$$E = V_R - jV_C = |E| \angle \phi$$

$$|E| = \sqrt{V_R^2 + V_C^2}, \quad \phi = \tan^{-1} \frac{V_C}{V_R}$$

$$\frac{E}{I} = \frac{V_R}{I} - j \frac{V_C}{I}$$

$$Z = R - jX_C = |Z| \angle \phi$$

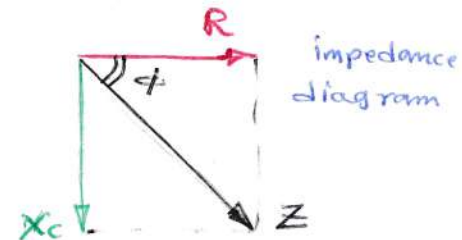

impedance diagram

$$|Z| = \sqrt{R^2 + X_C^2}$$

$$\phi = \tan^{-1} \frac{X_C}{R}$$

$$V_R = E \cos \phi, \quad V_C = E \sin \phi$$

$$R = Z \cos \phi, \quad X_C = Z \sin \phi$$

$$Y = \frac{1}{Z} \quad (\text{siemens}).$$


Example? calculate V_R , V_C , I and ϕ of current and supply voltage.

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 300 \times 10 \times 10^{-6}} = 53 \Omega$$

$$|Z| = \sqrt{R^2 + X_C^2} = \sqrt{(47)^2 + (53)^2} = 71 \Omega$$

$$\phi = \tan^{-1} \frac{X_C}{R} = \tan^{-1} \frac{53}{47} = 48.5^\circ$$

$$|I| = \frac{E}{|Z|} = \frac{100}{71} = 1.41 \text{ A}$$

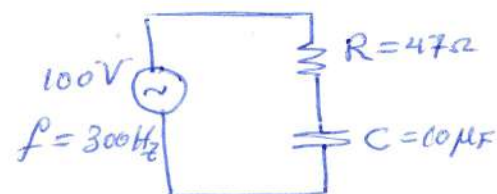


Example \sin^{-1}


$$V_R = E \cos \phi = 100 \cos (48.5) = 66.3$$

OR $V_R = IR = 1.41 \times 47 = 66.3$
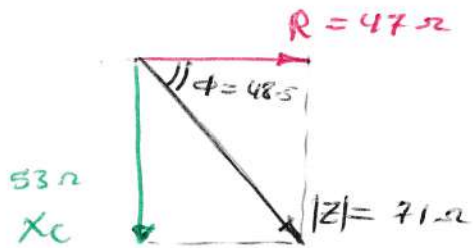
$$V_C = E \sin \phi = 100 \sin (48.5) = 74.9 = I \times X_C$$





impedance diagram

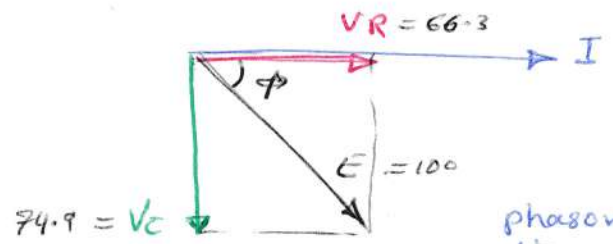


phasor diagram

Current lead E by ϕ
E Lag I by ϕ

6) series RLC in AC circuits:

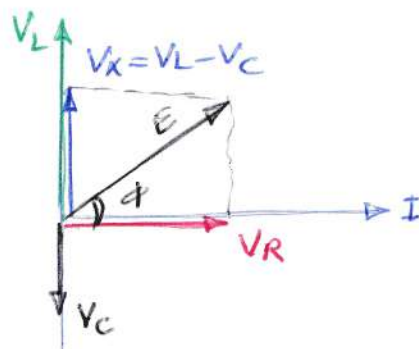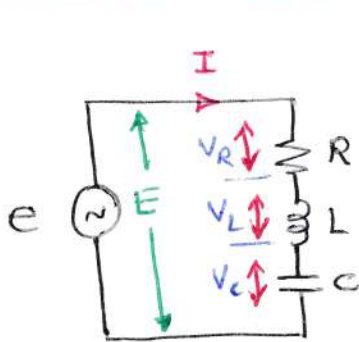

phasor diagram for $X_L > X_C$

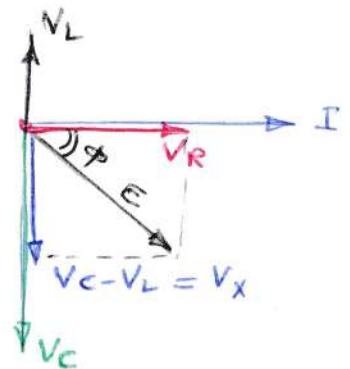

phasor diagram for $X_L < X_C$

$$E = V_R + j(V_L - V_C) = V_R + jV_x$$

$$V_x = V_L - V_C$$

$$E = |E| \angle \phi = \sqrt{V_R^2 + V_x^2} \angle \tan^{-1} \frac{V_x}{V_R}$$

$$|E| \angle \phi = |E| \cos \phi + j|E| \sin \phi$$


$$\underline{Z} = R + j(X_L - X_C) = |Z| \angle \phi$$

$$X_L - X_C = X_{eq}$$

$$|Z| = \sqrt{R^2 + X_{eq}^2}$$


$$\phi = \tan^{-1} \frac{X_{eq}}{R}$$
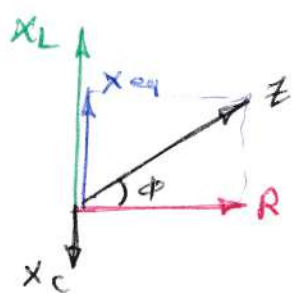
$$\underline{Z} \angle \phi = Z \cos \phi + jZ \sin \phi = R + jX_{eq}$$



impedance diagram

$$X_L > X_C$$

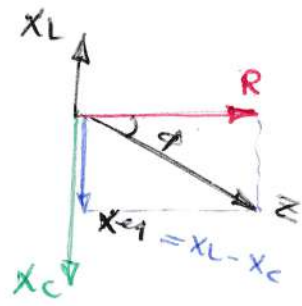


$$X_C > X_L$$

Example

series RLC circuit

Calculate I, V_R, V_L, V_C, ϕ

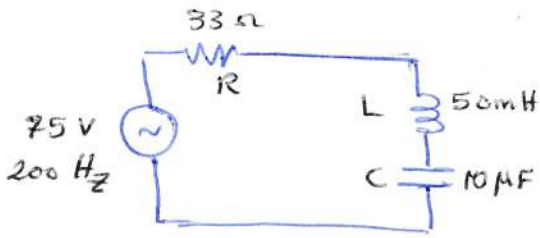

$$X_L = 2\pi fL = 62.8 \Omega$$

$$X_C = \frac{1}{2\pi fC} = 79.6 \Omega$$

$$\underline{Z} = R + j(X_L - X_C) = 33 + j(62.8 - 79.6) = 33 - j16.8 \Omega$$

$$X_{eq} = X_L - X_C = -16.8 \text{ Capacitive reactance.}$$


$$\underline{Z} = \sqrt{R^2 + X_{eq}^2} \angle \tan^{-1} \frac{X_{eq}}{R} = 37 \angle -27^\circ$$

$$I = \frac{E}{Z} = \frac{75}{37 \angle -27^\circ} = 2 \angle 27^\circ$$

$$V_R = I * R = 67 \text{ volt.}$$


$$V_L = I * X_L = 127 \text{ volt.}$$

$$V_C = I * X_C = 162 \text{ volt.}$$

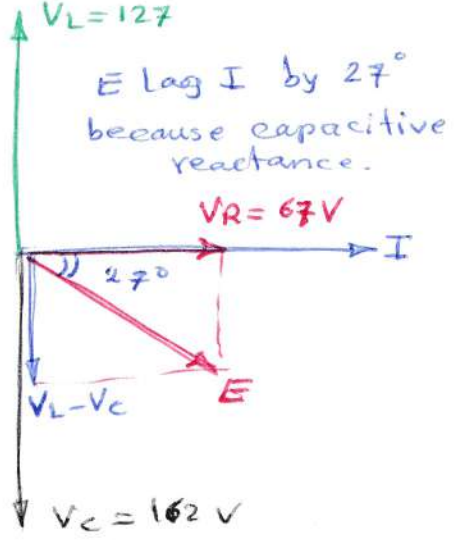

7) Resonance in series RLC .

impedance.
 $Z = R + j(X_L - X_C)$

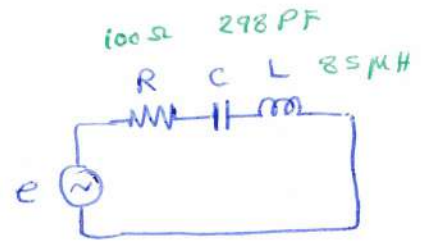

when $X_L = X_C \Rightarrow X_{eq} = 0$



$Z = R + j0 = R$ (Resistance only) - minimum impedance.

f_r : resonance frequency at which $X_L = X_C$

$$2\pi f_r L = \frac{1}{2\pi f_r C}$$

$$\Rightarrow f_r = \frac{1}{2\pi\sqrt{LC}}$$

$f_r = 1 \text{ MHz}$

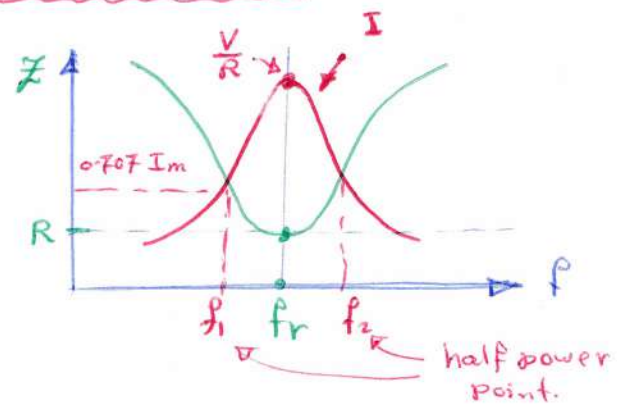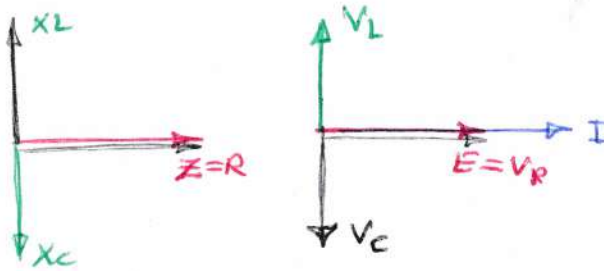

(Q) factor :

voltage magnification factor.

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} \text{ at } f_r$$

(example)

for LCR circuit at

$f_r = 500 \text{ kHz}$


$L = 100 \mu\text{H}, C = 1 \text{ nF}$

$R = 25 \Omega$


$$Q = \frac{1}{25} \sqrt{\frac{100 \times 10^{-6}}{1 \times 10^{-9}}} = 12.6$$

if $L = 200 \mu\text{H} \Rightarrow Q \approx 25$

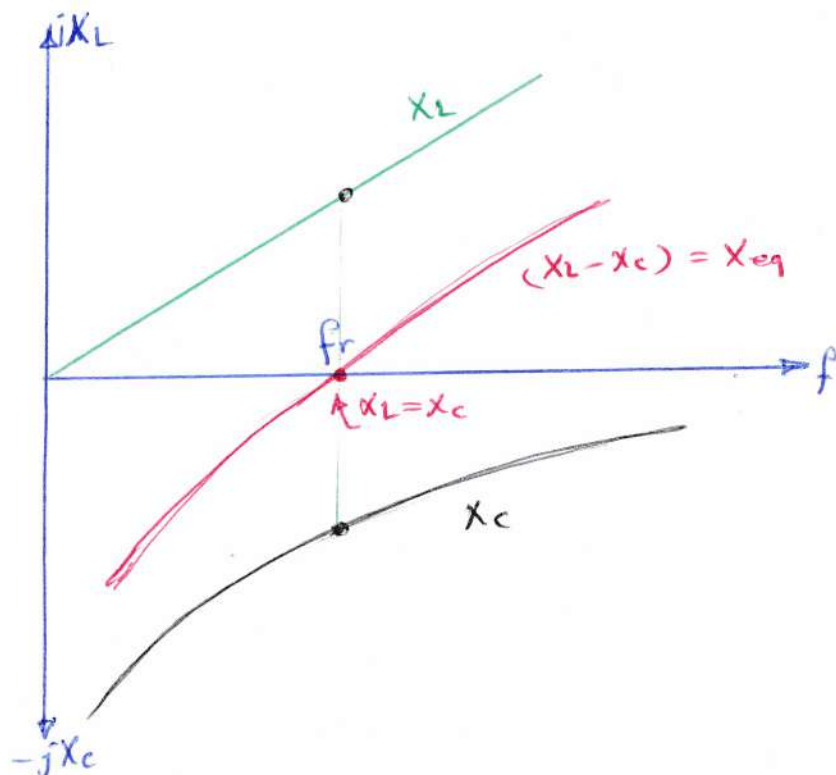
$$C = \frac{1}{4\pi^2 f_r^2 L} = 500 \text{ pF}$$



2) Parallel RLC Circuits:

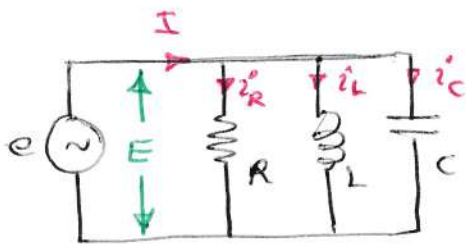

phasor diagram

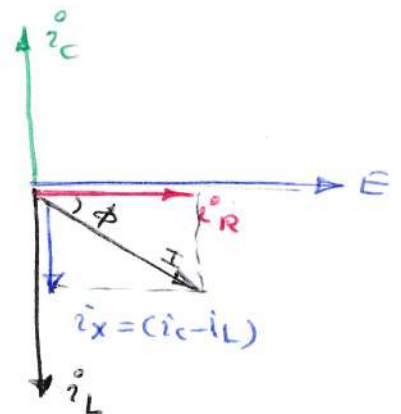

$$I = i_R + j(i_C - i_L)$$

$$I = i_R + j i_x$$

$$i_x = i_C - i_L$$

$$I = |I| \angle \phi = \sqrt{i_R^2 + i_x^2} \angle \tan^{-1} \frac{i_x}{i_R}$$

$$\frac{I}{E} = \frac{i_R}{E} + j \left(\frac{i_C}{E} - \frac{i_L}{E} \right)$$

$$\frac{1}{Z} = \frac{1}{R} + j \left(\frac{1}{X_C} - \frac{1}{X_L} \right)$$

$$Y = G + j(B_C - B_L)$$

admittance

inductive susceptance

conductance

capacitive susceptance

$$Y = G + j B_{eq}$$


$$B_{eq} = B_C - B_L$$

$$Y = |Y| \angle \phi$$

$$|Y| = \sqrt{G^2 + B_{eq}^2}$$


$$\phi = \tan^{-1} \left(\frac{B_{eq}}{G} \right)$$

admittance diagram

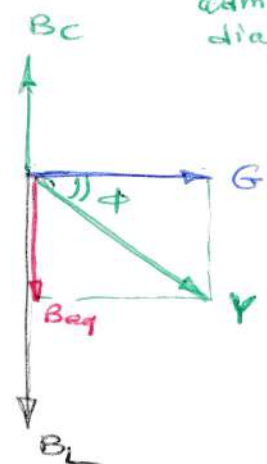

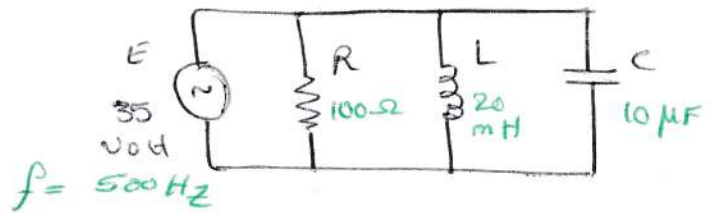Example

- Calculate i_R, i_L, i_C, I
- Determine the phase angle of I with respect to E .
- draw the phasor and admittance diagrams.



$$X_L = 2\pi fL = 62.8 \Omega$$

$$X_C = \frac{1}{2\pi fC} = 31.8 \Omega$$

$$i_R = \frac{E}{R} = \frac{35}{100} = 350 \text{ mA}$$

$$i_L = \frac{E}{X_L} = \frac{35}{62.8} = 557 \text{ mA}$$

$$i_C = \frac{E}{X_C} = 1.1 \text{ A}$$

$$i_x = i_C - i_L = 1.1 - 0.557 = 0.543 \text{ A}$$

$$I = i_R + j i_x = (0.35 + j 0.543) \text{ A}$$

$$I = \sqrt{i_R^2 + i_x^2} \angle \tan^{-1} \frac{i_x}{i_R} = \sqrt{(0.35)^2 + (0.543)^2} \angle \tan^{-1} \frac{0.543}{0.35}$$

$$I = 0.646 \angle 57.2^\circ$$

$$G = \frac{1}{R} = 10 \text{ mS}$$

$$B_L = \frac{1}{X_L} = 15.9 \text{ mS}$$

$$B_C = \frac{1}{X_C} = 31.4 \text{ mS}$$



$$B_{eq} = B_C - B_L = 15.5 \text{ mS}$$

$$Y = \sqrt{G^2 + B_{eq}^2} \angle \tan^{-1} \frac{B_{eq}}{G}$$

$$Y = 18.4 \text{ mS} \angle 57.2^\circ$$

$$Z = \frac{1}{Y} = \frac{1}{18.4 \text{ mS} \angle 57.2^\circ}$$


$$Z = 54.3 \Omega \angle -57.2^\circ$$

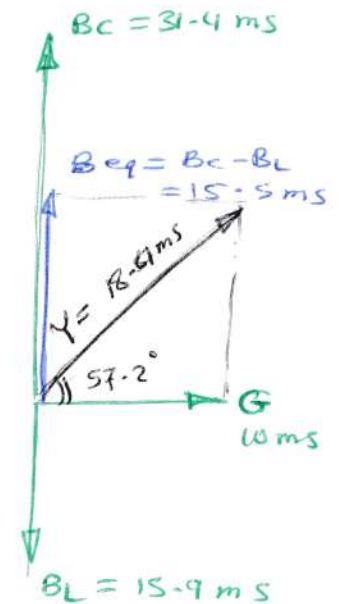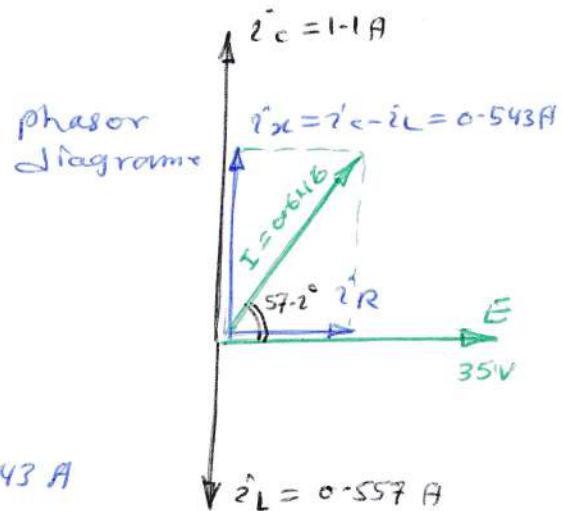

9) Resonance in parallel RLC



$$Y = \frac{1}{R_p} - j \frac{1}{X_L} + j \frac{1}{X_C}$$

$$I = i_R + j(i_C - i_L)$$

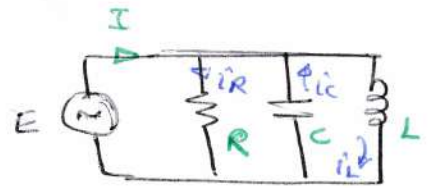

When $i_C = i_L \Rightarrow I = i_R$ (Resonance)


then E in phase with I

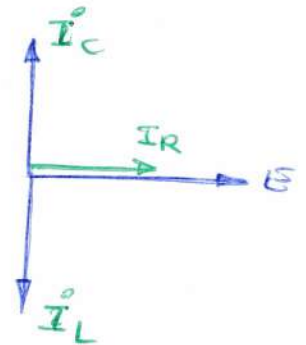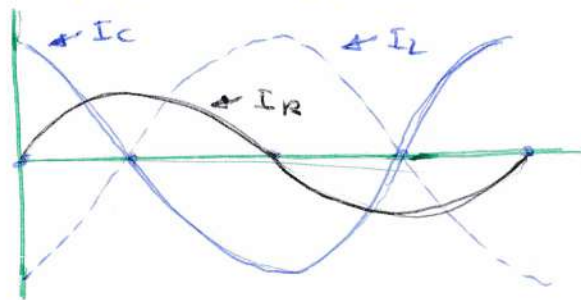

* for parallel RLC circuits

we have maximum Z impedance at f_r and minimum current.

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

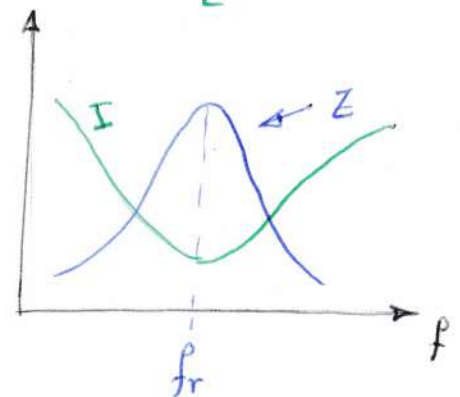

Example:



$L = 100 \mu\text{H}$, $R = 12 \Omega$, C Variable
 $200 \text{ pF} \leq C \leq 300 \text{ pF}$, find f_r range.

$$f_{r_{\min}} = \frac{1}{2\pi\sqrt{LC_{\max}}} = \frac{1}{2\pi\sqrt{100 \times 10^{-6} \times 300 \times 10^{-12}}} = 919 \text{ kHz}$$

$$f_{r_{\max}} = \frac{1}{2\pi\sqrt{LC_{\min}}} = \frac{1}{2\pi\sqrt{100 \times 10^{-6} \times 200 \times 10^{-12}}} = 1.13 \text{ MHz}$$


$$919 \text{ kHz} \leq f_r \leq 1.13 \text{ MHz}$$

10) Impedances in series :

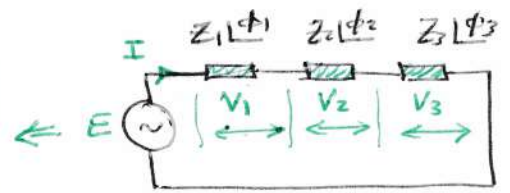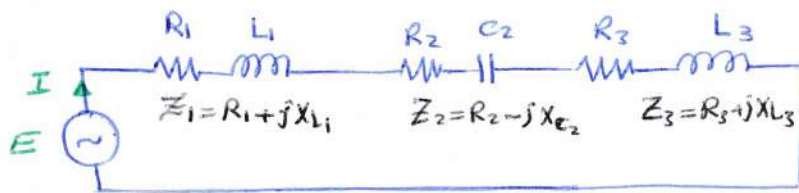

conversion from polar to rectangular form.

impedances in series

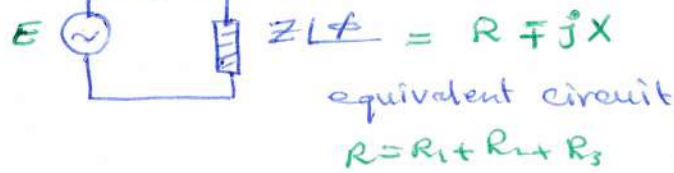

Example :

For circuit shown above $Z_1 = 70.7 \angle 45^\circ \Omega$
 $Z_2 = 92.4 \angle 33^\circ \Omega$, $Z_3 = 67 \angle 60^\circ \Omega$, $E = 100 \text{ volt}$.
 OR $E = 100 \angle 0^\circ \text{ volt}$.

- ① find I ② draw the phasor diagram of E & I .
- ③ find V_1 , V_2 , V_3 and draw complete phasor diagram.

Solution :

① $Z = Z_1 + Z_2 + Z_3$

$$Z_1 = 70.7 \cos 45^\circ + j 70.7 \sin 45^\circ = 50 + j 50 \Omega$$

$$Z_2 = 92.4 \cos 33^\circ + j 92.4 \sin 33^\circ = 80 - j 46.2 \Omega$$

$$Z_3 = 67 \cos 60^\circ + j 67 \sin 60^\circ = 33.5 + j 58 \Omega$$

$$\therefore Z = (50 + 80 + 33.5) + j (50 - 46.2 + 58) = 163.5 + j 61.8 \Omega$$


$$= 174.8 \angle 20.7^\circ$$

inductive impedance.

$$I = \frac{E}{Z} = \frac{100 \angle 0^\circ}{174.8 \angle 20.7^\circ} = 0.572 \angle -20.7^\circ \text{ A}$$

I Lag E by 20.7°

②

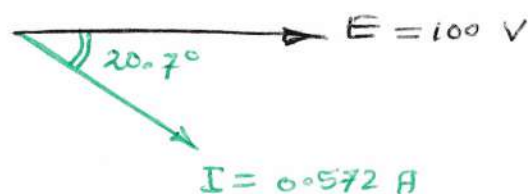

(2)

$$E = 100 \angle 0^\circ \quad \therefore Z = Z_1 + Z_2 + Z_3 = 174.8 \angle 20.7^\circ \Omega$$

$$V_1 = E * \frac{Z_1}{Z_1 + Z_2 + Z_3} = 100 \angle 0^\circ * \frac{70.7 \angle 45^\circ}{174.8 \angle 20.7^\circ} = 40.4 \angle 24.3^\circ \text{ V}$$

$$V_2 = E * \frac{Z_2}{Z_1 + Z_2 + Z_3} = 100 \angle 0^\circ * \frac{72.4 \angle 330^\circ}{174.8 \angle 20.7^\circ} = 52.9 \angle 309.3^\circ \text{ Volt}$$


$$V_3 = E * \frac{Z_3}{Z_1 + Z_2 + Z_3} = 100 \angle 0^\circ * \frac{67 \angle 60^\circ}{174.8 \angle 20.7^\circ} = 38.3 \angle 39.3^\circ \text{ Volt}$$

OR

$$V_1 = I * Z_1 = 0.572 \angle -20.7^\circ * 70.7 \angle 45^\circ = 40.4 \angle 24.3^\circ \text{ Volt}$$


$$V_2 = I * Z_2$$

$$V_3 = I * Z_3$$

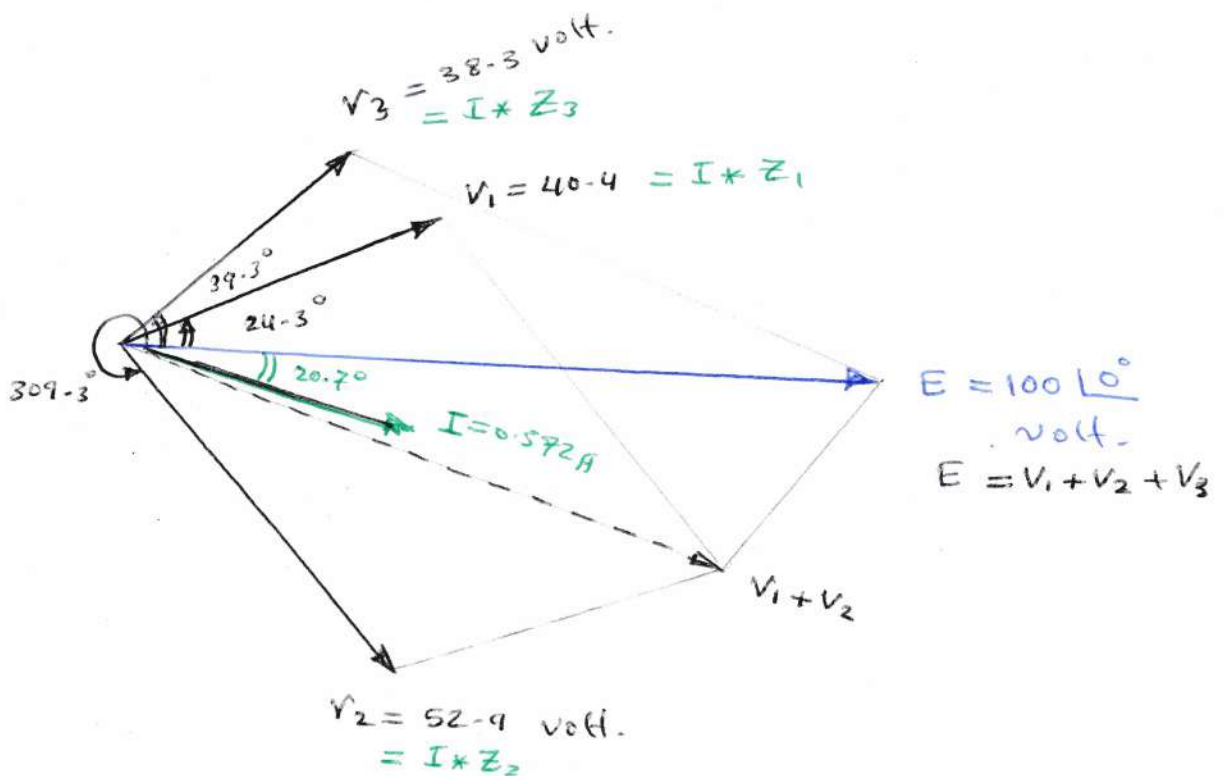



complete phasor diagram.

11) Impedances in parallel

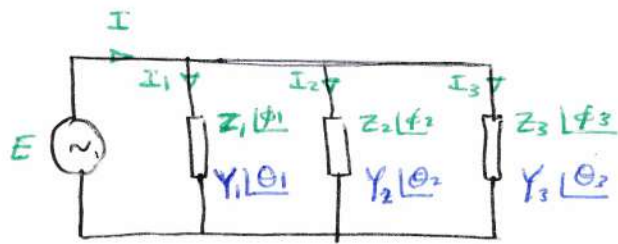


$$Y_1 \angle \theta_1 = \frac{1}{Z_1 \angle \phi_1} = \frac{1}{Z_1} \angle -\phi_1 = G_1 - jB_1$$
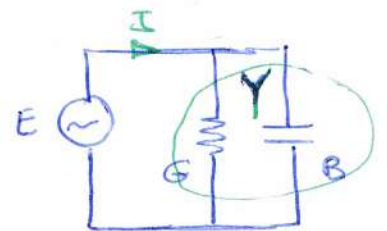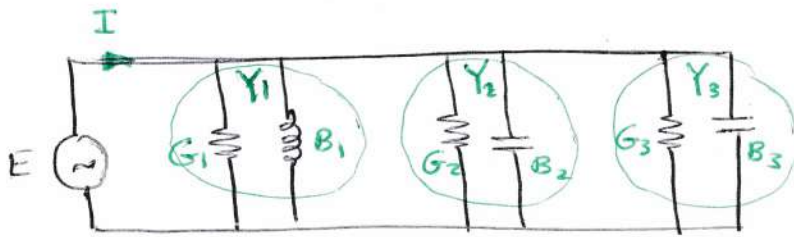
$$Y_2 \angle \theta_2 = \frac{1}{Z_2} \angle -\phi_2 = G_2 - jB_2$$



$$Y = Y_1 + Y_2 + Y_3 = G - jB = |Y| \angle \theta$$
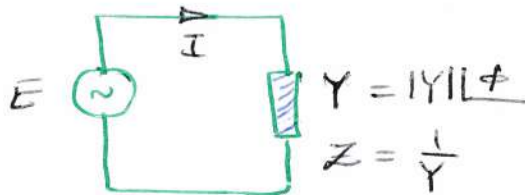
$$G = G_1 + G_2 + G_3 \quad , \quad B = B_1 + B_2 + B_3$$



equivalent circuit.

Example

For the parallel circuit shown above if

$$Z_1 = 1606 \angle 51^\circ \Omega \quad , \quad Z_2 = 977 \angle -33^\circ \Omega \quad , \quad Z_3 = 953 \angle -19^\circ \Omega$$

$E = 33$ volt. find:

① Z_{total} and I_1, I_2, I_3, I

② draw the complete phasor diagram of currents.

solution:

$$\textcircled{1} \quad Y_1 = \frac{1}{Z_1} = \frac{1}{1606 \angle 51^\circ} = 622.7 \angle -51^\circ \mu S = \underline{392 - j484} \mu S$$

$$Y_2 = \frac{1}{Z_2} = 1.02 \angle 33^\circ \text{ mS} = \underline{855 + j556} \mu S$$

$$Y_3 = \frac{1}{Z_3} = 1.05 \angle 19^\circ \text{ mS} = \underline{993 + j342} \mu S$$

$$\begin{aligned}
 Y &= Y_1 + Y_2 + Y_3 = (392 + 855 + 993) \mu S + j(-484 + 556 + 342) \mu S \\
 &= 2.24 + j 0.414 \text{ mS} \equiv G_{eq} + j B_{eq} \\
 &= 2.28 \angle 10.5^\circ \text{ mS}
 \end{aligned}$$

$$Z = \frac{1}{Y} = \frac{1}{2.28 \angle 10.5^\circ} = 439 \angle -10.5^\circ \Omega$$

$$\begin{aligned}
 I &= EY = 33 \angle 0^\circ * 2.28 \angle 10.5^\circ \text{ mS} = 75.2 \text{ mA} \angle 10.5^\circ \\
 &= \frac{E}{Z}
 \end{aligned}$$

$$I_1 = \frac{E}{Z_1} = EY_1 = 33 \angle 0^\circ * 622.7 \angle -51^\circ \mu S = 20.5 \angle -51^\circ \text{ mA}$$


$$I_2 = \frac{E}{Z_2} = EY_2 = 33.8 \angle 33^\circ \text{ mA}$$

$$I_3 = \frac{E}{Z_3} = EY_3 = 34.6 \angle 19^\circ \text{ mA}$$


OR using current divider

$$I_1 = I \frac{Y_1}{Y}, \quad I_2 = I \frac{Y_2}{Y}, \quad I_3 = I \frac{Y_3}{Y}$$
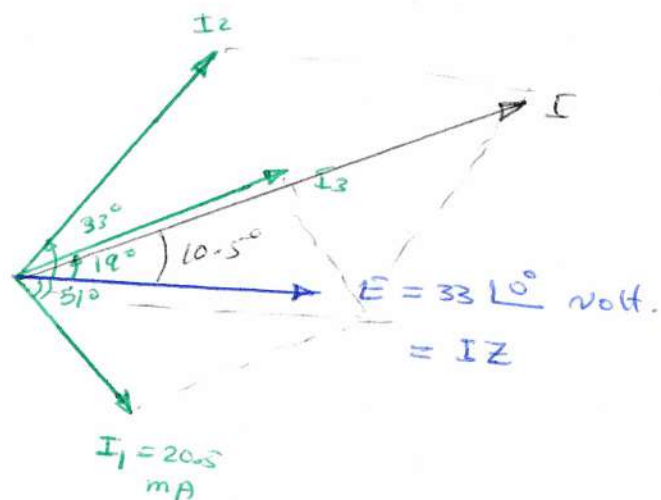
$$I = I_1 + I_2 + I_3 \quad (\text{phasor sum}).$$



12) Impedances in series and parallel:

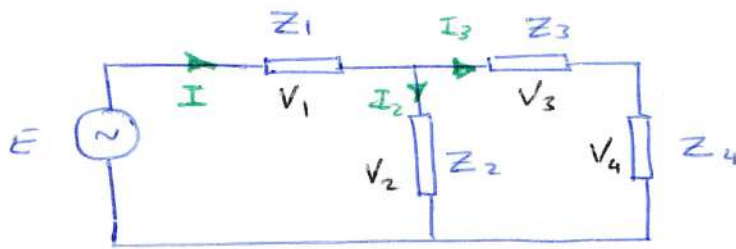

Note
all calculation
in complex form
or polar form.

$$Z_{eq} = Z_1 + [Z_2 \parallel (Z_3 + Z_4)]$$

$$I = \frac{E}{Z_{eq}} \quad ; \quad I_2 = I * \frac{(Z_3 + Z_4)}{Z_2 + Z_3 + Z_4}$$

$$I_3 = I * \frac{Z_2}{Z_2 + Z_3 + Z_4} \quad ; \quad I = I_2 + I_3$$

$$V_1 = I Z_1 \quad , \quad V_2 = I_2 Z_2 \quad , \quad V_3 = I_3 Z_3 \quad , \quad V_4 = I_3 Z_4$$

Example

for the circuit shown above if $Z_1 = 560 - j620 \Omega$
 $Z_2 = 330 + j470 \Omega$, $Z_3 = 390 + j270 \Omega$, $Z_4 = 220 - j220 \Omega$
 $E = 30$ volt. find I_2

$$Z_5 = Z_3 + Z_4 = 610 + j50 = 612 \angle 4.7^\circ \Omega$$

$$Z_2 = 330 + j470 \Omega = 574 \angle 54.9^\circ \Omega$$

$$Z_2 \parallel Z_5 = \frac{Z_2 Z_5}{Z_2 + Z_5} = 329 \angle 30.6^\circ = 283 + j167 \Omega$$

$$Z_{eq} = Z_1 + (Z_2 \parallel Z_5) = (560 - j620) + (283 + j167) = 843 - j453 \Omega$$

$$= 957 \angle -28.3^\circ$$

$$I = \frac{E}{Z_{eq}} = \frac{30 \angle 0^\circ}{957 \angle -28.3^\circ} = 31.3 \text{ mA} \angle 28.3^\circ$$

$$I_2 = I * \frac{Z_5}{Z_2 + Z_5} = 31.3 \text{ mA} \angle 28.3^\circ * \frac{612 \angle 4.7^\circ}{(330 + j470) + (610 + j50)}$$

$$= 17.8 \text{ mA} \angle 4^\circ$$

13) power in AC circuits

* Power dissipated in a resistance:


$$P = E I = \frac{E_m}{\sqrt{2}} * \frac{I_m}{\sqrt{2}} = \frac{1}{2} E_m I_m = \frac{1}{2} P_m \quad \text{with}$$

$$P = \frac{E^2}{R} = I^2 R = \frac{E I}{R}$$

* power in an inductance:

$$P = e * i = E_m I_m \sin(\omega t) \sin(\omega t - 90^\circ)$$

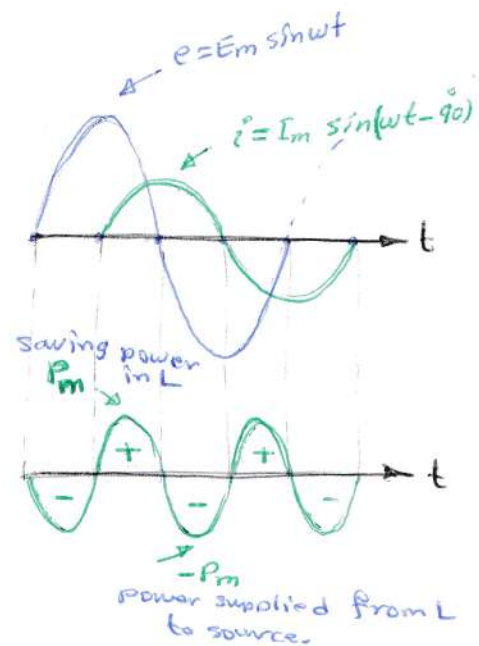∴ P ⇒ as shown 0 → P_m → 0 → -P_m
average power = 0




* power in a capacitance:

$$P = e * i = E_m I_m \sin(\omega t) - \sin(\omega t - 90^\circ)$$

∴ P ⇒ as shown
0 → P_m → 0 → -P_m →

average power is zero

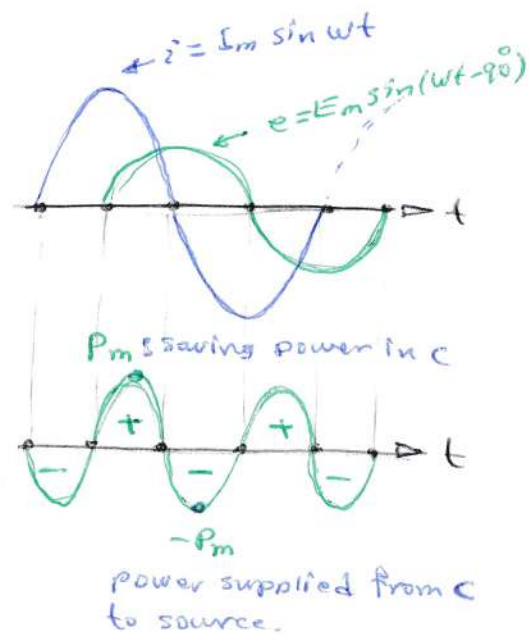

True power and reactive power :

* True power = power dissipated in Resistance.

$$\begin{aligned} &= P = EI \quad (\text{watt}) \quad (\text{heating resistance}) \\ &= I^2 R = E^2/R \end{aligned}$$

* Reactive power = power supplied to reactance X_L or X_C

$$= Q \quad (\text{average} = 0).$$

$$Q_L = \text{reactive power for } L = E_L I_L = I_L^2 X_L = \frac{E_L^2}{X_L} \quad (\text{VAR})$$

$$Q_C = \text{reactive power for } C = E_C I_C = I_C^2 X_C = \frac{E_C^2}{X_C} \quad (\text{VAR})$$

VAR = Volt-ampere, reactive.

Example : calculate the power supplied when a 120 V, 60 Hz source is connected to :

(a) 60 Ω resistor (b) $L = 50 \text{ mH}$ (c) $C = 33 \mu\text{F}$

solution :

$$(a) \quad P = \frac{E^2}{R} = \frac{(120)^2}{60} = 240 \text{ watt (true power)}$$




$$(b) \quad X_L = 2\pi fL = 18.8 \Omega$$

$$Q_L = \frac{E_L^2}{X_L} = \frac{(120)^2}{18.8} = 766 \text{ VAR (reactive power)}$$

$$(c) \quad X_C = \frac{1}{2\pi fC} = 80.4 \Omega$$

$$Q_C = \frac{E_C^2}{X_C} = \frac{(120)^2}{80.4} = 179 \text{ VAR (reactive power).}$$

power in RL circuit :

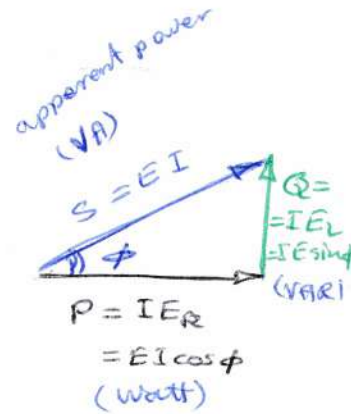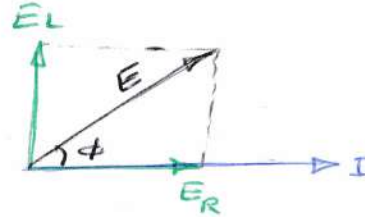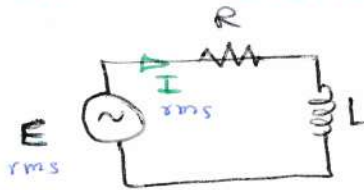

$S =$ apparent power (VA)
 $S = EI$ (VA) Volt. amper

Power triangle

$P =$ true power = resistive power = $I * \underbrace{E \cos \phi}_{E_R}$ watt

$Q =$ reactive power = $I * \underbrace{E \sin \phi}_{E_L}$ (VAR)

$\cos(\phi) =$ power factor = $\frac{\text{true power}}{\text{apparent power}} = \frac{P}{S}$

like efficiency

* we need to supply all ... power to load


$\cos(\phi) = 1$ (better case) , $S = P$ (no reactive power).

* for RL we have lagging power factor.

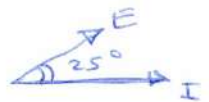Example : for series RL AC circuit.

$E = 50$ volt. , $I = 100$ mA $\angle 25^\circ$, find S, Q, P .
 power factor.


$S = EI = 50 * 100 \text{ mA} = 5 \text{ (VA)}$




$Q = EI \sin \phi = 50 * 100 \text{ mA} * \sin(25^\circ) = 2.1 \text{ (VAR)}$

$P = EI \cos \phi = 50 * 100 \text{ mA} * \cos(25^\circ) = 4.5 \text{ (watt)}$

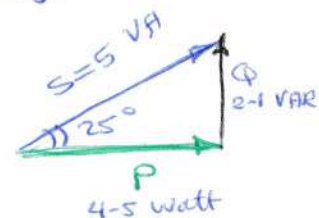
power factor = $\cos(\phi) = \cos(25^\circ) = 0.9$ Lagging
 = 90%




power in RC circuit:

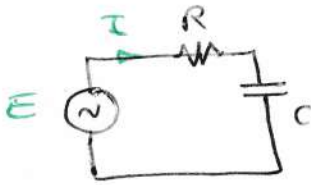

phasor diagram.

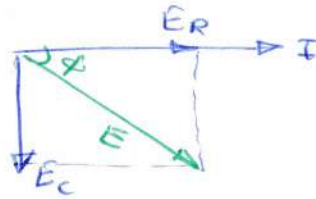

power triangle.

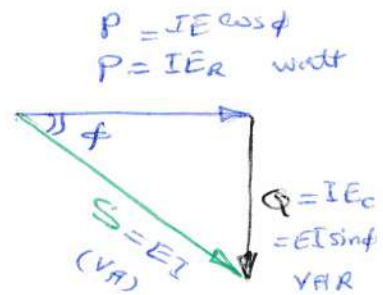

$S = EI$ Volt-ampere (VA) \Rightarrow apparent power.

$Q = IEc = EI \sin(\phi)$ (VAR) \Rightarrow reactive power

$P = IER = EI \cos(\phi)$ watt. \Rightarrow true power

power factor = $\cos(\phi)$ (leading) (I Lead E)

= true power P / apparen power S

Example: For series RC AC circuit we have:

$R = 1.2 \text{ k}\Omega$, $C = 0.1 \mu\text{F}$, $E = 45 \text{ volt}$.

$f = 1 \text{ kHz}$. find P, S, Q, power factor.


solution:

$$X_c = \frac{1}{2\pi f_c} = 1.59 \text{ k}\Omega$$

$$|Z| = \sqrt{R^2 + X_c^2} = \sqrt{(1200)^2 + (1590)^2} = 1.99 \text{ k}\Omega$$

$$\phi = \tan^{-1}\left(\frac{X_c}{R}\right) = 53^\circ$$

$$|I| = \frac{E}{|Z|} = \frac{45}{1.99 \text{ k}\Omega} = 22.6 \text{ mA}$$

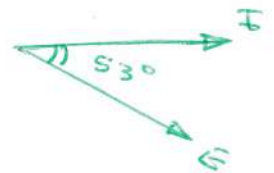

$$S = EI = 45 \times 22.6 \times 10^{-3} = 1 \text{ VA}$$

$$Q = EI \sin(\phi) = 45 \times 22.6 \times 10^{-3} \times \sin(53) = 0.81 \text{ VAR}$$

$$P = EI \cos \phi = 0.61 \text{ watt.}$$

$$= I^2 R$$

$$\text{also } Q = I^2 X_c$$


$$\text{power factor} = \cos(\phi) = \cos(53) = 0.6 \text{ Leading}$$

60% leading.

power factor correction:

$$H-W: \left. \begin{array}{l} 21.6 \cdot 1 \\ 21.6 \cdot 2 \end{array} \right\} 0.587$$

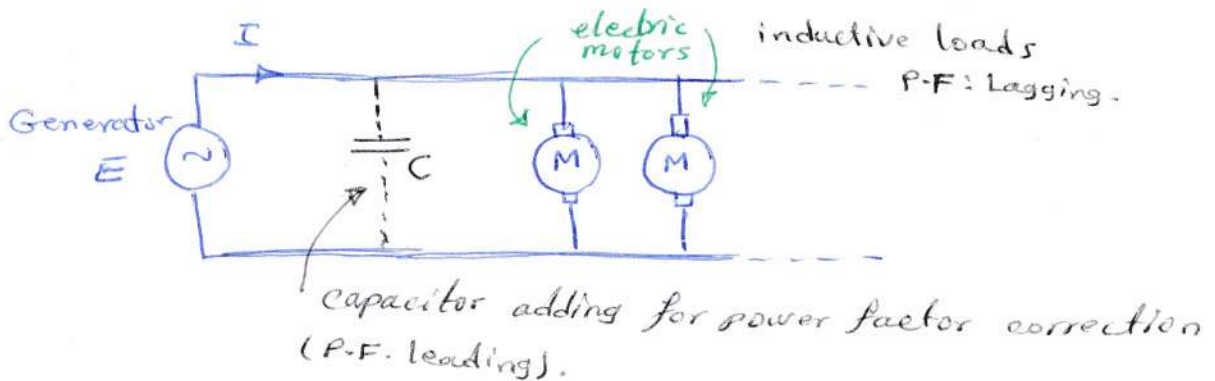For good electrical power systems $P-F. \cos \phi \approx 1$



ϕ becomes Zero $\Rightarrow P-F = \cos \phi = 1$
i.e. no reactive power. (only true power).

Example: The current taken from a 115V, 60 Hz supply is measured as 20 A with a lagging power factor of 75%. Calculate the apparent power S , true power P , reactive power Q . also determine the amount of capacitance that must be connected in parallel with the load to correct the power factors to 95% Lagging.

$$* P-F = \cos \phi = 75\% = 0.75 \text{ Lag} \Rightarrow \phi = \cos^{-1}(0.75) = 41.4^\circ$$

$$S = EI = 115 \times 20 = 2.3 \text{ KVA}$$

$$P = EI \cos \phi = 115 \times 20 \times 0.75 = 1.725 \text{ KW}$$

$$Q_L = EI \sin \phi = \frac{2300}{S} \times \sin(41.4^\circ) = 1.52 \text{ KVAR}$$

reactive power

$$* \text{ For } P-F = 95\% \text{ Lag} = 0.95 \text{ Lag} \Rightarrow \phi = 18.2^\circ$$

$$P = I^2 R = EI \cos \phi = 1725 \text{ watt remains at this value.}$$

$$S = EI = \frac{P}{\cos \phi} = \frac{1725}{0.95} = 1820 \text{ VA (new value)}$$

$$Q = EI \sin \phi = 1820 \times \sin(18.2^\circ) = 568 \text{ VAR (new value)}$$

$$Q = Q_L - Q_c \Rightarrow Q_c = Q_L - Q = 1520 - 568 = 952 \text{ VAR}$$



$$Q_c = \frac{E^2}{X_c} \Rightarrow X_c = (115)^2 / 952 = 13.9 \Omega$$

$$X_c = 1/2\pi f C \Rightarrow C = 191 \mu F$$

Chapter (13)

Three-Phase AC systems


Generation of 3 phase voltage :

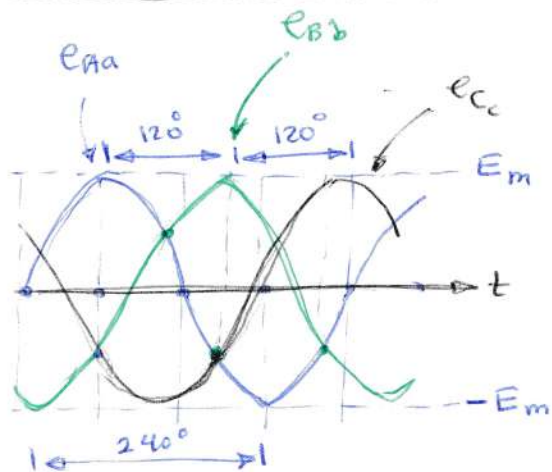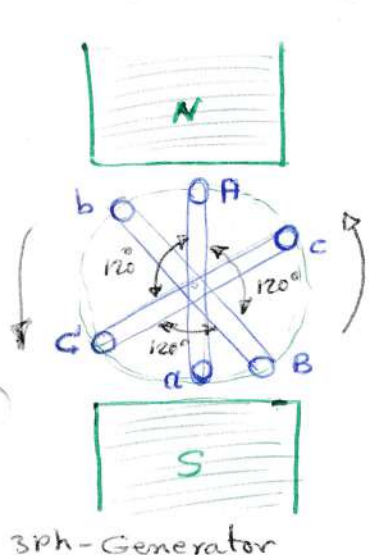

Three phase waveform


$$E_{Aa} = E_m \sin \alpha$$
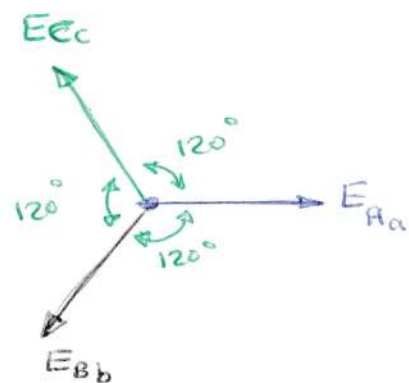
$$E_{Bb} = E_m \sin(\alpha - 120^\circ) ; E_{Cc} = E_m \sin(\alpha - 240^\circ)$$




phasor diagram of voltage.

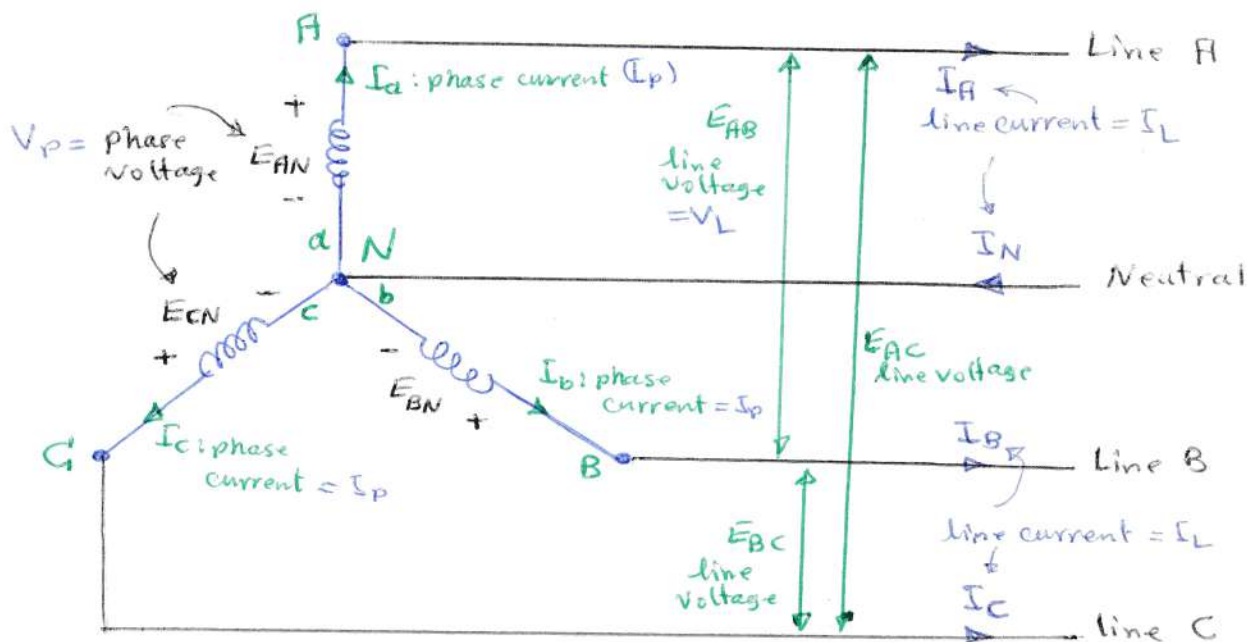3-phase generator circuit and phasors in WYE Y connection



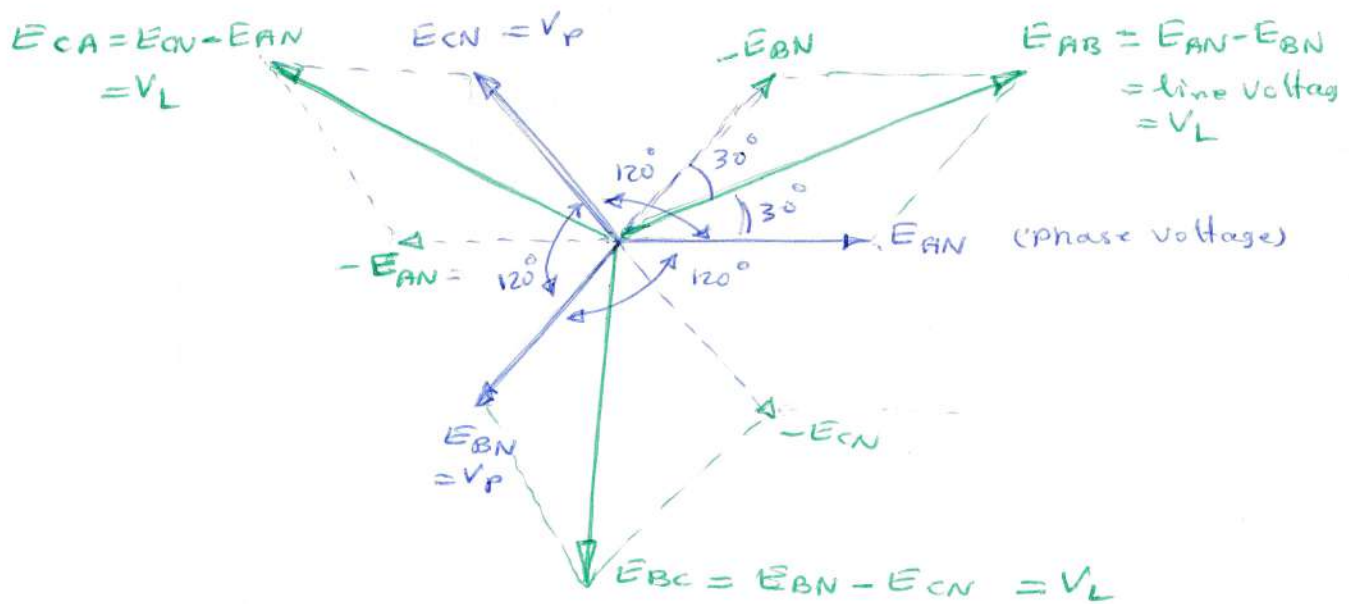$I_A = I_a$, $I_B = I_b$, $I_C = I_c \Rightarrow I_L = I_p$
 in Y connection phase current = line current.





$|E_{AN}| = |E_{BN}| = |E_{CN}| = V_p$: phase voltage.

$|E_{AB}| = |E_{BC}| = |E_{CA}| = V_L$: line voltage.

$$\begin{aligned}
 E_{AB} &= E_{AN} \cos(30^\circ) + (-E_{BN} \cos 30^\circ) \\
 &= V_p \cos(30^\circ) + V_p \cos(30^\circ) = 2 V_p \cos 30^\circ \\
 &= 1.732 V_p = \sqrt{3} V_p
 \end{aligned}$$

$$\therefore V_L = \sqrt{3} V_p \quad \& \quad I_L = I_p$$

Y-Y connection for generators and loads

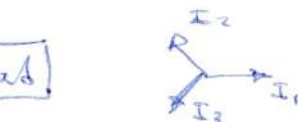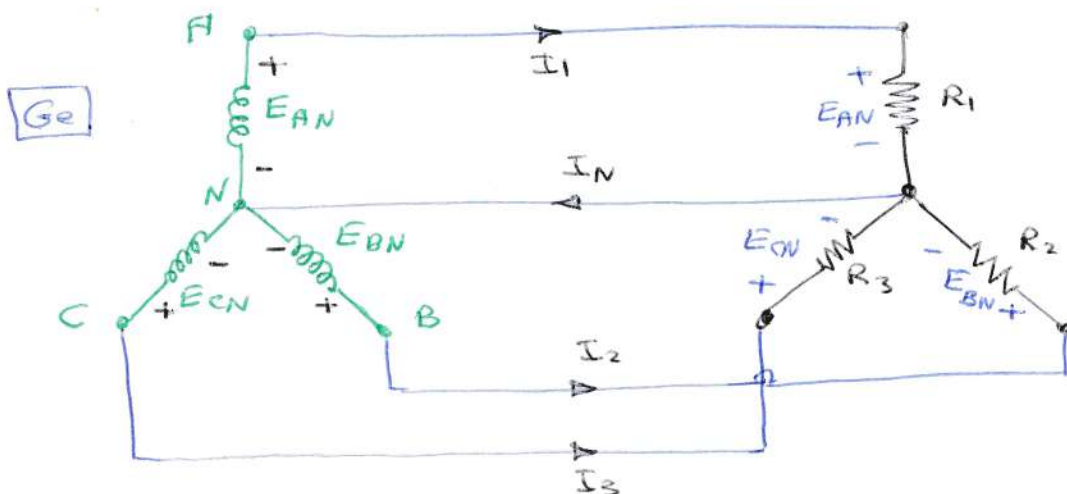

* For balanced load
 $I_1 = I_2 = I_3$
 $\therefore I_1 + I_2 + I_3 = 0$

Load currents and voltages = phase currents & voltages for Ge.

Note: Load R_1, R_2, R_3 can be used Z_1, Z_2, Z_3 with the same analysis.

$$P_p = V_p I_p \cos(\phi) \quad \text{watt} \quad (\text{phase power})$$

$$P = P_1 + P_2 + P_3 = 3 V_p I_p \cos \phi \quad \text{watt.}$$

$$V_L = \sqrt{3} V_p, \quad I_L = I_p.$$

$P = \sqrt{3} V_L I_L \cos \phi = 3 V_p I_p \cos \phi$	True power (Watt)
$Q = \sqrt{3} V_L I_L \sin \phi = 3 V_p I_p \sin \phi$	Reactive power (VAR)
$S = \sqrt{3} V_L I_L = 3 V_p I_p$	apparent power (VA)
$P.F. = \cos \phi = \frac{P}{S}$	

Example: 3-ph load resistors R_1, R_2 and R_3 have:

① equal values = 100Ω

② $100 \Omega, 200 \Omega, 50 \Omega$

$V_p = 100V$, find line current I_L , Neutral current I_N , line voltage V_L . (see figure before).


Solution:

① $E_{AN} = E_{BN} = E_{CN} = V_p = 100 \text{ Volt.}$

$I_L = I_1 = I_2 = I_3$ (balanced load.)

$I_L = V_p / R_1 = 100 / 100 = 1 \text{ A}$

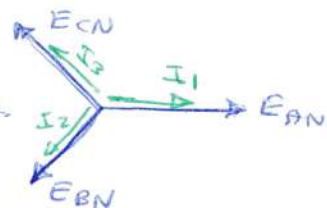$I_N = I_1 + I_2 + I_3 = 0$; $V_L = \sqrt{3} V_p = 173.2 \text{ Volt.}$



$$I_1 = \frac{E_{AN}}{R_1} = \frac{100 \angle 0^\circ}{100 \Omega} = 1 \angle 0^\circ = 1 + j0 \text{ A}$$

$$I_2 = \frac{E_{BN}}{R_2} = \frac{100 \angle -120^\circ}{100} = 1 \angle -120^\circ = -0.5 - j0.8 \text{ A}$$

$$I_3 = \frac{E_{CN}}{R_3} = \frac{100 \angle -240^\circ}{100} = 1 \angle -240^\circ = -0.5 + j0.8$$

②

$$I_1 = \frac{E_{AN}}{R_1} = \frac{100 \angle 0^\circ}{100} = 1 \angle 0^\circ \text{ A} = 1 + j0$$

$$I_2 = \frac{E_{BN}}{R_2} = \frac{100 \angle -120^\circ}{200} = 0.5 \angle -120^\circ = -0.25 - j0.433 \text{ A}$$

$$I_3 = \frac{E_{CN}}{R_3} = \frac{100 \angle -240^\circ}{50} = 2 \angle -240^\circ = -1 + j1.73 \text{ A}$$

$$I_N = I_1 + I_2 + I_3 = -0.25 + j1.3 \text{ A} = 1.32 \angle 100.9^\circ \text{ A}$$

$$V_L = \sqrt{3} V_p = 173.2 \text{ volt as before}$$

③ if we have $Z_1 = 100 \Omega$, $Z_2 = 100 - j40 \Omega = 107.7 \angle -21.8^\circ$
 $Z_3 = 100 + j60 \Omega = 116.6 \angle 31^\circ$

find the lines currents and neutral current.

$$I_1 = \frac{E_{AN}}{Z_1} = \frac{100 \angle 0^\circ \text{ volt}}{100 \Omega} = 1 \angle 0^\circ \text{ A} = 1 + j0 \text{ A}$$

$$I_2 = \frac{E_{BN}}{Z_2} = \frac{100 \angle -120^\circ}{107.7 \angle -21.8^\circ} = 0.9 \angle -98^\circ = -0.133 - j0.92 \text{ A}$$

$$I_3 = \frac{E_{CN}}{Z_3} = \frac{100 \angle -240^\circ}{116.6 \angle 31^\circ} = 0.86 \angle -271^\circ = 0.015 + j0.858 \text{ A}$$

$$I_N = I_1 + I_2 + I_3 = 0.882 - j0.062 \text{ A} \\ = 0.884 \angle -4^\circ \text{ A}$$

Example: find for part ③ the power dissipated in the load.


$$P_1 = V_{p1} I_{p1} \cos \phi_1 = 100 \text{ V} * 1 \text{ A} * \cos(0) = 100 \text{ watt}$$

$$P_2 = V_{p2} I_{p2} \cos \phi_2 = 100 * 0.9 * \cos(21.8) \approx 86.3 \text{ w}$$

$$P_3 = V_{p3} I_{p3} \cos \phi_3 = 100 * 0.858 * \cos(31) = 73.5 \text{ w}$$


$$P_T = P_1 + P_2 + P_3 = 259.8 \text{ watt.}$$

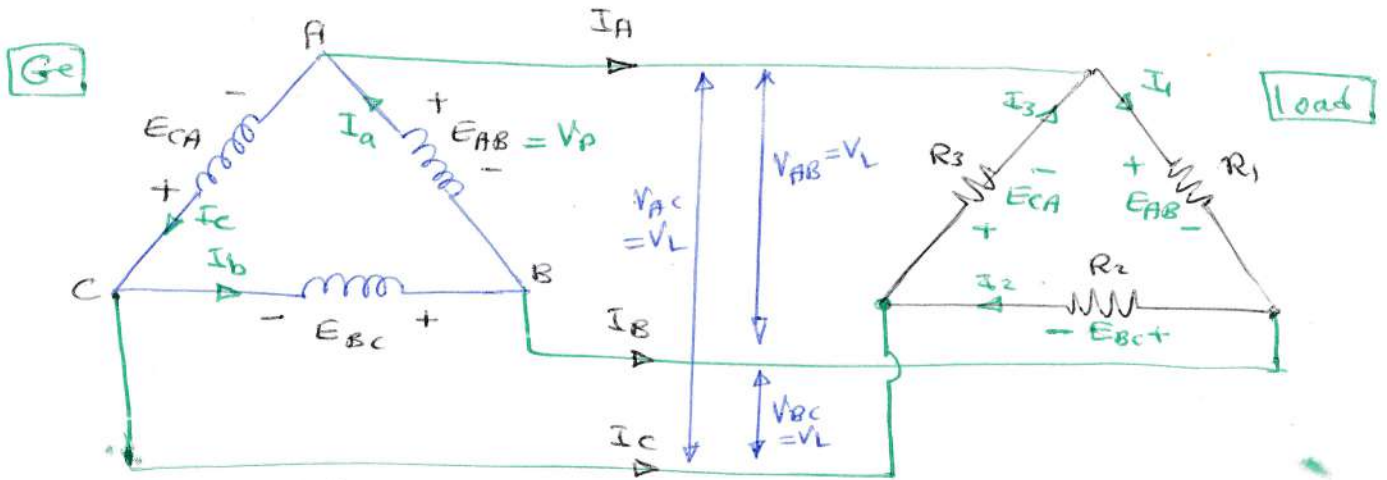Δ - Δ connections for generators and loads.



$$V_p = V_L$$

$$I_L = \sqrt{3} I_p$$

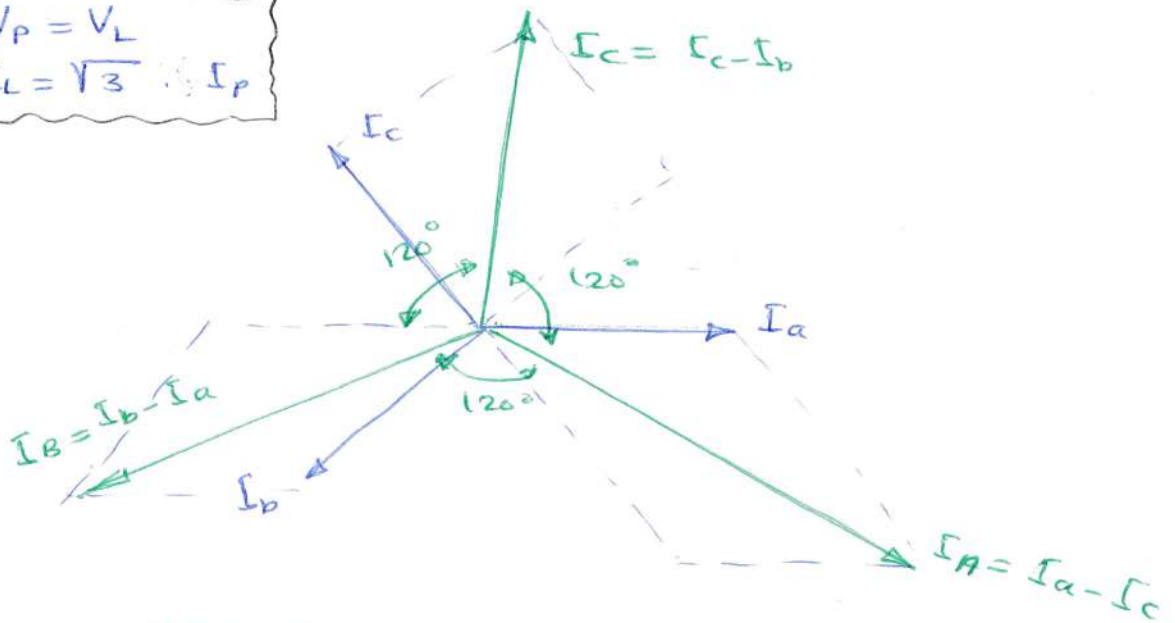

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$= 3 V_p I_p \cos \phi \quad \text{watt}$$

$$Q = \sqrt{3} V_L I_L \sin \phi \quad \text{VAR}$$

$$= 3 V_p I_p \sin \phi$$

$$S = \sqrt{3} V_L I_L \quad \text{VA}$$

$$= 3 V_p I_p$$