

**Ministry of high Education and Scientific Research  
Southern Technical University  
Technological institute of Basra  
Department of Electrical Techniques**



**Learning package**


# **Power Electronics**

**For**

**Second year students**

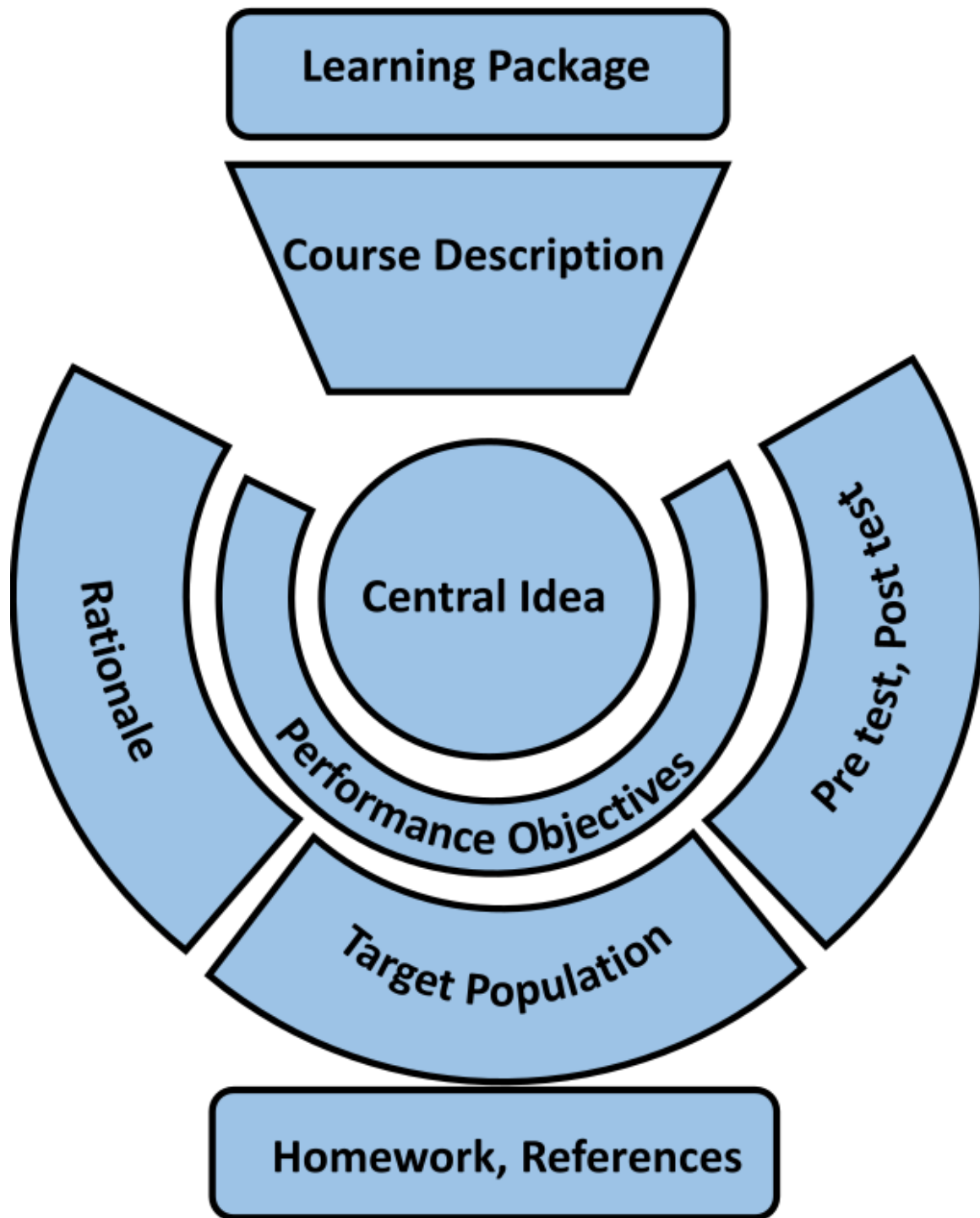**By**

**M.Sc. Humam Qahtan ALhassan  
Dep. Of Electrical Techniques  
2025**



Course Description

Course Name:	
Power electronics Applications	
Course Code:	
Semester / Year:	
Semester	
Description Preparation Date:	
14/ 05/ 2025	
Available Attendance Forms:	
Attendance only	
Number of Credit Hours (Total) / Number of Units (Total)	
60 hours/4 hour weekly/4 unit	
Course administrator's name (mention all, if more than one name)	
Name: Humam Qahtan	
Email: humam.alhasan@stu.edu.iq	
Course Objectives	
<ul style="list-style-type: none"> <li>❖ Differentiate between the general electronic circuits and power electronic devices.</li> <li>❖ Understand the main functions of power electronics: Power control and Power conversion.</li> <li>❖ Use the transistors for switching control.</li> <li>❖ Understand the various applications of UJT and op-amp circuits.</li> <li>❖ Learn the SCR structure, functions, circuits, and types.</li> <li>❖ Understand and differentiate between the different kinds of power conversion: AC-DC (rectifiers), DC-DC (choppers), DC-AC (invertors), AC-AC (convertors).</li> <li>❖ Connect the most important power electronic circuits in the Lab. and measure their parameters and characteristics.</li> </ul>	<ul style="list-style-type: none"> <li>• .....</li> <li>• .....</li> <li>• .....</li> </ul>

Teaching and Learning Strategies					
1. Cooperative Concept Planning Strategy. 2. Brainstorming Teaching Strategy. 3. Note-taking Sequence Strategy.					
Course Structure					
Weeks	Hours	Required Learning Outcomes	Unit or subject name	Learning method	Evaluation method
1	4hours	❖ Understand and differentiate between the different kinds of power conversion: AC-DC (rectifiers), DC-DC (choppers), DC-AC (invertors), AC-AC (convertors). ❖ Connect the most important power electronic circuits in the Lab. and measure their parameters and characteristics.	Chapter 5: Silicon Controlled Rectifiers (SCRs) Chapter 6: AC-DC Converters Chapter 7: DC-DC Converters (DC Choppers) Chapter 8: DC-AC Inverters Chapter 9: AC-AC Converters	1.Conducting laboratory experiments to build and test digital circuits. This enhances theoretical understanding and develops practical skills.	Weekly, Monthly, Daily and Written Exams, and Final Term Exam.
2	4hours			2.Seeking feedback from instructors and peers to identify strengths and weakness	
3	4hours			3.Reviewing concepts periodical and applying them to new problems to reinforce memory and understanding.	
4	4hours			4.Using educational software an interactive applications to better understand concepts, s	
5	4hours			5.Encouraging self-research on r topics in electronics and explori recent 7e4t4developments.	
6	4hours				
7	4hours				
8	4hours				
9	4hours				
10	4hours				
11	4hours				
12	4hours				
13	4hours				
14	4hours				
Course Evaluation					
Distribution as follows: 20 points for Midterm Theoretical Exams for the first semester, 20 points for Midterm Practical Exams for the first semester, 10 points for Daily Exams and Continuous Assessment, and 50 points for the Final Exam.					
Learning and Teaching Resources					

Required textbooks (curricular books, if any)	W.Shepherd,andL.Hulley, <b>PowerElectronicsandMotorControl</b> ,2ndedition,Camb ridgeUniversityPress,1996.
Main references (sources)	T.L. Floyd, <b>Electronic Devices</b> , 9th edition, Merrill Publishing Company, 1988.
Recommended books and references (scientific journals, reports...)	M.H.Rashid, <b>Power Electronics Handbook: Devices,CircuitsandApplications</b> ,2nd. AcademicPress:Elsevier,2007.
Electronic References, Websites	<a href="https://zlibrary-asia.se/">https://zlibrary-asia.se/</a>

**Ministry of high Education and Scientific Research  
Southern Technical University  
Technological institute of Basra  
Department of Electrical Techniques**



**Learning package**  
**In**  
**Power Electronics**  
**For**

Students of Second Year

**By**


**M.Sc. Humam Qahtan ALhassan**  
**Dep. Of Electrical Techniques**  
**2025**

# **Chapter 5**


## **Silicon Controlled Rectifiers (SCRs)**
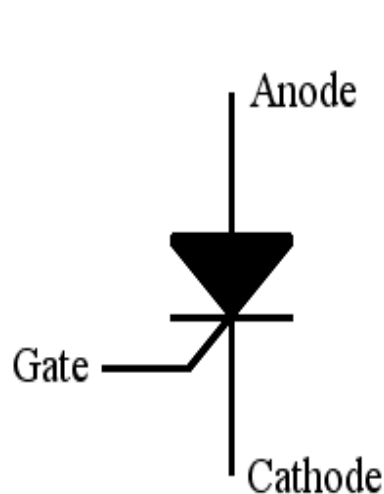
# Silicon Controlled Rectifier (SCR)


- Silicon Controlled Rectifier (or Semiconductor Controlled Rectifier) is a four layer solid state device that controls current flow.
- The name “silicon controlled rectifier” is a trade name for the type of **Thyristor** commercialized at General Electric in 1957.



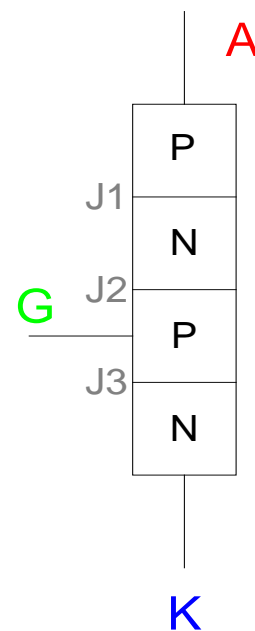- Anode and Cathode as in conventional pn junction diode.
- Gate terminal is used for controlling input signal.




**Structure**

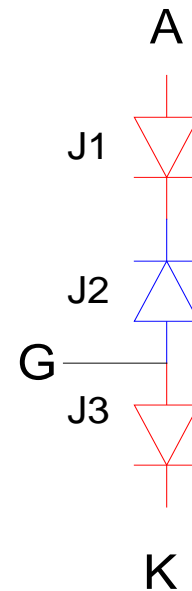

**Diode Equivalent Circuit**





# Two-Transistor Model of Thyristors

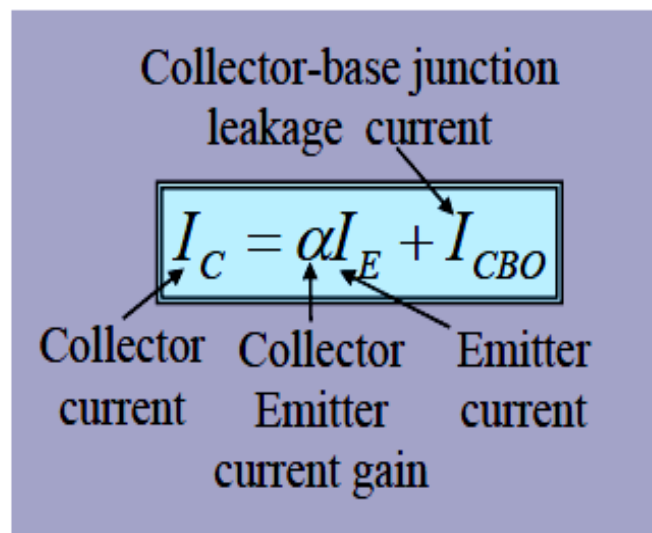

$$Q_1 \longrightarrow I_{C1} = \alpha_1 I_A + I_{CBO1}$$

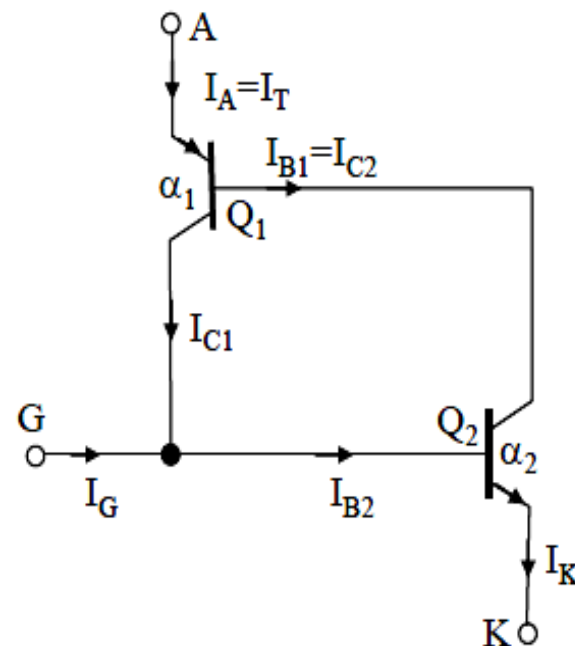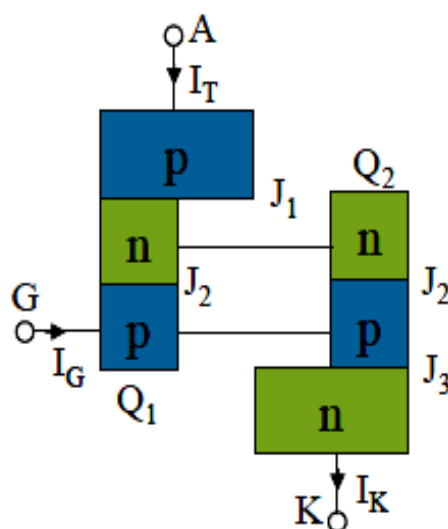
$$Q_2 \longrightarrow I_{C2} = \alpha_2 I_K + I_{CBO2}$$




$$I_A = I_{C1} + I_{C2} = \alpha_1 I_A + I_{CBO1} + \alpha_2 I_K + I_{CBO2}$$

$$I_K = I_A + I_G \quad \Rightarrow \quad I_A = \frac{\alpha_2 I_G + I_{CBO1} + I_{CBO2}}{1 - (\alpha_1 + \alpha_2)}$$

# Characteristics of Thyristors

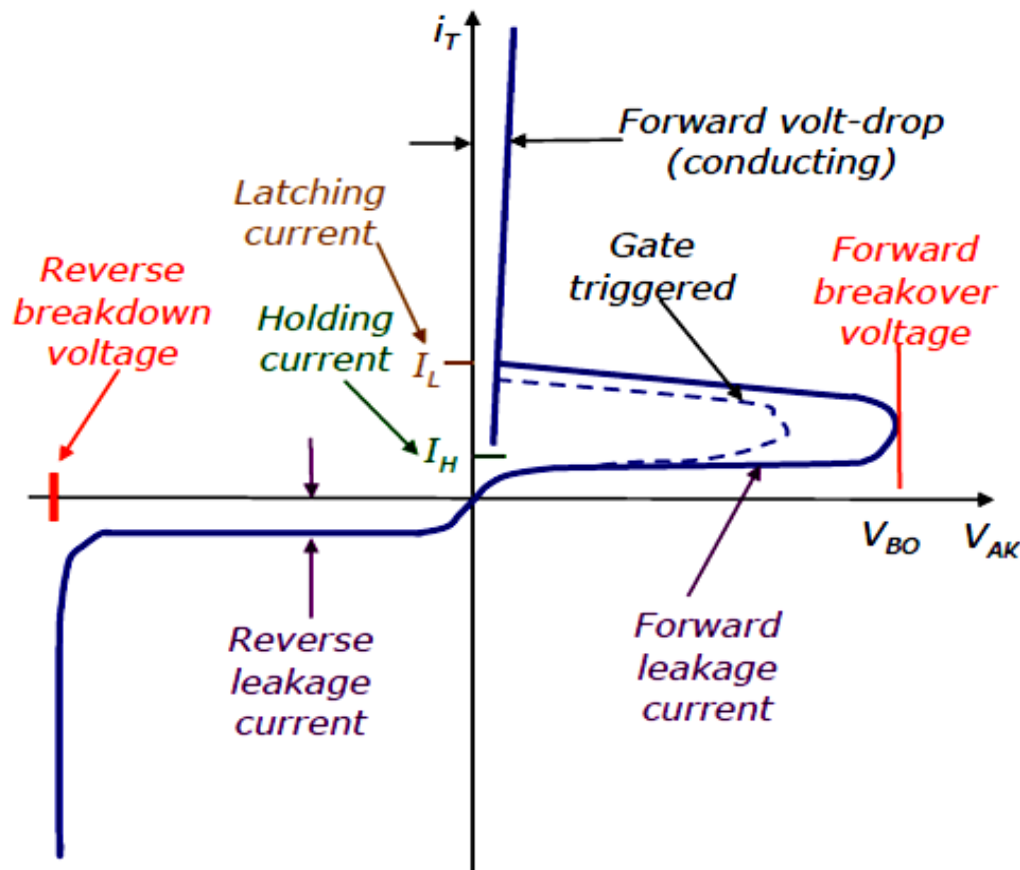

**V-I Characteristics**

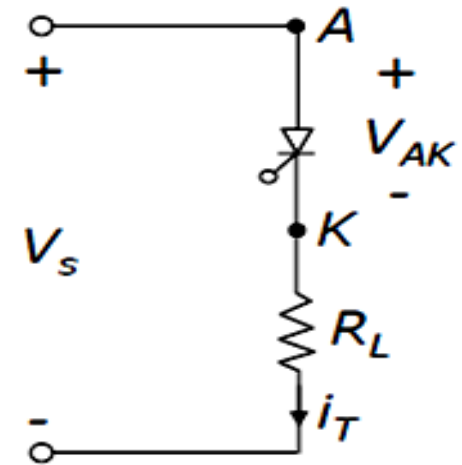

**Circuit**

## Turning ON Conditions:

$$\left\{ \begin{array}{l} V_{AK} > 0 \\ I_G > 0 \\ I_T > I_L \end{array} \right\} \quad \text{Thyristor turns ON and remains in this state even if } I_G \text{ is just one pulse.}$$

## Turning OFF Conditions:

$$\{ I_T < I_H \} \quad \text{Thyristor turns OFF and remains in this state if turning ON conditions are not satisfied}$$

# Thyristor Operating modes

**Thyristors have three modes of operation:**

## Forward blocking mode:

- Anode is positive w.r.t cathode, but the anode voltage is less than the break over voltage  $V_{BO}$ .
- Only leakage current flows, so the thyristor is not conducting.

## Forward conducting mode:

- When anode voltage becomes greater than  $V_{BO}$ , thyristor switches from forward blocking to forward conduction state, and a large forward current flows.
- If  $I_G = I_{G1}$ , thyristor can be turned ON even when the anode voltage is less than  $V_{BO}$ . The current must be more than the latching current  $I_L$ .
- Once the SCR is turned ON, it remains ON even after removal of gate signal, as long as the Holding Current ( $I_H$ ), is maintained.
- If the current reduced less than the holding current  $I_H$ , thyristor switches back to forward blocking state.

## Reverse blocking mode:

When cathode is more positive than anode, small reverse leakage current flows. However if cathode voltage is increased to reverse breakdown voltage, Avalanche breakdown occurs and large current flows.

# Thyristor Turn ON methods

- Thyristor turning **ON** is also known as **Triggering**.
  
- With **Anode** positive with respect to **Cathode**, a thyristor can be turned **ON** by any one of the following techniques :
  - **Forward Voltage Triggering**
  - **Gate Triggering**
  - *dv/dt* **Triggering**
  - **Temperature Triggering**
  - **Light Triggering**


# Thyristor Commutation

- **Commutation:** Process of turning **OFF** a conducting thyristor.
  - Current Commutation
  - Voltage Commutation
- **SCR** cannot be turned **OFF** via gate terminal.
- Thyristor will turn Off only after the anode current is negated either naturally or using forced commutation techniques.
- Methods of turning Off do not refer to the case when the anode current is gradually reduced below the Holding Current ( $I_H$ ) manually or through a slow process.
- **Commutation Classification:**
  - Natural commutation
  - Forced commutation
- **Natural Commutation of Thyristor takes place in:**
  - AC Voltage Regulators
  - Phase Controlled Rectifiers
  - Cycloconverters

# Turning The SCR Off:
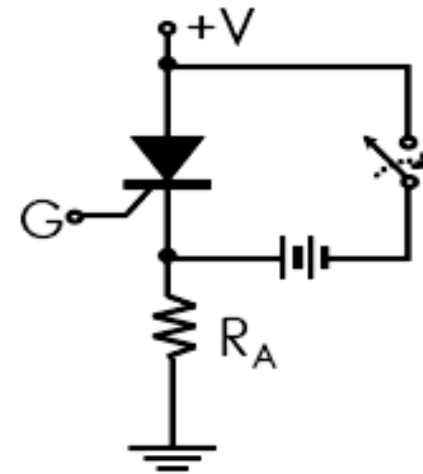
## Forced Commutation

- Forced commutation uses an external circuit to momentarily force current in the opposite direction to forward conduction.
- SCRs are commonly used in ac circuits, which forces the SCR out of conduction when the ac reverses.
- Applied to DC circuits.
- Applied to choppers and inverters.
- **Forced Commutation methods:**
  - ✓ Resonant Load
  - ✓ Self commutation
  - ✓ Auxiliary commutation
  - ✓ Capacitive commutation
  - ✓ External pulse commutation



**Forced Commutation**


# Thyristor Protection Circuits

- Reliable operation of a thyristor demands that its specified ratings are not exceeded.
- Various techniques are adopted for the protection of SCRs:
  - ☐ ***di/dt* protection**
  - ☐ ***dv/dt* protection**
  - ☐ **Over-Voltage protection**
  - ☐ **Over-Current protection**
  - ☐ **Thermal protection**
  - ☐ **Gate protection**

# ***di/dt* Protection**

- A thyristor requires a minimum time to spread the current conduction uniformly throughout the junctions.
- Otherwise, a localized “hot-spot” heating may occur due to high current density.


$$\frac{di}{dt} = \frac{V_s}{L_s}$$

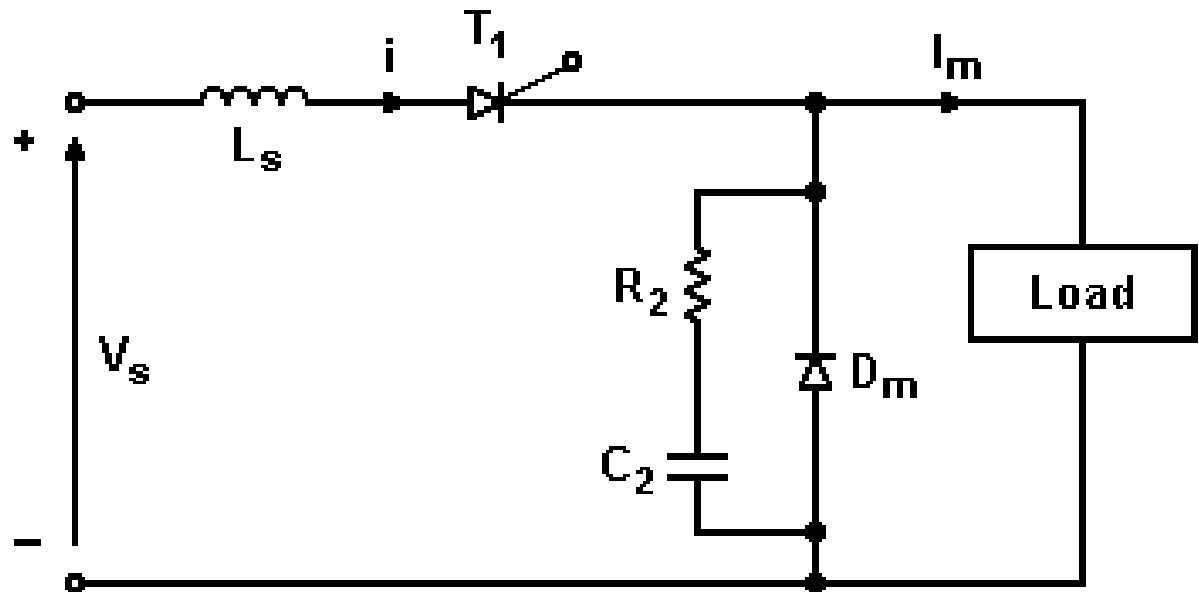



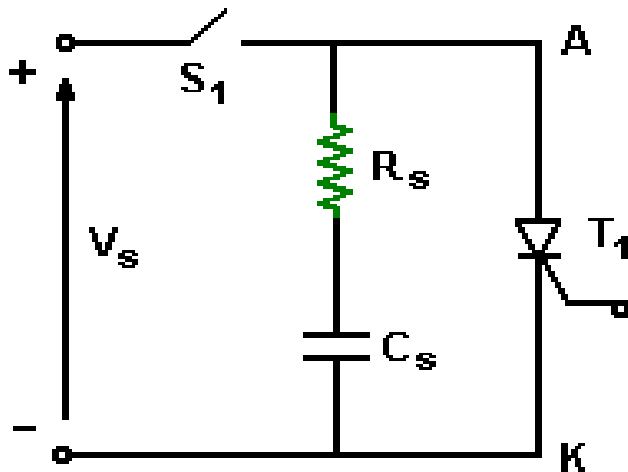
# ***dv/dt Protection (Snubber Circuit)***

- A snubber circuit consists of a series combination of resistance  $R_s$  and capacitance  $C_s$  in parallel with the thyristor.
- A capacitor  $C_s$  in parallel with the device is sufficient to prevent unwanted  $dv/dt$  triggering of the SCR.
- Typical values of  $dv/dt$  are 20 – 500 V/ $\mu$ sec



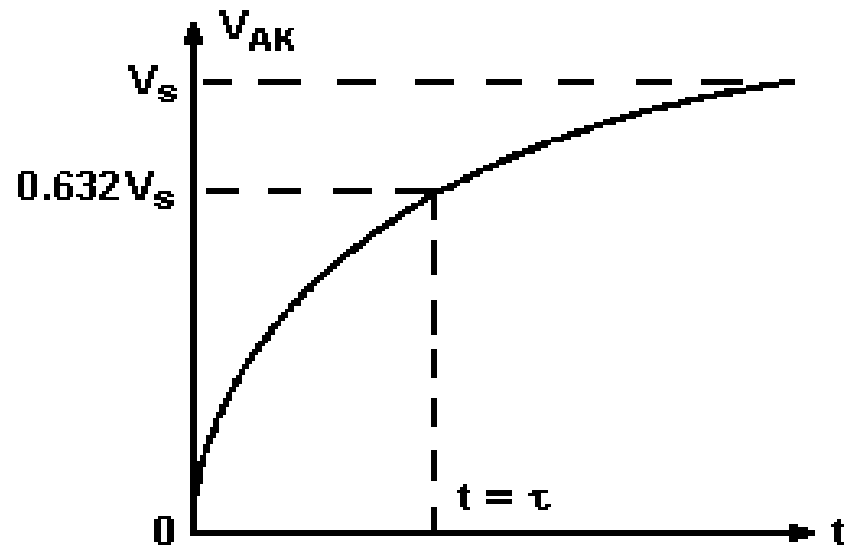
$$\frac{dv}{dt} = \frac{0.632 V_s}{R_s C_s}$$



$$V_c = V_s \left( 1 - e^{-t / R_s C_s} \right)$$

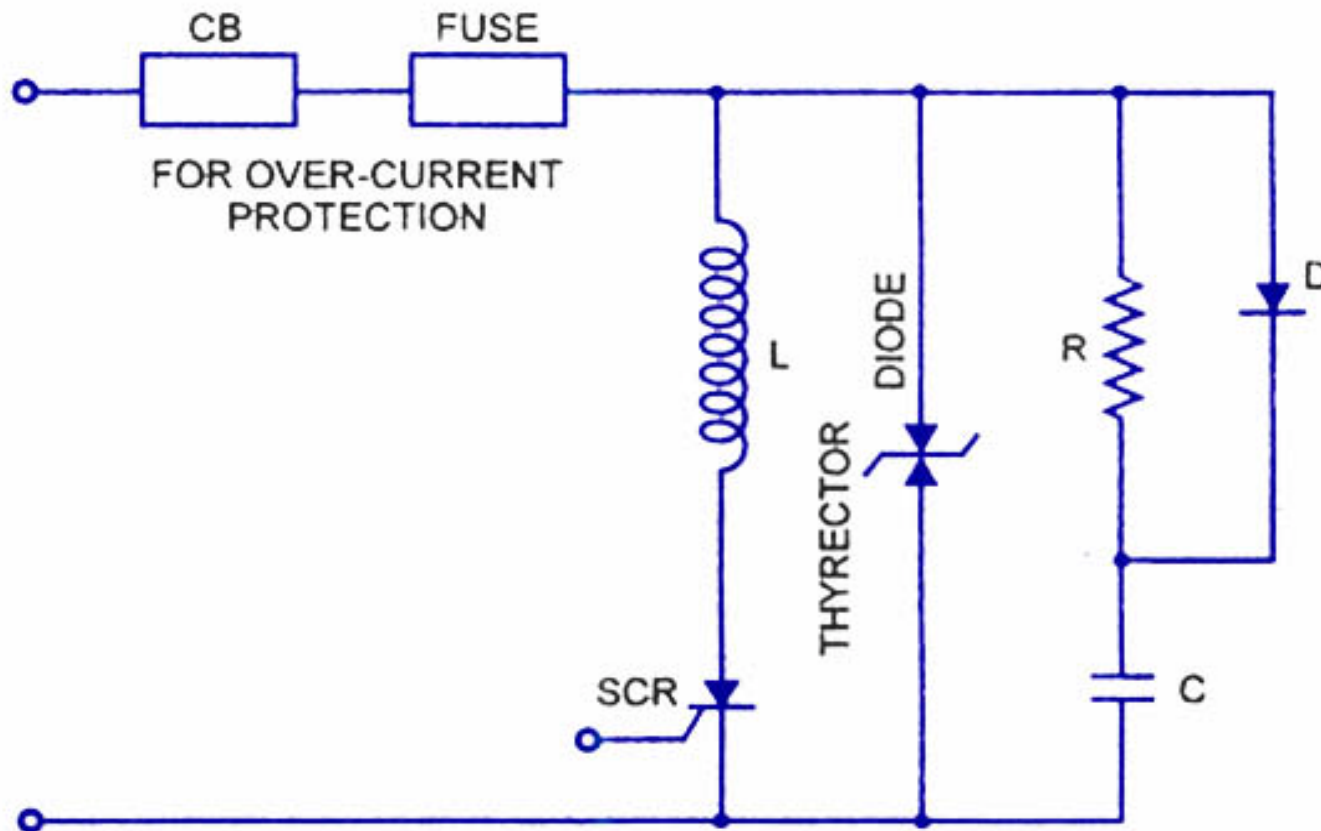
# Over-Voltage Protection

High forward voltage protection is inherent in SCRs. The SCR will breakdown and start conducting before the peak forward voltage is attained so that high voltage is transferred to the load.


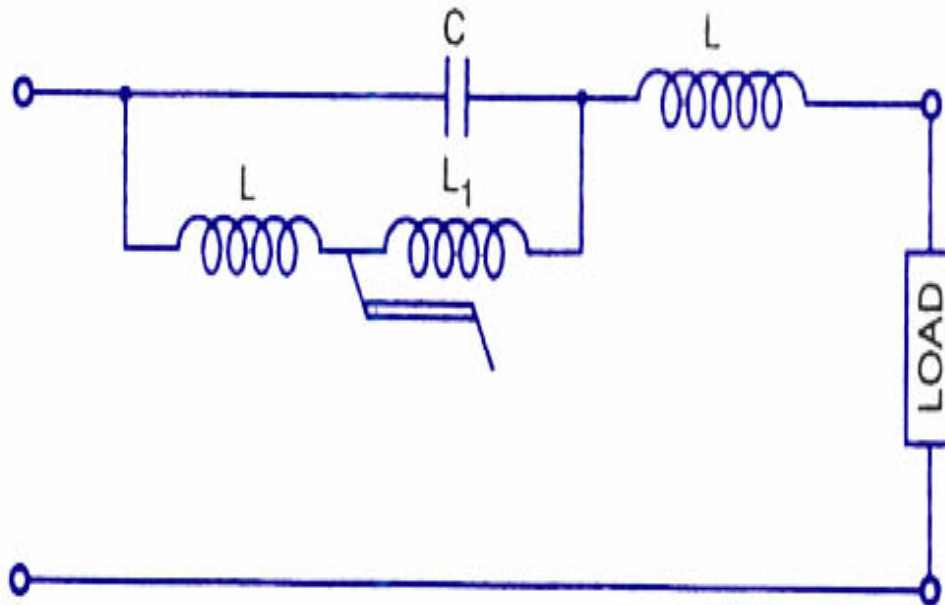
# Over-Current Protection

- If the output to the load is alternating current, LC resonance provides over-current protection as well as filtering.
- A current limiting device employing a saturable reactor  $L_1$ .
- With normal currents,  $L_1$  offers high impedance and  $C$  and  $L$  are in series to provide zero impedance to the flow of current of fundamental harmonic.
- An over-current saturates  $L_1$  and so gives negligible impedance. There is LC parallel resonance and hence infinite impedance to the flow of current at the resonant frequency.



# Temperature protection

➤ For **10cm** square plate of copper or aluminium with length side **L** (in meter) to air, heat sink is estimated from the following equation:

$$R_{sa} = 0.5 / L$$


➤ Thermal power loss: 
$$P = \frac{T_{j \max} - T_a}{R_{ja}}$$

➤  $R_{sa}$  = thermal sink to air resistance,

➤  $R_{ja}$  = total junction to air resistance.



➤ The transient thermal impedance  $Z_{js}$  decreases in value as the temperature rises and result in high power dissipation.
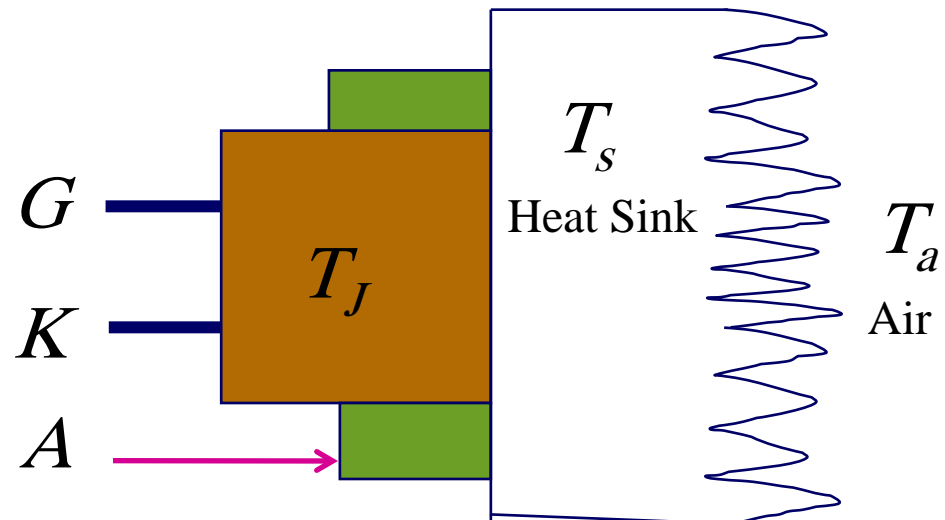
$$Z_{js} = \frac{\text{Temperature Rise}}{\text{Power Loss}}$$




# Gate protection circuits

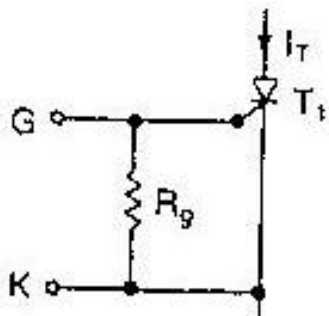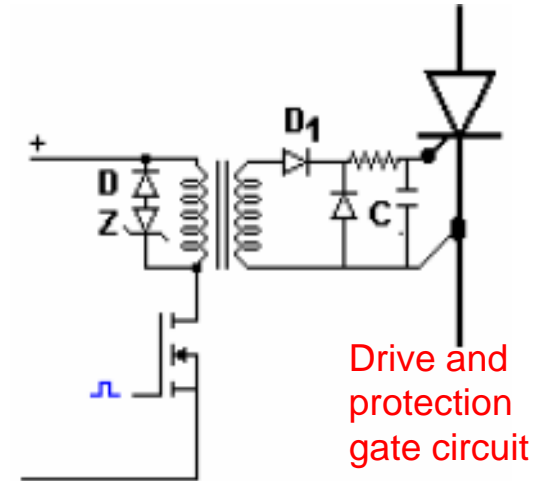
- (a) 1-Increase  $dv/dt$  capability, 2-keep gate clamped , 3-lower  $t_g$  time, and 4-noise immunity
- (b) 1- Increase  $dv/dt$  capability, 2 remove high frequency noise.
- (c)  $D_g$  Provide fixed negative bias, 2-protect gate and gate supply from reverse transient , and 3- lower toff.
- (d)  $D_1$  provide positive triggering.




(a)

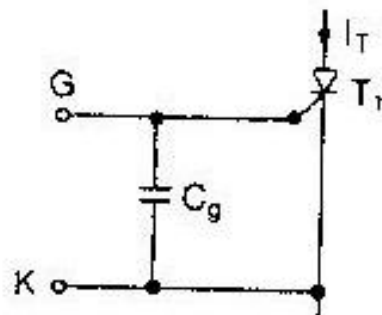

(b)

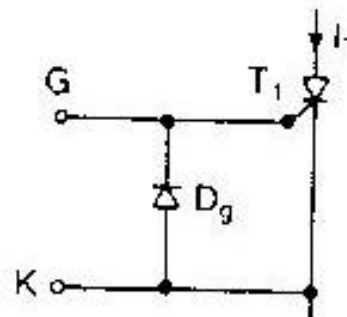


(c)

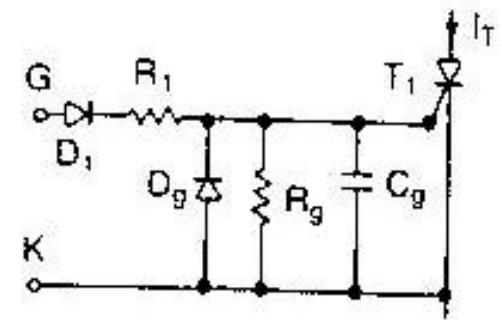

(d)

# Complete protection circuit

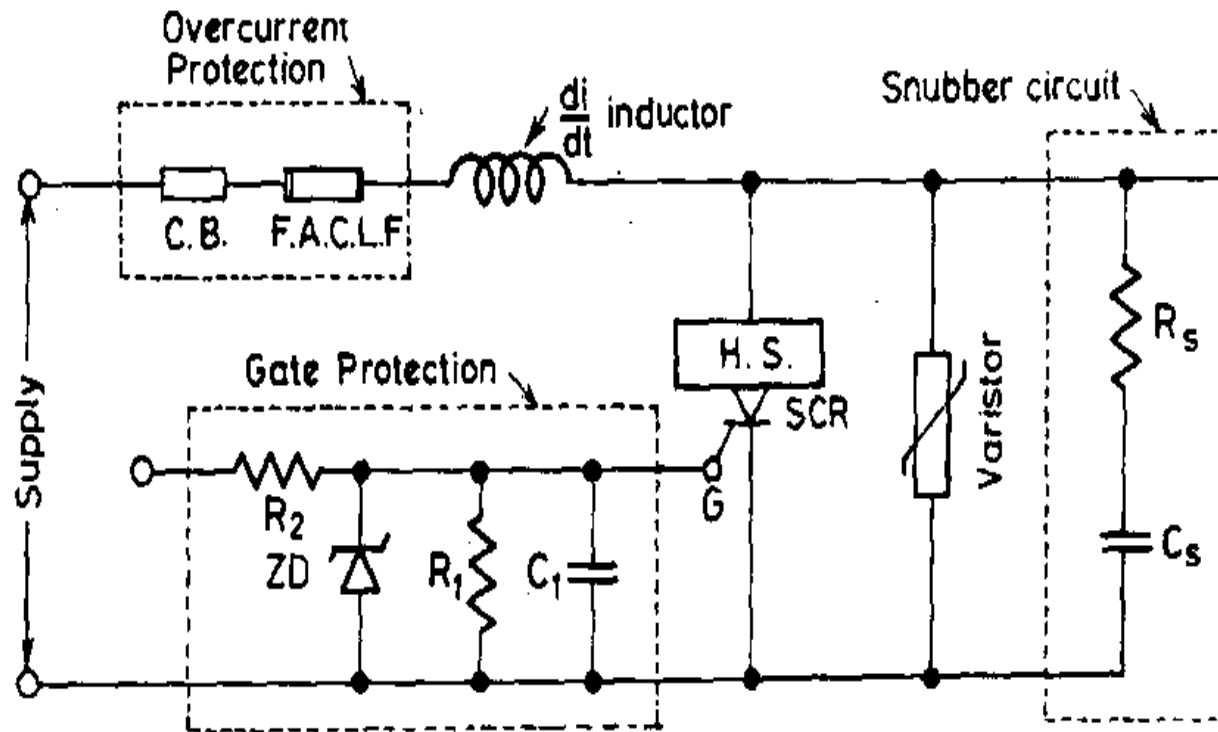


C.B.—Circuit breaker ; F.A.C.L.F.—Fast acting current limiting fuse ; H.S.—Heat sink ; ZD—Zener diode.

## Example 1

An SCR with 1V voltage drop across the anode–cathode terminals is connected to 12V source and 50 mA Lamp. Determine the power in:

- a) the lamp
- b) the SCR

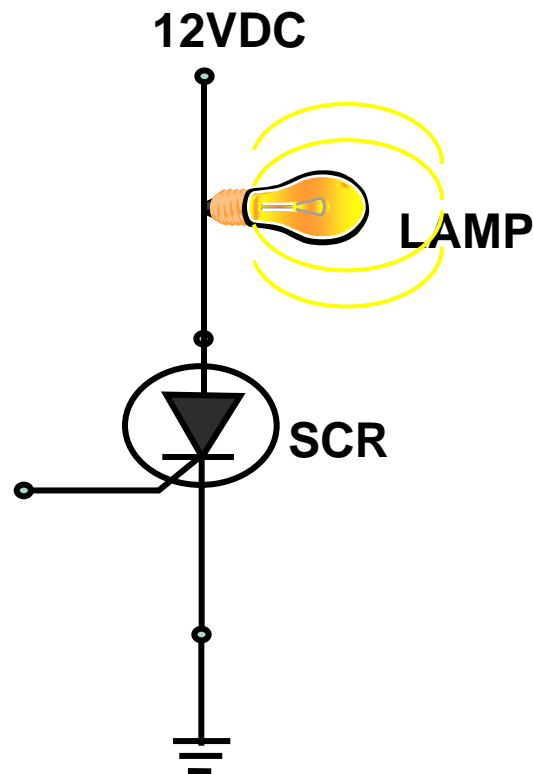

$$P = I \times E$$

$$P_{\text{LAMP}} = I_{\text{LAMP}} \times E_{\text{LAMP}}$$

$$P_{\text{LAMP}} = 50 \text{ mA} \times 11\text{V}$$

$$P_{\text{LAMP}} = 550 \text{ mW}$$

$$P_{\text{SCR}} = I_{\text{SCR}} \times E_{\text{SCR}}$$

$$P_{\text{SCR}} = 50\text{mA} \times 1\text{V}$$

$$P_{\text{SCR}} = 50 \text{ mW}$$

# Gate Triggering Circuits

- It represents efficient and reliable methods for turning ON the SCR with different types as:

- ☐ **DC-Triggering circuits**


- ☐ **AC-Triggering circuits**

- R-Triggering circuit
  - RC-Triggering circuit
  - LC-Triggering circuit


- ☐ **Pulse-Triggering circuits [UJT or BJT circuits]**



## DC-Triggering Circuits

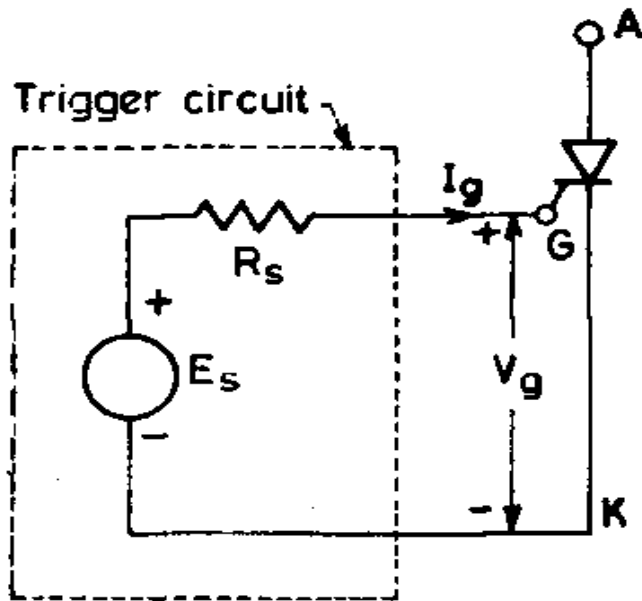

(a)

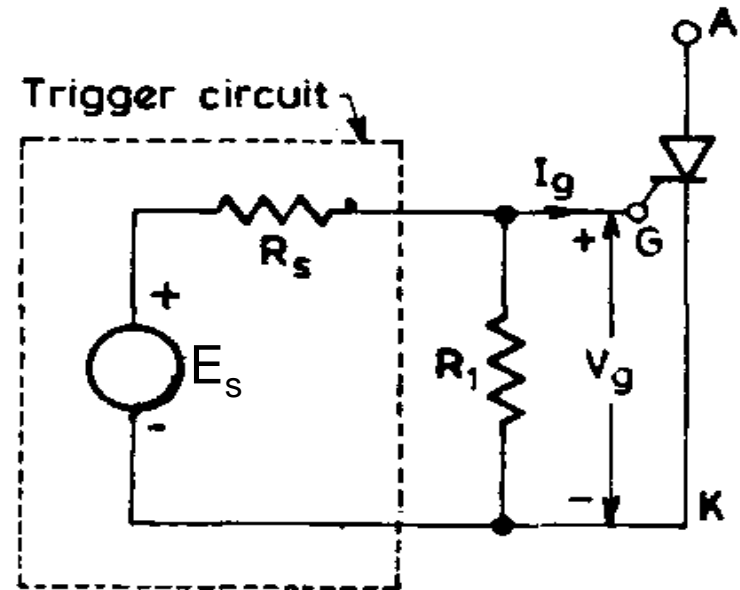

(b)

$$E_s = V_g + I_g R_s$$

$$E_s = V_g + \left( I_g + \frac{V_g}{R_1} \right) R_s$$

## Example 2

Design a suitable gate triggering circuit for an SCR with 800V, 110A, connected with 6V DC power supply of maximum permissible current  $I_{dc-MAX} = 0.2A$  and short circuit current  $I_{S/C} = 0.5A$ . The SCR has the following gate parameters:-  
 $V_G = 2.5V$  ,  $I_G = 50mA$  ,  $V_{GM} = 3V$  ,  $I_{GM} = 0.1A$  ,  $P_{GM} = 0.5W$

### Solution:

1) For a Gate drive circuit without  $R_g$  , we have

$$R_s = \frac{E_s}{I_{S/C}} = \frac{6}{0.5} = 12\Omega$$

To protect the source from excessive current, the minimum value of  $R_1$  in series with  $R_s$  is:

$$R_s + R_1 \geq \frac{E_s}{I_{dc-MAX}} = \frac{6}{0.2} = 30\Omega \quad \Rightarrow \quad \therefore R_1 \geq 30 - 12 = 18\Omega$$

Also, to protect the gate-cathode junction of the SCR, the minimum value of  $R_1$  in series with  $R_s$  is given by:

$$R_s + R_1 \geq \frac{E_s}{I_{GM}} = \frac{6}{0.1} = 60\Omega \quad \Rightarrow \quad \therefore R_1 \geq 60 - 12 = 48\Omega$$

Therefore,  $R_1$  should be greater than  $48\Omega$

## *Solution: (cont.)*


Now, corresponding to the typical values of  $V_G = 2.5V$  and  $I_G = 50mA$ , the maximum value of  $R_1$  in series with  $R_s$  is given by:

$$R_s + R_1 \leq \frac{E_s - V_G}{I_G} = \frac{6 - 2.5}{0.05} = 70\Omega \quad \Rightarrow \quad \therefore R_1 \leq 70 - 12 = 58\Omega$$

Therefore,  $48\Omega \geq R_1 \geq 58\Omega$ , and we will choose  $R_1 = 56\Omega$



The value of  $R_g$  is given by the voltage divider as:
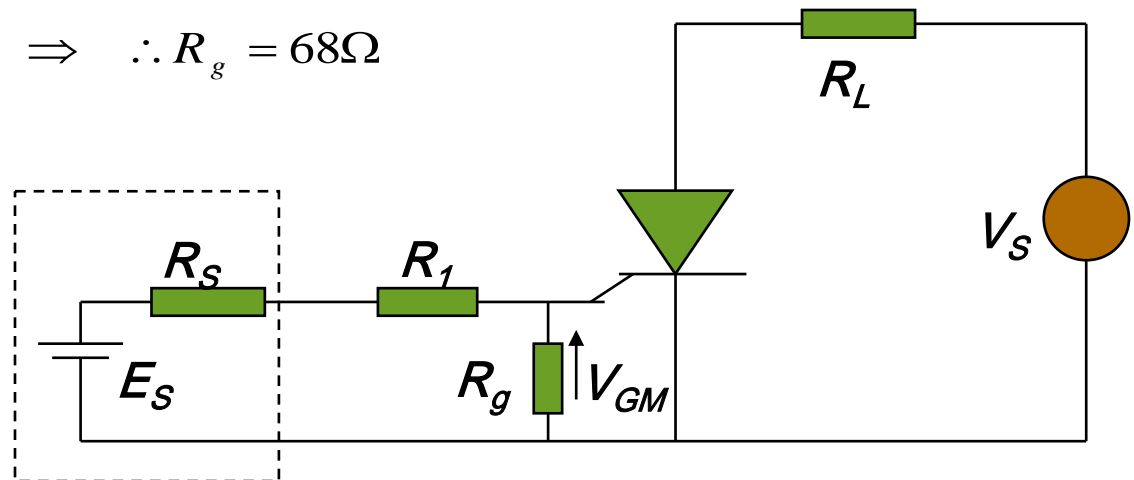
$$E_s \times \frac{R_g}{R_g + R_s + R_1} \leq V_{GM} \quad \Rightarrow \quad \therefore R_g = 68\Omega$$



**The complete design of DC trigger circuit**

# UJT-Trigger Circuit

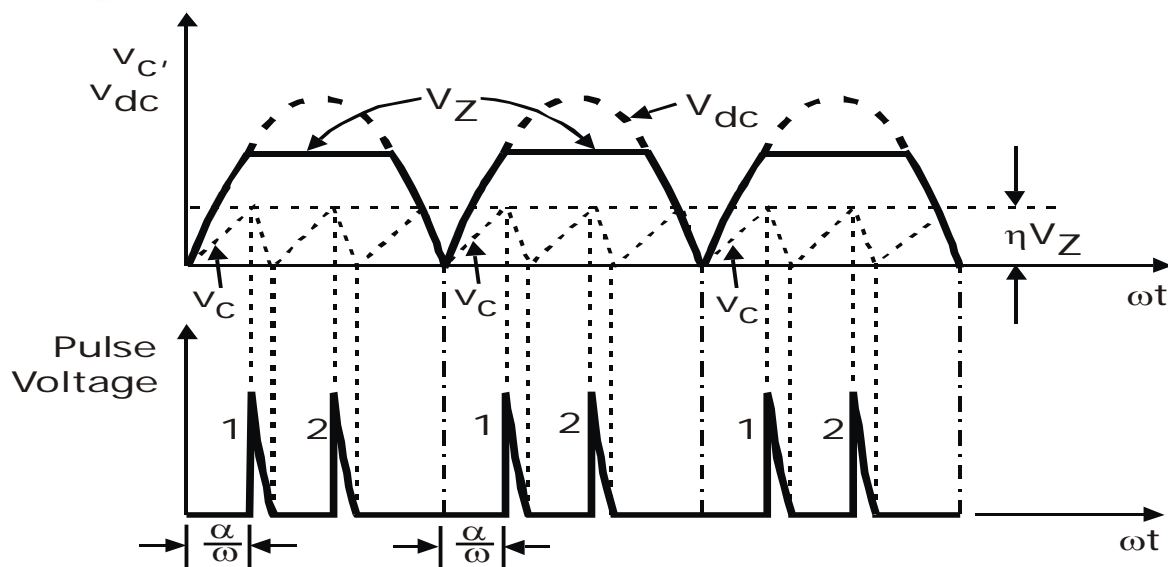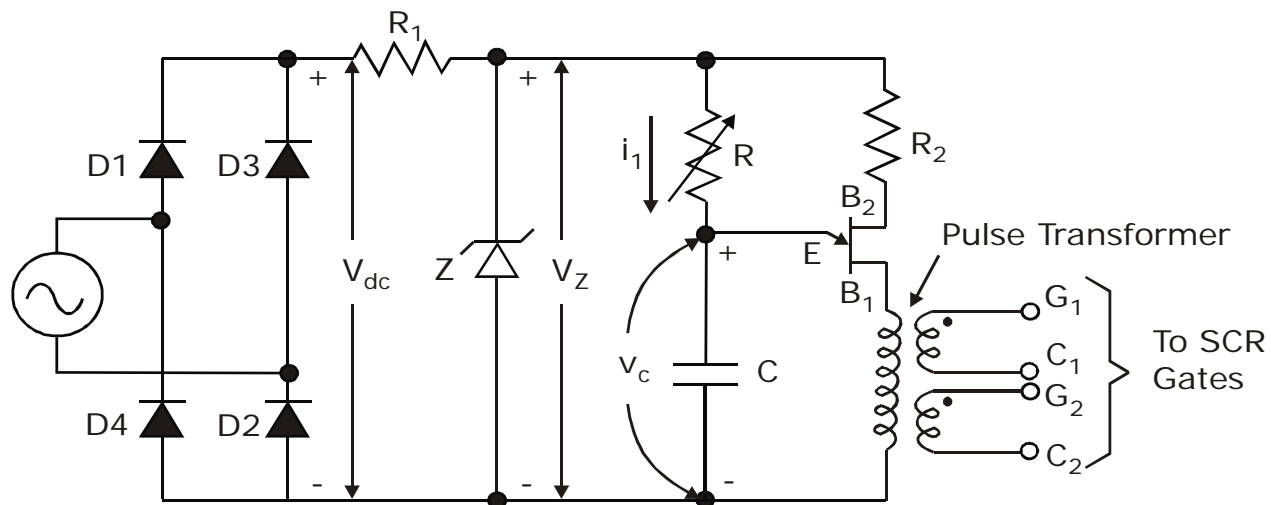

Firing angle:


$$\alpha = \omega T = 2\pi f$$

$$T = R_E C \ln \left( \frac{1}{1 - \eta} \right)$$


Voltage waveforms of UJT trigger circuit
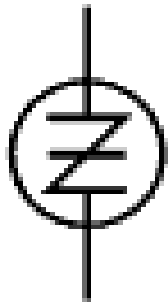
# ***Thyristor Family Members***


- **SCR:** Silicon Controlled Rectifier
- **DIAC:** Diode on Alternating Current
- **TRIAC :** Triode for Alternating Current
- **SCS:** Silicon Control Switch
- **SUS:** Silicon Unilateral Switch (*Shockley Diode*)
- **SBS:** Silicon Bidirectional Switch
- **SIS:** Silicon Induction Switch
- **LASCS:** Light Activated Silicon Control Switch
- **LASCR:** Light Activated Silicon Control Rectifier or LTT
- **SiTh :** Static Induction Thyristor
- **RCT:** Reverse Conducting Thyristor
- **GTO :** Gate Turn-Off Thyristor
- **MCT:** MOSFET Controlled Thyristor
- **ETOs:** Emitter Turn ON Thyristor
- **IGCT:** Integrated Gate-Commutated Thyristor
- **SIDAC:** Silicon Diode for Alternating Current
- **QUADRACS:** DIAC+TRIAC in single package where the DIAC is a triggering device for the TRIAC




SIDAC

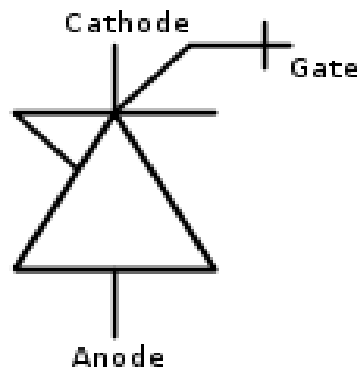


IGCT

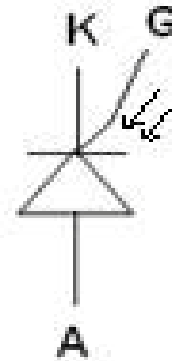



LASCR

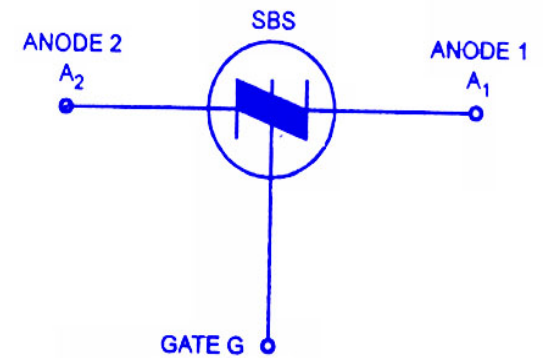

SBS

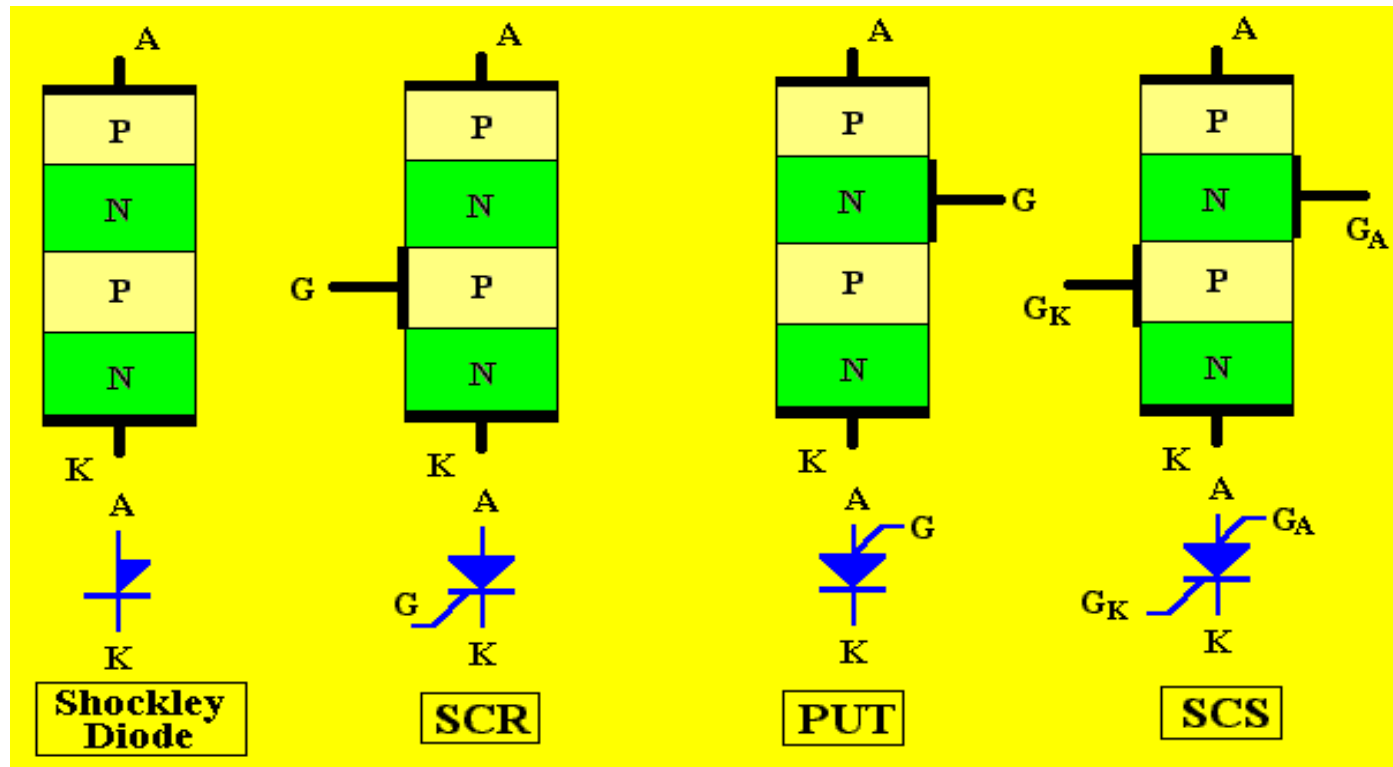


# DIAC Thyristor

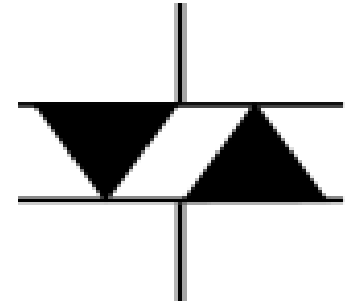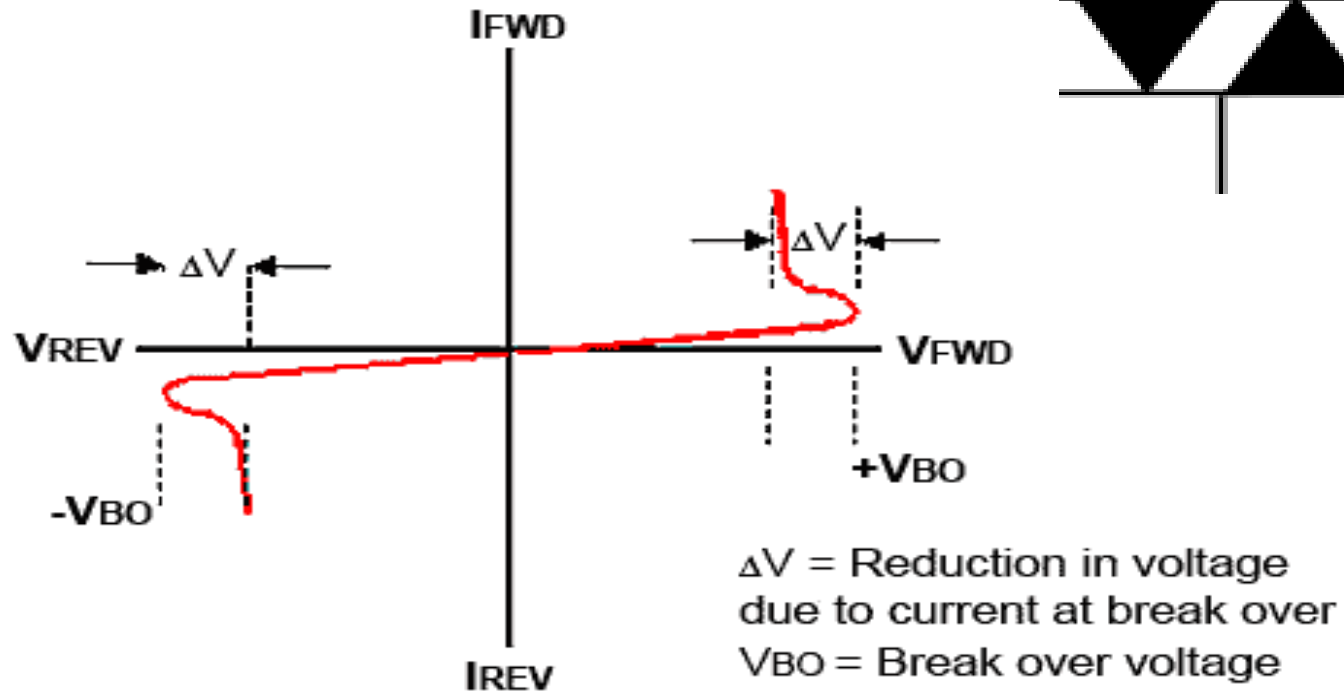



DIAC Characteristics
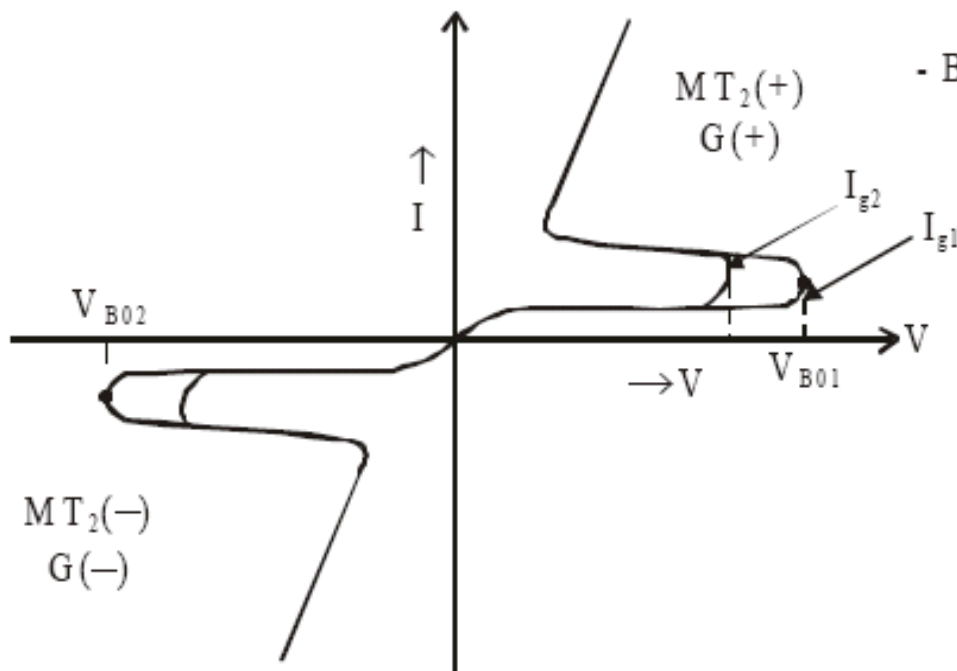
# ***Bidirectional Triode Thyristors (TRIAC)***



TRIAC Characteristics

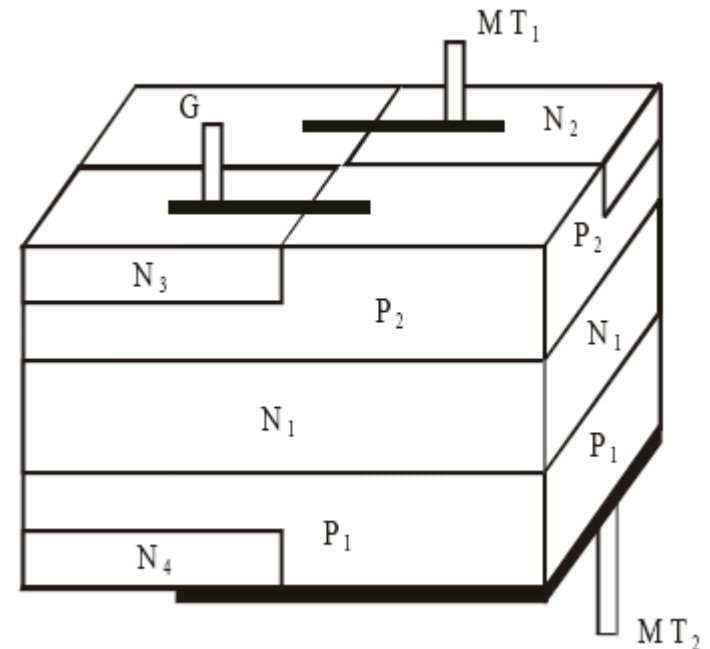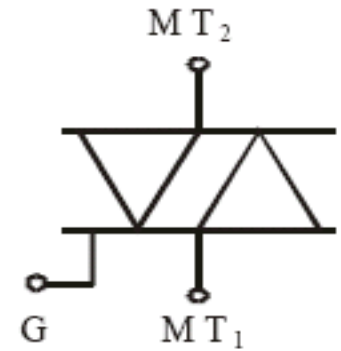$V_{B01}, V_{B02}$   
- Breakover voltages  
 $I_{g2} > I_{g1}$






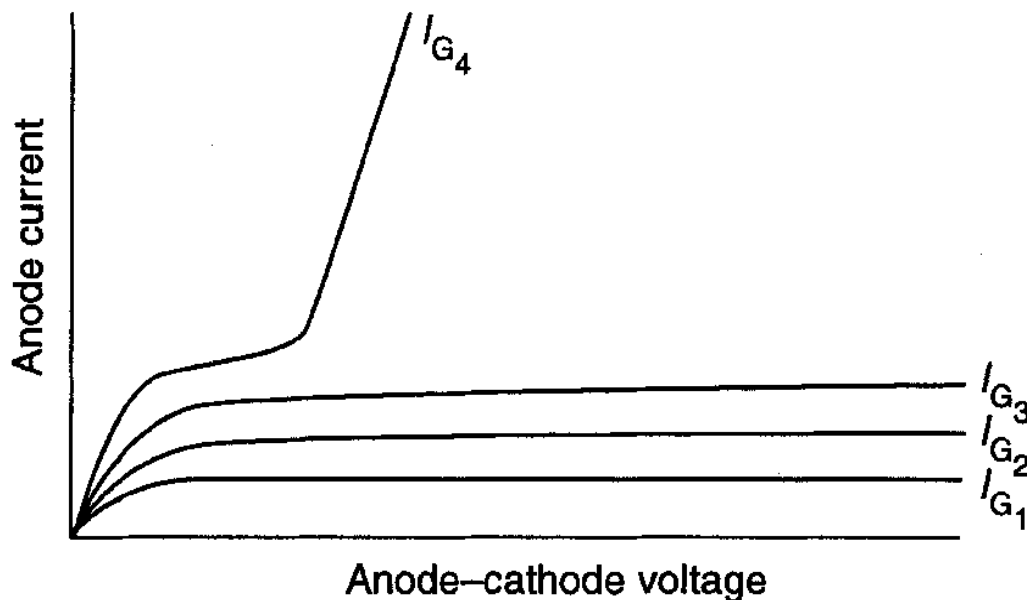
# GTO Thyristor

can be turned-on by a gate signal, and can also be turned-off by a gate signal of negative polarity

The main applications of GTO are in variable speed motor drives, high power, inverters and traction



GTO Characteristics

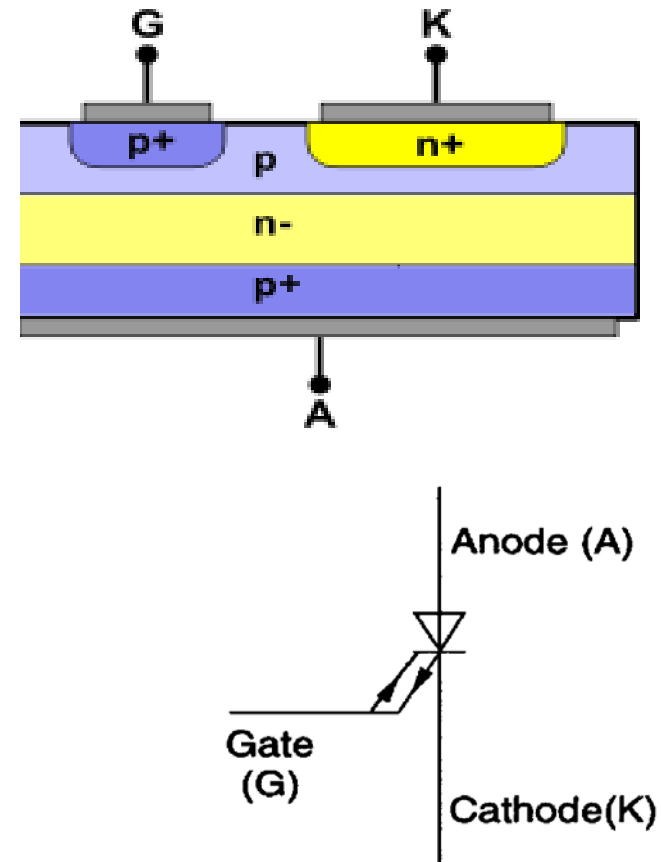

# Problems and Solutions

**Question 1** What are the different operation regions of the SCR?

**Solution:**

SCR will have three regions of operations based on the mode in which the device is connected as:

**Reverse blocking region:** When the cathode of is made positive with respect to the anode and no gate signal is applied. In this region, SCR exhibits reverse blocking characteristics similar to the diode.

**Forward blocking region:** the anode is made positive with respect to the cathode and no gate signal is applied to the thyristor. A small leakage current flow in this mode of operation.

**Forward conduction region:** when the forward voltage applied between the anode and cathode increases at particular break over voltage, avalanche breakdown takes place and thyristor starts conducting current in forward direction. By this type of triggering the device may damages the SCR. Hence a gate signal is applied before the forward break over voltage to trigger the SCR.

---

**Question 2** What is the Latching current ( $I_L$ ) ?

**Solution:**

It is the minimum anode current to keep the thyristor in conducting state after the gate pulse is removed.

---

**Question 3** What is the Holding current ( $I_H$ ) ?

**Solution:**

It is the minimum anode current at which the thyristor continue to conduct. If the anode current becomes less than  $I_H$ , the thyristor will be turned off.

**Question 4** What is the relation between the gate signal and forward break over voltage ( $V_{BO}$ )?

**Solution:**

Thyristor can be triggered by increasing the forward voltage between the anode and cathode. At forward break over voltage, it starts conducting. However this process may damage the thyristor. So it is usually triggered on through a gate pulse before reaching the break over voltage. Forward voltage at which the thyristor triggered on depends on the magnitude of gate current. Higher is the gate current lower is the forward break over voltage.

**Question 5** What are the different losses that occur in thyristor while operating?

**Solution:**

- Forward conduction losses during conduction of the thyristor.
- Loss due to leakage current during forward and reverse blocking.
- Power loss at gate or Gate triggering loss.
- Switching losses at turn-on and turn-off..

**Question 6** What are the different turns ON methods of the SCR?

**Solution:**

- Forward voltage triggering.
- Gate triggering.
- $dv/dt$  triggering.
- Temperature triggering.
- Light triggering

**Question 7** What is the thyristor commutation?

**Solution:**

It is the process to **turn-off** the thyristor by changing the direction of current flow.

**Question 8** What is the snubber circuit?


**Solution:**

It is a series combination of resistor and capacitor and used for  $dv/dt$  protection of the SCR.

**Question 9** Define the SCR or thyristor and draw its symbol.

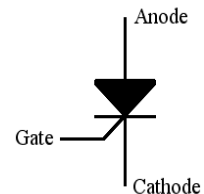
**Solution:**

SCR stands for Silicon Controlled Rectifier. It is a four layer (p-n-p-n) semiconductor and three terminals (anode, cathode, and gate) device.



**Question 10** Label the terminals on a TRIAC with their proper designations:

**Solution:**

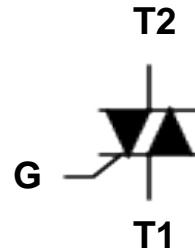

---

**Question 11** Identify at least three different types of thyristors (besides SCRs)

**Solution:**

- **RCT**: Reverse Conducting Thyristor
- **GTO**: Gate Turn-Off Thyristor
- **MCT**: MOSFET Controlled Thyristors

---

**Question 12** Outline the successful gate trigger conditions for an SCR.

**Solution:**

- 1-  $V_G$  and  $I_G$  should be within the trigger zone.
- 2- The gate pulse should be timed properly (synchronization).
- 3- Minimum gate power dissipation.

### Question 13

#### Choose the correct answer for the following Questions


- 1) The SCR is considered to be a semi-controlled device because.....
- A. It can be turned OFF but not ON with a gate pulse.
  - B. It conducts only during one half-cycle of an alternating current wave
  - ☒ C. It can be turned ON but not OFF with a gate pulse.
  - D. It can be turned ON only during one half-cycle of an alternating voltage wave.
- 

- 2) The Silicon Controlled Switch (SCS) is similar in construction to the.....
- A. Triac.
  - B. Diac.
  - ☒ C. SCR.
  - D. Four-Layer Diode
- 

- 3) The SCR can be triggered ON by a pulse at the.....
- A. Anode.
  - B. Cathode.
  - ☒ C. Gate.
  - D. None of the above.
- 

- 4) How many semiconductor layers are thyristors constructed with?
- A. 2
  - B. 3
  - ☒ C. 4
  - D. 5

5) Which symbol represents the SCS?

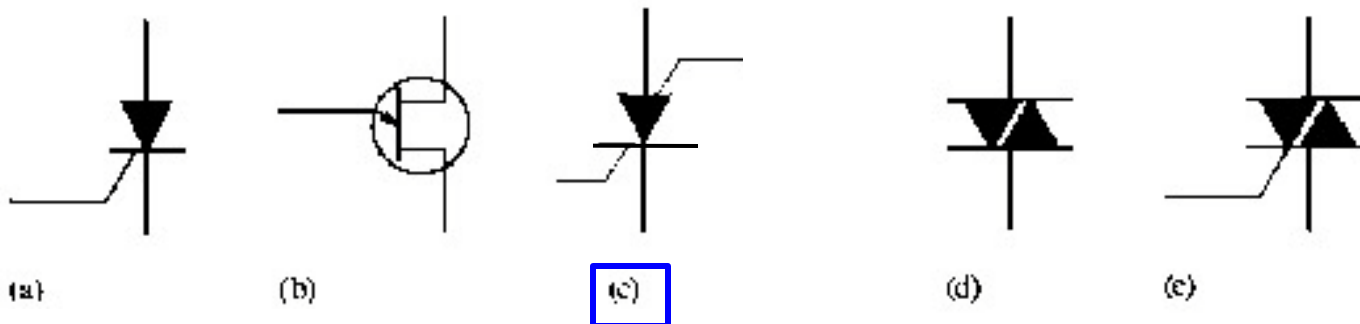

6) Holding current of the thyristor is.....

- ☒ A. Less than latching current      B. More than latching current  
C. Equal to latching current      D. Zero

7) For an SCR,  $dv/dt$  protection is achieved through the use of.....

- A. RL in series with SCR      ☒ B. RC across SCR  
C. L in series with SCR      D. RC in series with SCR

8) The procedure of switching off an SCR is called:.....

- A. Forcing      ☒ B. Commutation      C. Triggering      D. Latching

9) Anode current in an thyristor is made up of.....  
A. electrons only      B. electrons or holes      ☒ C. electrons and holes      D. holes only

---

10) An SCR can only be turned off via it's.....  
A. cathode      ☒ B. anode      C. gate      D. none of the above

---

11) In a thyristor,  $di/dt$  protection is achieved by the use of  
☒ (A) An inductance  $L$  in series with the thyristor  
(B) A resistor in series with the thyristor  
(C)  $RC$  in series with the thyristor  
(D)  $RL$  in series with the thyristor

### Question 14    Fill in the blanks with the appropriate word(s)

- i. Forward break over voltage of a thyristor decreases with increase in the..... current.
- ii. Reverse..... voltage of a thyristor is .....of the gate current.
- iii. Reverse saturation current of a thyristor ..... with gate current.
- iv. In the pulsed gate current triggering of a thyristor ,the gate current pulse width should be larger than the..... time of the device.
- v. To prevent unwanted turn ON of a thyristor, all spurious noise signals between the gate and the cathode must be less than the gate .....voltage.

**Answers:** (i) gate; (ii) break down, independent; (iii) increases; (iv) Turn ON; (v) non- trigger.

---

### Question 15    Fill in the blanks with the appropriate word(s)

- i. A thyristor is turned on by applying a.....gate current pulse when it is.....biased.
- ii. Total turn on time of a thyristor can be divided into..... time.....time, and..... time.
- iii. During rise time the rate of rise of anode current should be limited to avoid creating local.....
- iv. A thyristor can be turned off by bringing its anode current below.....current and applying a reverse voltage across the device for duration larger than the..... time of the device.
- v. Reverse recovery charge of a thyristor depends on the.....of the forward current just before turn off and its.....
- vi. Inverter grade thyristors have.....turn off time compared to a converter grade thyristor.

**Answers:** (i) positive, forward; (ii) delay, rise, spread; (iii) hot spots (iv) holding, turn off; (v) magnitude, rate of decrease (vi) faster



## Question 16      Fill in the blanks with the appropriate word(s)

- i. Peak non-repetitive over voltage may appear across a thyristor due to..... or ..... surges in a supply network.
- ii. VRSM rating of a thyristor is greater than the..... rating but less than the..... rating.
- iii. Maximum average current a thyristors can carry depends on the.....of the thyristor and the..... of the current wave form.
- iv. The ISM rating of a thyristor applies to current waveforms of duration .....than half cycle of the power frequency where as the  $\int i^2 dt$  rating applies to current durations.....than half cycle of the power frequency.
- v. The gate non-trigger voltage specification of a thyristor is useful for avoiding unwanted turn on of the thyristor due to.....voltage signals at the gate.

**Answers:** (i) switching, lightning; (ii) VRRM, VBRR;                      (iii) case temperature, conduction angle;  
(iv) greater, less; (v) noise

## Question 17      Fill in the blanks with the appropriate word(s)

- i. A Triac is a.....minority carrier device.
- ii. A Triac behaves like two.....connected thyristors.
- iii. The gate sensitivity of a triac is maximum when the gate is.....with respect to MT1 while MT2 is positive with respect to MT1 or the gate is.....with respect to MT1 while MT2 is negative with respect to MT1 .
- iv. A Triac operates either in the.....or the..... quadrant of the I-V characteristics.
- v. In the.....quadrant, the triac is fired with..... gate current while in the..... quadrant the gate current should be.....
- vi. The maximum possible voltage and current rating of a Triac is considerably..... compared to thyristor due to.....of the two current carrying paths inside the structure of the triac.
- vii. To avoid unwanted turn on of a triac due to large  $dv/dt$ ..... are used across triacs.
- viii. For “clean turn ON” of a triac, the.....of the gate current pulse should be as..... as possible.

**Answers:** (i) bidirectional; (ii) anti parallel; (iii) positive, negative; (iv) first, third; (v) first, positive, third, negative (vi) lower, interaction; (vii) R-C snubbers; (viii) rise time, small.

**Question 18**     **Fill in the blanks with the appropriate word(s)**

- i. A thyristor is a \_\_\_\_\_ carrier semi controlled device.
- ii. A thyristor can conduct current in \_\_\_\_\_ direction and block voltage in \_\_\_\_\_ direction.
- iii. A thyristor can be turned ON by applying a forward voltage greater than forward \_\_\_\_\_ voltage or by injecting a positive \_\_\_\_\_ current pulse under forward bias condition.
- iv. To turn OFF a thyristor the anode current must be brought below \_\_\_\_\_ current and a reverse voltage must be applied for a time larger than \_\_\_\_\_ time of the device.
- v. A thyristor may turn ON due to large forward \_\_\_\_\_.

Answers: (i) minority; (ii) one, both; (iii) break over, gate; (iv) holding, turn off;


(v)  $dv/dt$

## Question 19

Calculate the protective resistance ( $R$ ) shown in the given circuit for voltage gate  $V_G = 3\text{V}$  and current gate  $I_G = 150\text{ mA}$ , where the supply voltage  $V = 12\text{V}$ .

Solution:
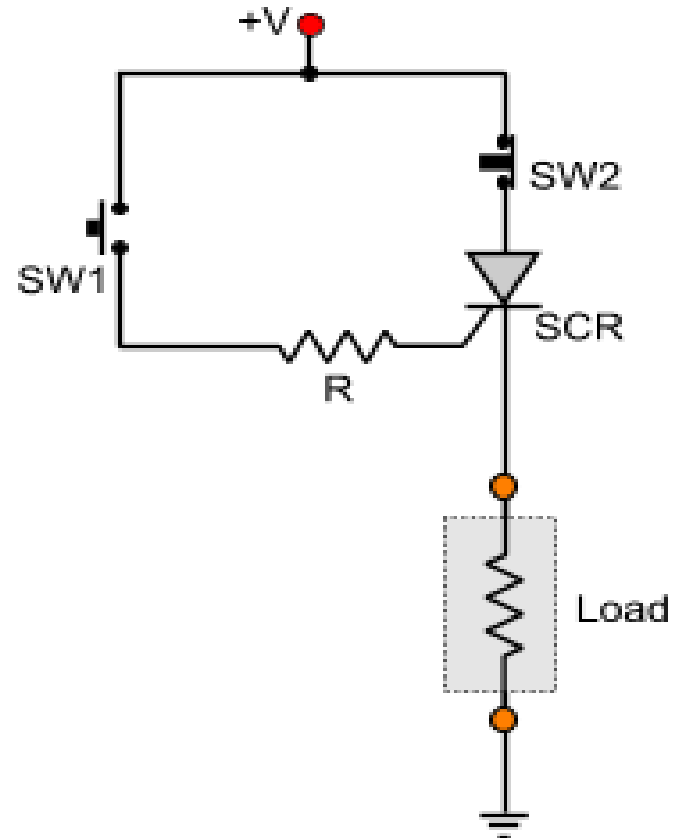
$$R = \frac{V - V_G}{I_G} = \frac{12 - 3}{0.15} = 60\Omega$$



### Question 20

UJT relaxation oscillator is used to trigger single SCR in AC circuit [220V, 50Hz] , for  $\alpha = 90^\circ$  and  $\eta = 0.6$ ,  $R_E = 1k\Omega$  , find the value of  $C$ .

Solution:

$$\alpha = 90^\circ = \frac{\pi}{2} = \omega T \Rightarrow T = \frac{\alpha}{\omega} = \frac{\pi/2}{2\pi f_i} = \frac{1}{4f_i} = \frac{1}{200} = 5m \text{ sec}$$



$$C = \frac{T}{R \ln\left(\frac{1}{1-\eta}\right)} \Rightarrow C = \frac{5 \times 10^{-3}}{1 \times 10^3 \ln\left(\frac{1}{1-0.6}\right)} = 1.09 \mu F$$

### Question 21

The circuit shown below, if  $V_s = 600V$  and  $[dv/dt]_{\max} = 100 V/\mu s$  , determine the snubber time constant .

Solution:
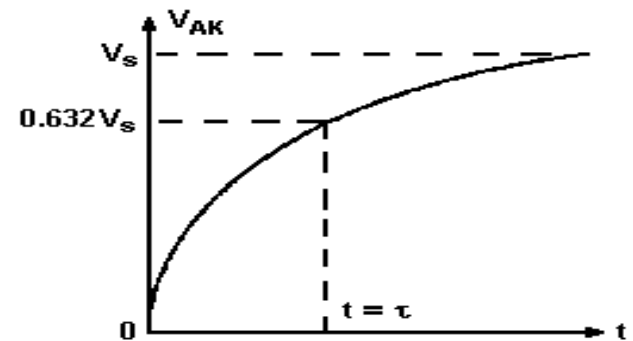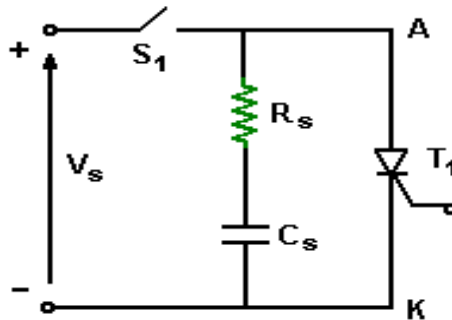
$$\frac{dv}{dt} = \frac{0.632 V_s}{R_s C_s}$$



$$\therefore \text{ Snubber time constant, } T_s = R_s C_s = 0.632 \times \frac{V_s}{\left(\frac{dv}{dt}\right)_{\max}} = 0.632 \times \frac{600}{100} = 3.8 \mu \text{ sec}$$

### Question 22

A thyristor has a load resistance of  $15\Omega$  and operates from 240V supply. If the thyristor has a  $[di/dt]_{\max}$  rating of  $12A/\mu\text{sec}$ , calculate the series inductance that must be included in the circuit to protect it.

Solution:

$$\boxed{\frac{di}{dt} = \frac{V_s}{L_s}} \Rightarrow L_s = \frac{240}{12} = 20\mu H$$

### Question 23

A 200 V, 10A thyristor has a thermal resistance of  $1^\circ\text{C}/\text{W}$ . What is the steady state power loss if the working junction temperature is  $100^\circ\text{C}$  and the ambient temperature is  $15^\circ\text{C}$ .

Solution:

$$\boxed{P_{\text{loss}} = \frac{T_{j\max} - T_a}{R_{ja}}} \Rightarrow P_{\text{loss}} = \frac{100 - 15}{1^\circ\text{C}/\text{W}} = 85 \text{ Watt}$$

### Question 24

A thyristor has thermal resistance of  $1.5^\circ\text{C}/\text{W}$  from junction to air ( including the heat sink). The ambient temperature is  $25^\circ\text{C}$ . If  $T_{J\max} = 125^\circ\text{C}$ , calculate the maximum power loss of the thyristor.

Solution:

$$\boxed{P_{\text{loss}} = \frac{T_{j\max} - T_a}{R_{ja}}} \Rightarrow P_{\text{loss}} = \frac{125 - 25}{1.5^\circ\text{C}/\text{W}} = 66.7 \text{ Watt}$$

# **Chapter 6**

## **AC to DC Convertors**


# AC to DC Convertors

## (Controlled Rectifications)

- Rectifiers can be classified as: **uncontrolled** and **controlled**.
- Controlled rectifiers are divided as: **semi-controlled** and **fully-controlled**.
- Uncontrolled rectifier circuits are built with diodes.
- Fully controlled rectifier circuits are built with SCR's.
- Both diodes and SCR's are used in semi-controlled rectifier circuits.


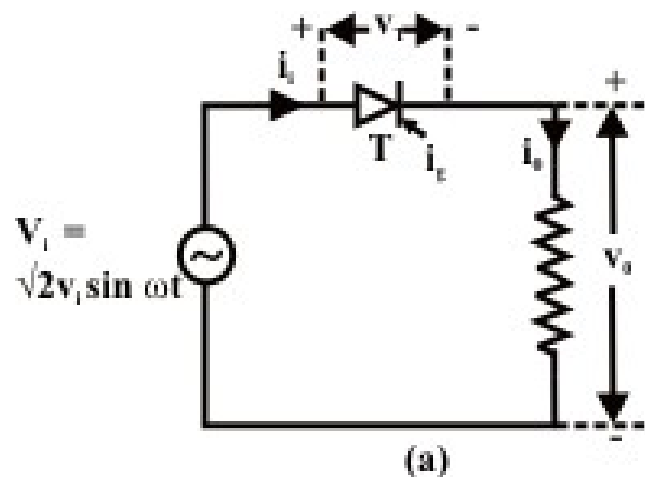
# Single Phase Half Wave Controlled Rectifier with Resistive Load




For  $\alpha < \omega t \leq \pi$

$$v_o = v_i = \sqrt{2} V_i \sin \omega t$$

$$i_o = \frac{v_o}{R} = \sqrt{2} \frac{V_i}{R} \sin \omega t$$

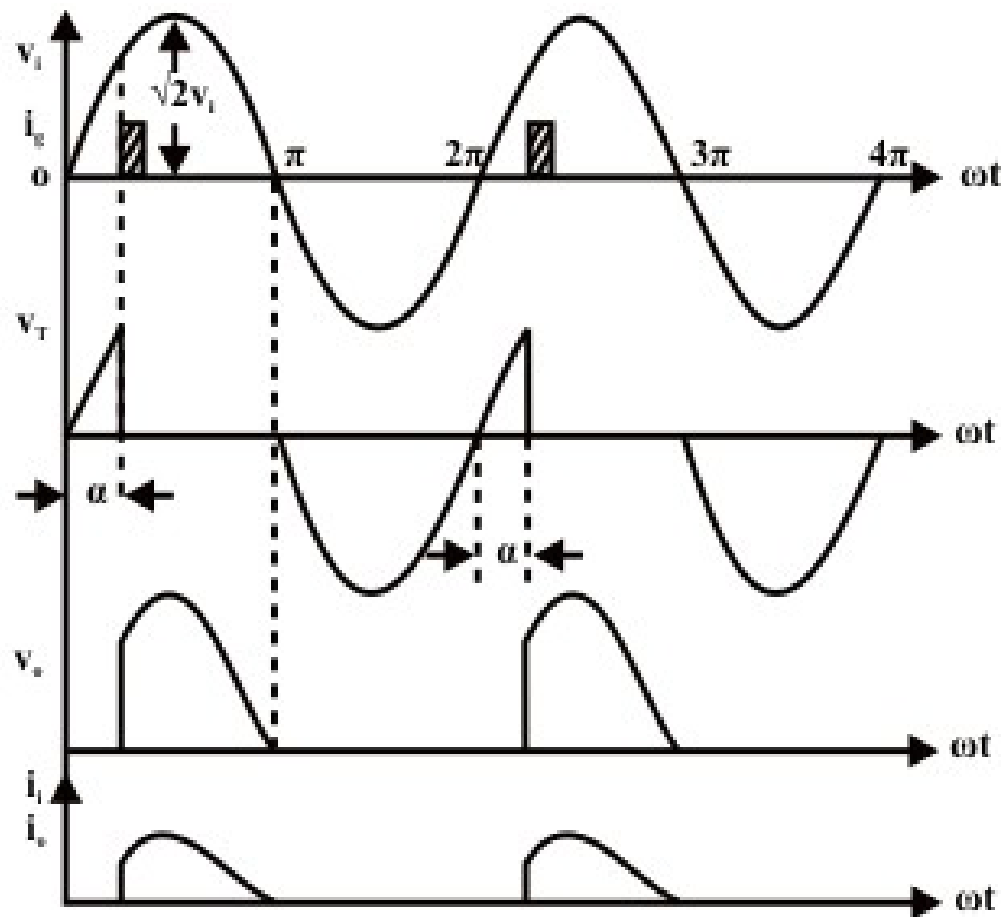
$$V_{o(avg)} = \frac{V_m (1 + \cos \alpha)}{2\pi}$$



These equations tell us that the magnitude of the output voltage is controlled by the firing angle. Increasing  $\alpha$  by firing the SCR later in the cycle lowers the voltage, and vice versa. The maximum output voltage,  $V_{do} = V_m/\pi$ , occurs when  $\alpha = 0^\circ$ . This is the same voltage as for a half-wave diode circuit. Therefore, if the SCR is fired at  $\alpha = 0^\circ$ , the circuit acts like a diode rectifier.

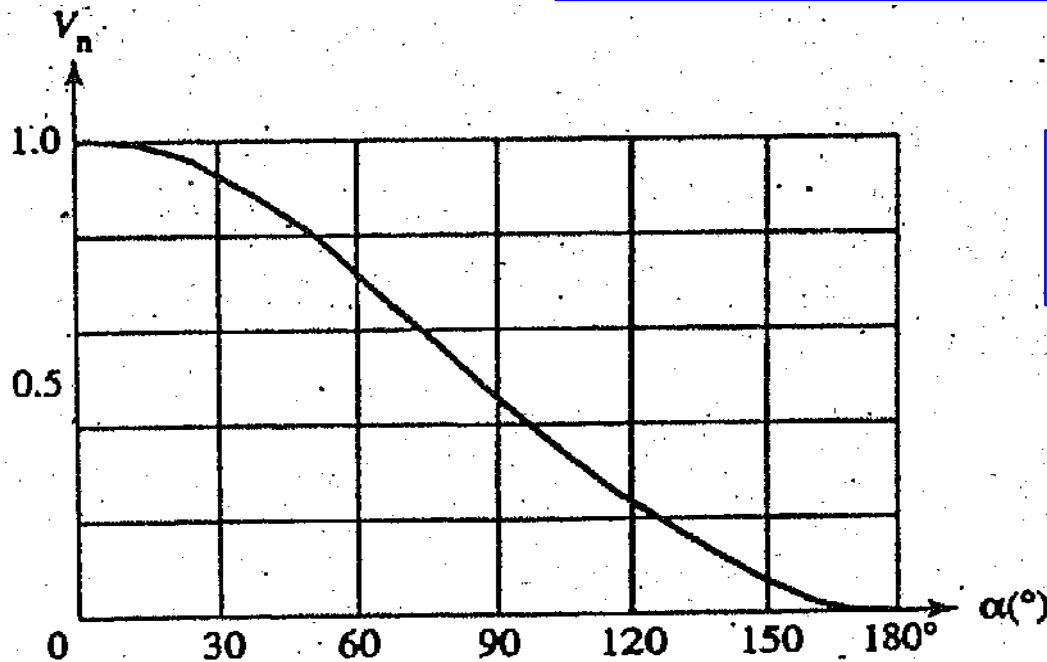**The normalized average voltage is:**


$$V_n = \frac{V_{o(avg)}}{V_{do}} = \frac{V_m (1 + \cos \alpha) / 2\pi}{V_m / \pi} = \frac{1 + \cos \alpha}{2}$$




Delay (firing ) angle:  $\alpha$   
Conduction angle:  $180 - \alpha$

$V_n$  as a function of  $\alpha$  is known as the control characteristic of the rectifier

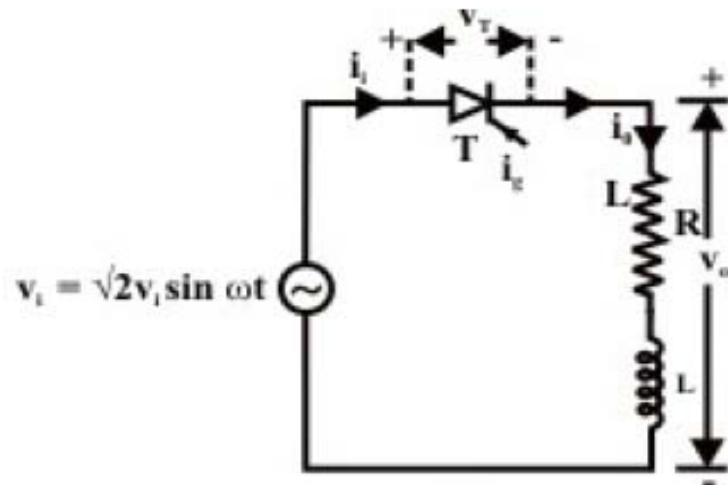
# Single Phase Half Wave Controlled Rectifier with Resistive - Inductive Load



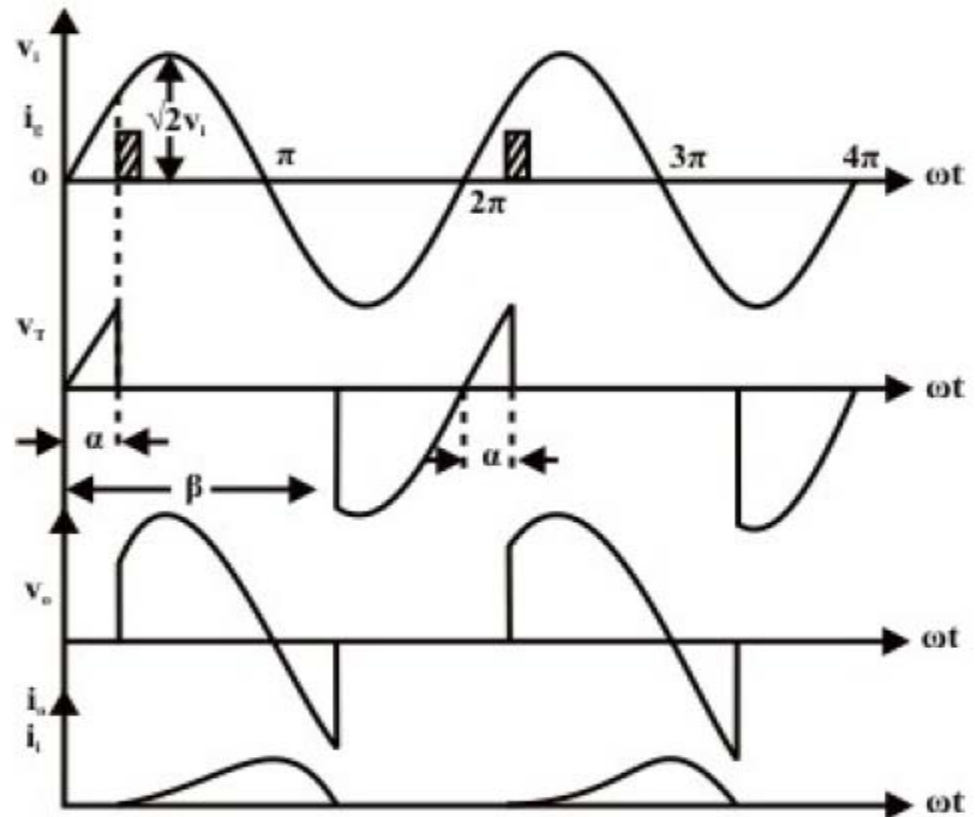
For  $\alpha \leq \omega t \leq \beta$   
 $v_o = v_i = \sqrt{2} V_i \sin \omega t$   
 $v_o = 0$  otherwise


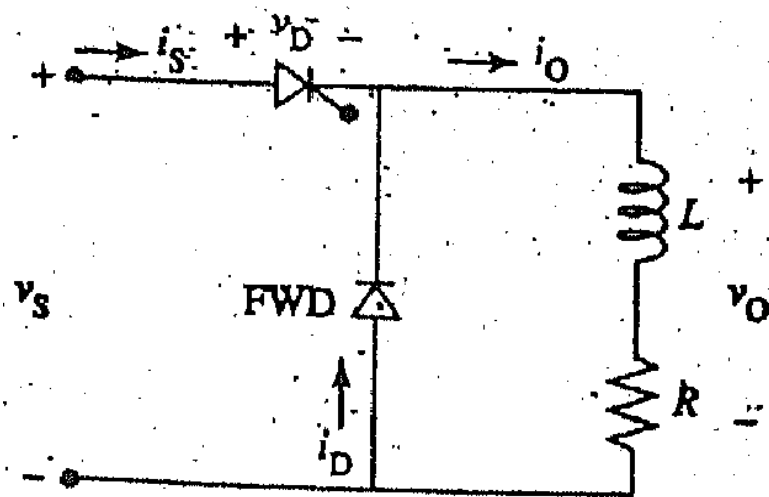
# Single Phase Half Wave Controlled Rectifier with RL Load and Free Wheeling Diode (FWD)


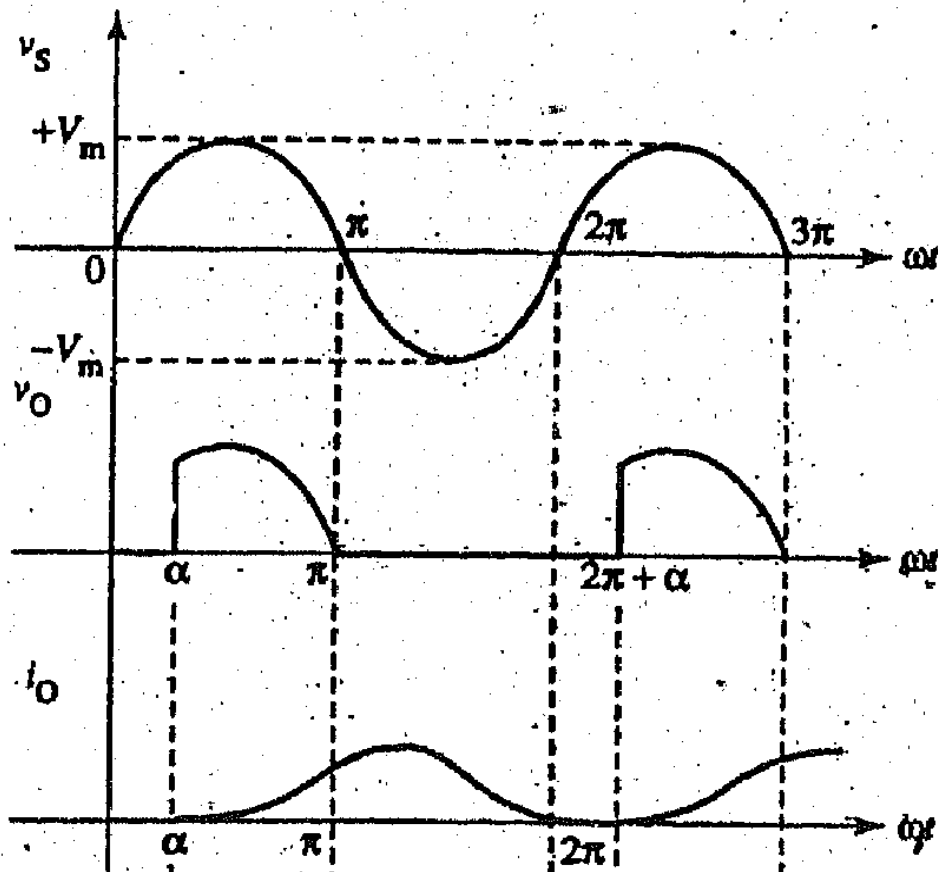
$$V_{o(avg)} = \frac{V_m (1 + \cos \alpha)}{2\pi}$$



### Example 1

A half-wave controlled rectifier is supplied from a 120 V source. If the load resistance is  $10\ \Omega$ , find the load voltage and power to the load for the following delay angles:

a)  $\alpha = 0^\circ$

b)  $\alpha = 45^\circ$

### Solution:

$$\text{peak load voltage} = V_m = \sqrt{2} V_s = 1.414 \cdot 120 = 170\text{ V}$$

$$\text{average load voltage} = \frac{V_m (1 + \cos \alpha)}{2\pi}$$

a) For  $\alpha = 0^\circ$ , we get

$$V_{o(\text{avg.})} = \frac{170 (1 + \cos 0^\circ)}{2\pi} = 54.0\text{ V}$$

$$P_L = V_{o(\text{avg.})}^2 / R = 54.0^2 / 10 = 293\text{ W}$$

b) For  $\alpha = 45^\circ$ , we get

$$V_{o(\text{avg.})} = \frac{170 (1 + \cos 45^\circ)}{2\pi} = 46.2\text{ V}$$

$$P_L = V_{o(\text{avg.})}^2 / R = 46.2^2 / 10 = 213\text{ W}$$

## Example 2

Half wave controlled rectifier connected to 150 V, 60Hz source is supplying a resistive load of  $10\Omega$  .if the delay angle  $\alpha$  is  $30^\circ$ , find:-

- a- The maximum load current,    b- The average load voltage,    c- The average load current,  
d-The RMS load current,    e- The power supplied to the load , f- The conduction angle  
g- The ripple frequency,    h- The power factor

### Solution:

$$V_m = \sqrt{2} V_s = 1.414 \times 150 = 212 \text{ V}$$

a) maximum load current

$$I_m = \frac{V_m}{R} = \frac{212}{10} = 21.2 \text{ A}$$

$$\text{b) average load voltage} = \frac{V_m(1 + \cos \alpha)}{2 \pi} = \frac{(212)(1 + \cos 30^\circ)}{2 \pi} = 63 \text{ V}$$

$$\text{c) average load current} = \frac{(I_m)(1 + \cos \alpha)}{2 \pi} = \frac{(21.2)(1 + \cos 30^\circ)}{2 \pi} = 6.3 \text{ A}$$

d) RMS load current

$$\begin{aligned} I_{\text{RMS}} &= \left( \frac{I_m}{2} \right) \sqrt{\left[ 1 - \frac{\alpha}{\pi} + \frac{\sin 2 \alpha}{2 \pi} \right]} \\ &= \frac{(21.2)}{2} \sqrt{\left[ 1 - \frac{30}{180} + \frac{\sin 60}{2 \pi} \right]} \\ &= 10.5 \text{ A} \end{aligned}$$

- e) power supplied to the load =  $I_{\text{RMS}}^2 R = 10.5^2(10) = 1094 \text{ W}$   
 f) conduction angle

$$\theta = 180^\circ - \alpha = 180^\circ - 30^\circ = 150^\circ$$

- g) ripple frequency

$$f_r = \text{input supply frequency} = 60 \text{ Hz}$$

- h)  $S = V_s \cdot I_{\text{RMS}} = 150 \cdot 10.5 = 1575 \text{ VA}$

$$\text{PF} = \frac{P}{S} = \frac{1094}{1575} = 0.69$$

**Example 3** A half wave controlled rectifier is connected to a 120 V source , Calculate the firing angle necessary to deliver 150 W of power to  $10\Omega$  load.

**Solution:**

$$V_{\text{O(avg.)}} = \frac{V_m(1 + \cos \alpha)}{2\pi}$$

Rearranging.

$$V_m (1 + \cos \alpha) = 2 \pi V_{\text{O(avg.)}}$$

$$1 + \cos \alpha = \frac{2\pi V_{\text{O(avg.)}}}{V_m}$$

$$\cos \alpha = \frac{2\pi V_{\text{O(avg.)}}}{V_m} - 1$$

$$\alpha = \cos^{-1} \left\{ \frac{2\pi V_{\text{O(avg.)}}}{V_m} - 1 \right\}$$

$$V_m = \sqrt{2} \cdot 120 = 170 \text{ V}$$

$$P_{\text{avg.}} = \frac{V_{\text{O(avg.)}}^2}{R}$$



$$V_{\text{O(avg.)}}^2 = P_{\text{avg.}} \cdot R = 150 \cdot 10 = 1500$$

$$V_{\text{O(avg.)}} = \sqrt{1500} = 38.7 \text{ V}$$

Therefore

$$\begin{aligned} \alpha &= \cos^{-1} \left\{ \frac{2\pi \cdot 38.7}{170} - 1 \right\} \\ &= 64.5^\circ \end{aligned}$$
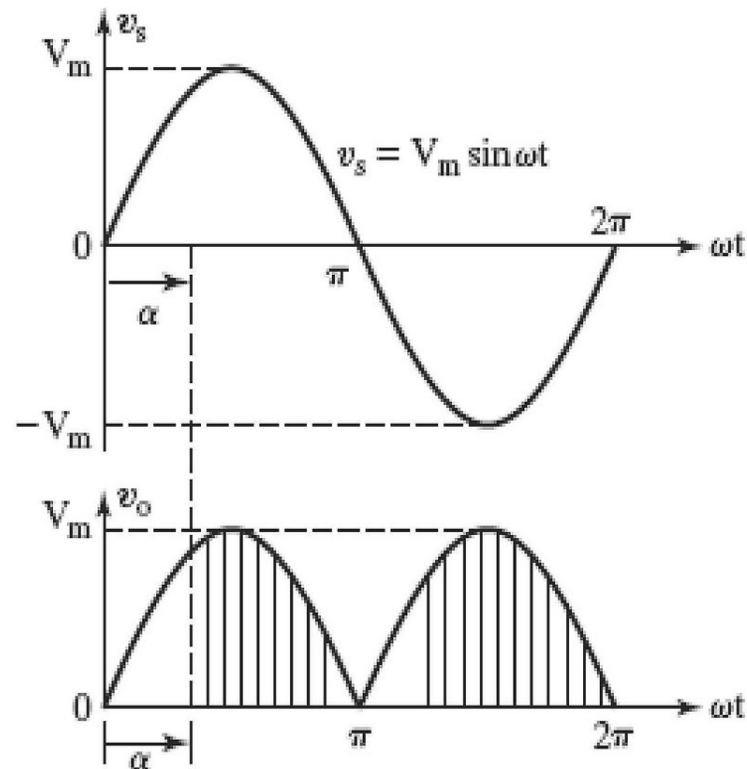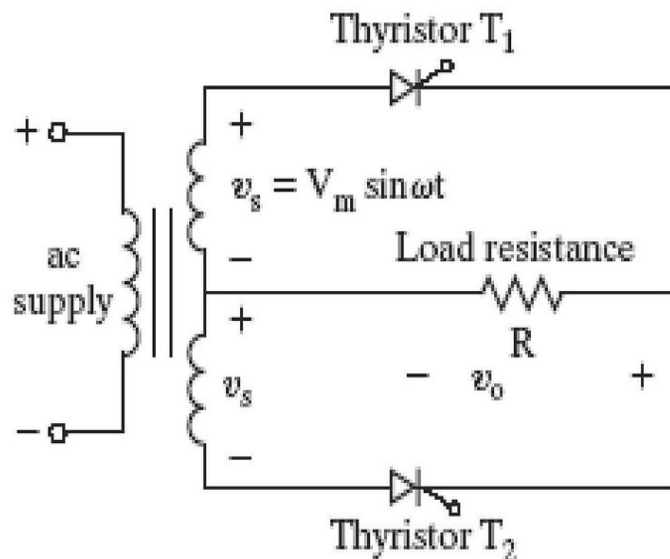
# Single Phase Full Wave Controlled Rectifier with Center-Tap Transformer and R Load



Delay (firing ) angle:  $\alpha$   
Conduction angle:  $180-\alpha$



$$V_{o,DC} = \frac{V_m}{\pi} (1 + \cos \alpha)$$

$$V_{o,RMS} = V_m \sqrt{\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin(2\alpha)}{4\pi}}$$

$$I_{o,RMS} = \frac{V_{o,RMS}}{R}$$


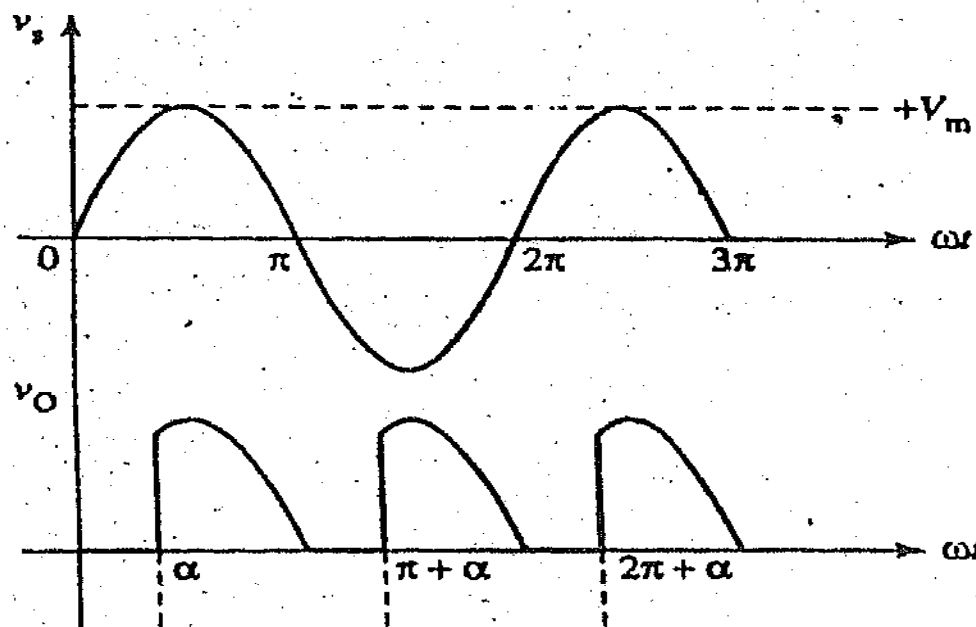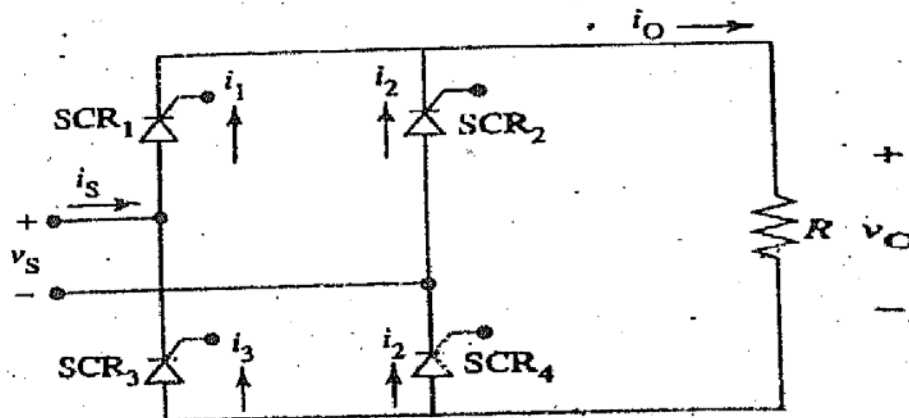
# Single Phase Full Wave Bridge Controlled Rectifier with R Load



Delay (firing) angle:  $\alpha$   
Conduction angle:  $180^\circ - \alpha$


$$V_{o,DC} = \frac{V_m}{\pi} (1 + \cos \alpha)$$

$$V_{o,RMS} = V_m \sqrt{\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin(2\alpha)}{4\pi}}$$

$$I_{o,RMS} = \frac{V_{o,RMS}}{R}$$

$$I_{o(avg)} = \frac{V_{o,DC}}{R} = \frac{I_m (1 + \cos \alpha)}{\pi}$$
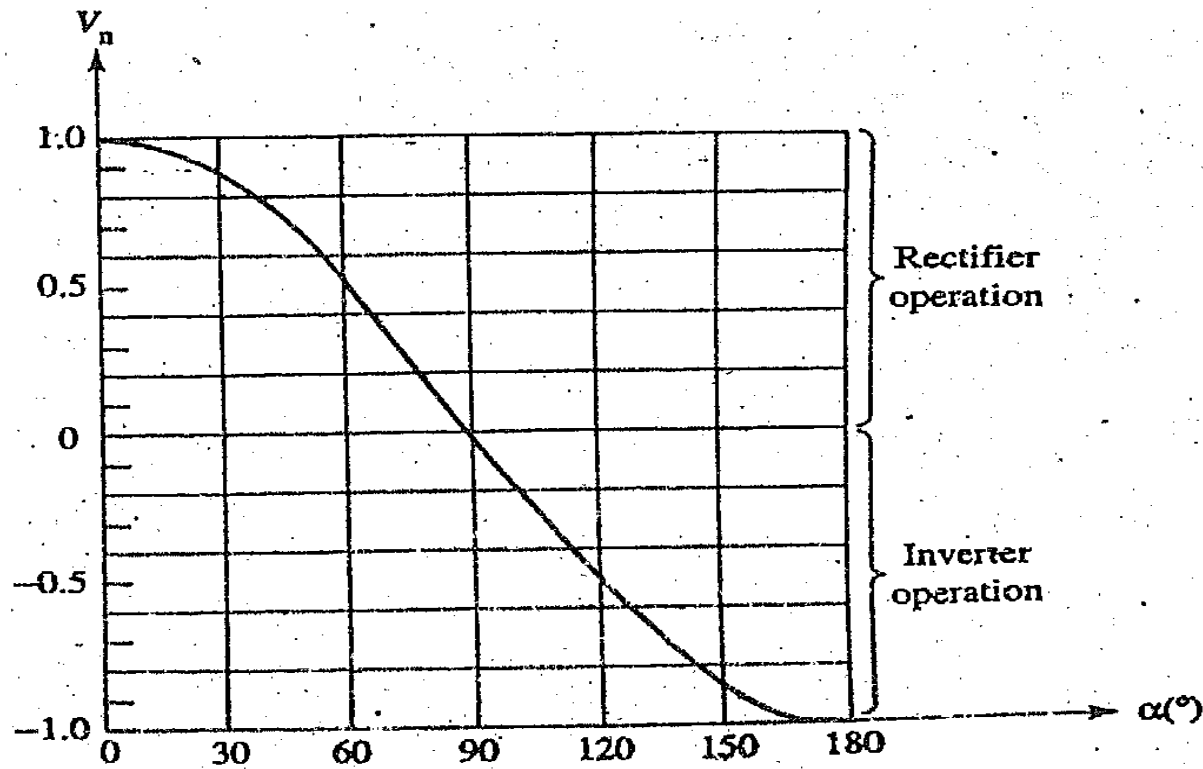
# Control Characteristics for the Bridge Rectifier



- When  $\alpha$  becomes larger than  $90^\circ$ , the average value of output voltage becomes negative. This means that  $90^\circ$  to  $180^\circ$  power flows from the DC load side to the AC source side and the circuit operates as an inverter.
- When rectification and inversion are obtained from one converter, the process is called two-quadrant operation and the converter is called a full converter.

## Example 4

Full wave controlled rectifier connected to 150 V, 60Hz source is supplying a resistive load of  $10\Omega$ . if the delay angle  $\alpha$  is  $30^\circ$ , find: a- The average load voltage, b- The average load current c- The maximum load current, d- The RMS load current, e- The power supplied to the load, f- The conduction angle, g- The ripple frequency, h- The power factor.

### Solution:

$$V_m = \sqrt{2} (150) = 212 \text{ V}$$

$$\text{a) average load voltage} = \frac{V_m(1 + \cos \alpha)}{\pi} = \frac{(212)(1 + \cos 30^\circ)}{\pi} = 126 \text{ V}$$

$$\text{b) average load current} = \frac{(V_m)(1 + \cos 30^\circ)}{R\pi} = 12.6 \text{ A}$$

c) maximum load current

$$I_m = \frac{V_m}{R} = \frac{212}{10} = 21.2 \text{ A}$$

$$\begin{aligned} \text{d) RMS load current} \quad I_{\text{RMS}} &= \frac{I_m}{\sqrt{2}} \sqrt{\left[1 - \frac{\alpha}{\pi} + \frac{\sin 2\alpha}{2\pi}\right]} \\ &= 14.8 \text{ A} \end{aligned}$$

$$\text{e) Power supplied to the load} = I^2_{\text{rms}} \cdot R = 14.8^2(10) = 2182 \text{ W}$$

$$\text{f) The conduction angle} = 180^\circ - \alpha = 150^\circ$$

$$\text{g) Ripple frequency} \quad f_r = 2 \times \text{input supply frequency} = 2 \times 60 = 120 \text{ Hz}$$

$$\text{h) } S = V_s \times I_{\text{rms}} = 150 \times 14.8 = 2220 \text{ VA}$$

$$\text{P.F} = P / S = 2182 / 2220 = 0.98$$

# Problems and Solutions

- Question 1** A full-wave center-tap rectifier is fed from a transformer with a secondary voltage of 120 V (center-tap to line). If it is used to charge a 12 V battery having an internal resistance of  $0.1 \Omega$ , find
- (a) the firing angle necessary to produce a charging current of 10 A
  - (b) the average SCR current
  - (c) the PIV rating of the SCR

Solution:

$$\text{a) } I_{dc} = \frac{V_{dc} - E}{R} \Rightarrow 10 = \frac{V_{dc} - 12}{0.1} \Rightarrow V_{dc} = 13 \text{ Volt}$$

$$V_{dc} = \frac{V_m (1 + \cos \alpha)}{\pi}$$

$$13 = \frac{(1.414 \times 120)(1 + \cos \alpha)}{\pi} \Rightarrow \cos \alpha = -0.16 \Rightarrow \therefore \alpha = 99.2^\circ$$

$$\text{b) } I_{SCR(avg)} = \frac{I_{dc} (180 - \alpha)}{2\pi} = \frac{10(180 - 99.2)}{360} = 2.24 \text{ A}$$

$$\text{c) } PIV = 2V_m = 2 \times (1.414 \times 120) = 340 \text{ Volt}$$

## Question 2

A half-wave controlled rectifier is supplied from a 120 V source is used to control the power to a  $15\Omega$  load. If the delay angle is  $75^\circ$ , find:-

- a) the power supplied to the load , b) the maximum SCR current  
c) the average SCR current, d) the SCR maximum reverse voltage

### Solution:

$$\text{a) } P_s = \frac{V_{o,RMS}^2}{R} \Rightarrow V_{o,RMS}^2 = \left( \frac{V_m}{2} \right)^2 \left( 1 - \frac{\alpha}{\pi} + \frac{\sin 2\alpha}{2\pi} \right)$$

$$V_{o,RMS}^2 = \left( \frac{1.414 \times 120}{2} \right)^2 \left( 1 - \frac{75}{180} + \frac{\sin(2 \times 75)}{2 \times 3.14} \right) = 4761 \text{ V}^2$$

$$\therefore P_s = \frac{4761}{15} = 317.7 \text{ Watt}$$

$$\text{b) } I_{SCR(MAX)} = I_m = \frac{V_m}{R} = \frac{1.414 \times 120}{15} = 11.3 \text{ A}$$

$$\text{c) } I_{SCR(avg)} = \frac{V_{dc}}{R} = \frac{V_m (1 + \cos \alpha) / 2\pi}{R} = \frac{(1.414 \times 120)(1 + \cos 75)}{2 \times 3.14 \times 15} = 2.3 \text{ A}$$

$$\text{d) } PIV = V_m = 1.414 \times 120 = 170 \text{ Volt}$$

### Question 3

A full - wave fully controlled rectifier with R load is fed from 200V source supplies an average current of 10A. If the firing angle is  $30^\circ$ , find:

- a) the average power delivered to the load, b) the average SCR current,  
c) the maximum SCR current, d) the SCR peak reverse voltage, e) the load resistance

### Solution:

$$\text{a) } P_{avg} = V_{avg} I_{avg} \Rightarrow \boxed{V_{avg} = V_{dc} = \frac{V_m (1 + \cos \alpha)}{\pi}}$$

$$V_{avg} = \frac{(1.414 \times 200)(1 + \cos 30)}{3.14} = 168 \text{ Volt}$$

$$\text{b) } I_{SCR(avg)} = \frac{I_{dc} (180 - \alpha)}{2\pi} = \frac{10(180 - 30)}{360} = 8.33 \text{ A}$$

$$\text{c) } I_m = \frac{V_m}{R} = \frac{1.414 \times 200}{(168/10)} = 16.8 \text{ A}$$

$$\text{d) } PIV = V_m = 1.414 \times 200 = 282.8 \text{ Volt}$$

$$\text{e) } R = \frac{V_{avg}}{I_{avg}} = \frac{168}{10} = 16.8 \Omega$$

#### Question 4

A single phase Half-Wave converter is fed by transformer whose secondary voltage is  $325\sin\omega t$ . It supplies a resistance load of  $20\Omega$  for firing angle of  $45^\circ$ , calculate:

a) average values of load voltage and current, b) rms values of load voltage and current, c)  $P_{dc}$ ,  $P_{ac}$  and rectification efficiency  $\eta$ , d) form factor (FF), e) the VA rating  $S$  of the transformer and utilization factor UTF, g) PIV of the thyristor.

#### Solution:

$$\text{a) } V_{avg} = \frac{V_m (1 + \cos \alpha)}{2\pi} = \frac{325(1 + \cos 45)}{2 \times 3.14} = 88.5 \text{ Volt}$$

$$I_{avg} = V_{avg} / R = 88.5 / 20 = 4.4 \text{ A}$$

$$\text{b) } V_{oRMS} = \left( \frac{V_m}{2} \right) \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin 2\alpha}{2\pi}} = \left( \frac{325}{2} \right) \sqrt{1 - \frac{45}{180} + \frac{\sin 90}{2 \times 3.14}} = 155 \text{ Volt}$$

$$I_{oRMS} = V_{oRMS} / R = 155 / 20 = 7.75 \text{ A}$$

$$\text{c) } P_{dc} = V_{dc}^2 / R = (88.5)^2 / 20 = 387.2 \text{ W}$$

$$P_{ac} = V_{oRMS}^2 / R = (155)^2 / 20 = 1201 \text{ W}$$

$$\eta = (P_{dc} / P_{ac}) \times 100\% = (387.2 / 1201) \times 100\% = 32\%$$

$$\text{d) } FF = V_{oRMS} / V_{dc} = 155 / 88.5 = 1.75$$

$$\text{e) } VA = S = V_{RMS} I_{RMS} = (325 / \sqrt{2}) \times 7.75 = 1781.3 \text{ W}$$

$$TUF = (P_{dc} / S) \times 100\% = (387.2 / 1781.3) \times 100\% = 21.7\%$$

$$\begin{aligned} \text{g) } PIV &= V_m \\ &= 325 \text{ Volt} \end{aligned}$$

**Question 5**

A single phase Half-Wave converter is used to control 1kw power of  $10\Omega$  dc load , for 240V, 50Hz supply, calculate the firing angle  $\alpha$

Solution:

$$P_{dc} = V_{avg}^2 / R = 1000 \Rightarrow V_{avg} = \sqrt{1000 \times 10} = 100 \text{ Volt}$$

$$V_{avg} = \frac{V_m (1 + \cos \alpha)}{2\pi} \Rightarrow V_{avg} = \frac{(1.414 \times 240)(1 + \cos \alpha)}{2 \times 3.14} = 100 \Rightarrow \alpha = 31.7^\circ$$

**Question 6**

A single phase Half-Wave converter is connected to  $15\Omega$  load and supply voltage of 230V,50Hz. For firing angle  $\alpha = 30^\circ$  and  $60^\circ$ , calculate:  $V_{dc}$  and  $V_{SCR}$ .

Solution:

$$V_m = 1.414 \times 230 = 325 \text{ Volt}$$

$$V_{avg} = \frac{V_m (1 + \cos \alpha)}{2\pi} \quad V_{SCR} = \frac{V_m (1 - \cos \alpha)}{2\pi}$$

$$\text{For } \alpha = 30^\circ \Rightarrow V_{avg} = \frac{325(1 + \cos 30)}{2 \times 3.14} = 96.7 \text{ Volt}$$

$$V_{SCR} = \frac{325(1 - \cos 30)}{2 \times 3.14} = 6.7 \text{ Volt}$$

Similarly for  $\alpha = 60^\circ \Rightarrow V_{avg} = 77.7 \text{ Volt}$ , and  $V_{SCR} = 25.9 \text{ Volt}$



### Question 7

For the given single phase Half-Wave converter, the delay angle  $\alpha = 90^\circ$ . Calculate the:  
a) efficiency  $\eta$ , b) form factor (FF), c) transformer utilization factor UTF, d) SCR current.

#### Solution:

$$V_m = 1.414 \times 45 = 63.63 \text{ Volt}$$

$$V_{avg} = \frac{V_m (1 + \cos \alpha)}{2\pi} = \frac{63.63 (1 + \cos 90)}{2 \times 3.14} = 10.7 \text{ Volt}$$

$$I_{avg} = V_{avg} / R = 10.7 / 33 = 0.324 \text{ A}$$

$$V_{oRMS} = \left( \frac{V_m}{2} \right) \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin 2\alpha}{2\pi}} = \left( \frac{63.63}{2} \right) \sqrt{1 - \frac{90}{180} + \frac{\sin 180}{2 \times 3.14}} = 22.5 \text{ Volt}$$

$$I_{oRMS} = V_{oRMS} / R = 22.5 / 33 = 0.681 \text{ A}$$

$$\text{a) } \eta = (P_{dc} / P_{ac}) \times 100\% = (V_{dc}^2 / V_{oRMS}^2) \times 100\% = ((10.7)^2 / (22.5)^2) \times 100\% = 20\%$$


$$\text{b) } FF = V_{oRMS} / V_{dc} = 22.5 / 10.7 = 2.23$$

$$\text{c) } P_{dc} = V_{avg} I_{avg} = 10.7 \times 0.324 = 3.47 \text{ W}$$

$$VA = S = V_{RMS} I_{RMS} = 22.5 \times 0.681 = 15.3 \text{ W}$$

$$TUF = (P_{dc} / S) \times 100\% = (3.47 / 15.3) \times 100\% = 10.15\%$$
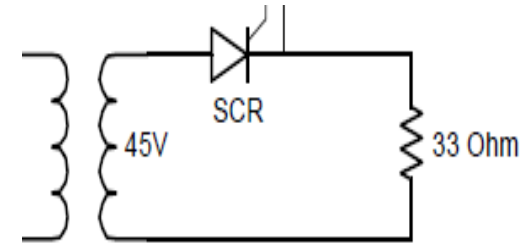
$$\text{d) } I_{SCR} = I_{avg} = 0.324 \text{ A}$$





**Question 8** For the given single phase Half-Wave converter, the delay angle  $\alpha = 30^\circ$ .  
Solution: Calculate: a)  $I_{dc}$ , b) draw the waveforms of  $V_{Load}$ , and  $I_{Load}$ .

a)  $V_m = 1.414 \times 45 = 63.63 \text{ Volt}$

$$V_{avg} = \frac{V_m (1 + \cos \alpha)}{2\pi} = \frac{63.63 (1 + \cos 30)}{2 \times 3.14} = 15.2 \text{ Volt}$$

$$I_{dc} = I_{avg} = V_{avg} / R = 15.2 / 33 = 0.46 \text{ A}$$

b)

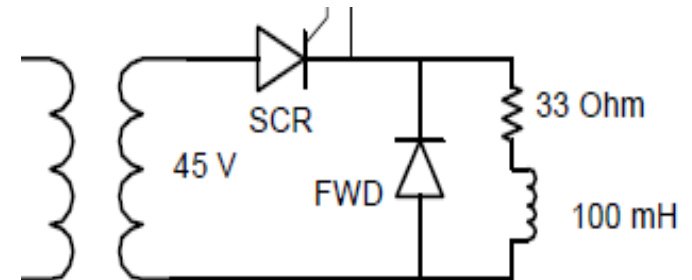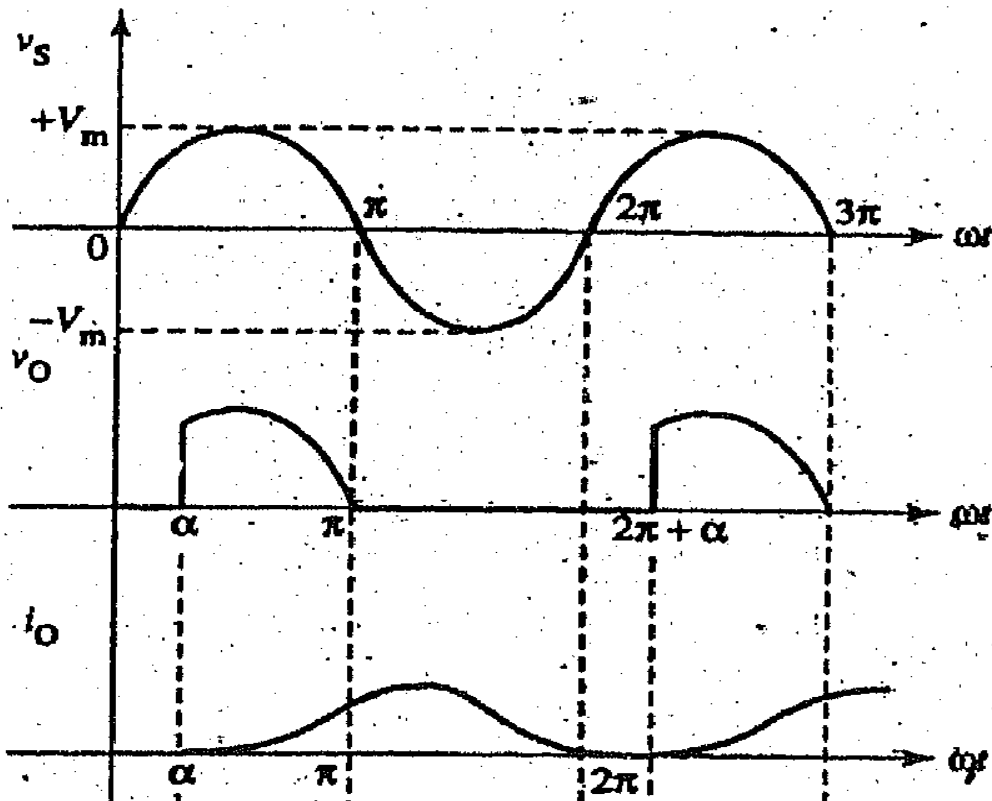

### Question 9

A 1- $\Phi$  full wave converter is operated at 230V, 50Hz for a resistive load of  $12\Omega$ . If the average output voltage is 25% of maximum possible average output voltage, find (i) delay angle (ii) average and rms output currents (iii) average and rms thyristors currents.

#### Solution:

$$\text{i) } V_{avg} = 0.25 \times V_{avg(\max)} = 0.25 \times \frac{2V_m}{\pi} = \frac{V_m (1 + \cos \alpha)}{\pi}$$

$$\Rightarrow \cos \alpha = -0.5 \Rightarrow \alpha = 120^\circ$$

$$\text{ii) } I_{avg} = \frac{V_{avg}}{R} = \frac{V_m (1 + \cos \alpha)}{\pi R} = \frac{(1.414 \times 230)(1 + \cos 120)}{3.14 \times 12} = 4.3 \text{ A}$$

$$V_{oRMS} = \left( \frac{V_m}{2} \right) \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin 2\alpha}{2\pi}} = \left( \frac{1.414 \times 230}{2} \right) \sqrt{1 - \frac{120}{180} + \frac{\sin 240}{2 \times 3.14}} = 100.8 \text{ Volt}$$

$$I_{oRMS} = V_{oRMS} / R = 100.8 / 12 = 8.4 \text{ A}$$

$$\text{iii) } I_{SCRavg} = I_{avg} / 2 = 4.3 / 2 = 2.65 \text{ A}$$

$$I_{SCRrms} = I_{SCRavg} / \sqrt{2} = 2.65 / 1.414 = 1.87 \text{ A}$$

## Question 10 Choose the correct answer for the following Questions

1) A thyristor of half wave controlled converter has a supply voltage of 240V at 50Hz and a load resistance of 100 Ohm. When the firing angle is 30, the average value of load current is.....

- A. 126 A,      B. 2.4 A,      **C.** 126 mA,      D. 24 A
- 

2) A half-controlled bridge converter is operating from an r.m.s input voltage of 120 V. Neglecting the voltage drops, what are the mean load voltage at a firing delay angle of  $0^\circ$  and  $180^\circ$ , respectively ?

- (A)  $\frac{120 \times 2\sqrt{2}}{\pi}$  V and 0      **(C)**  $\frac{120\sqrt{2}}{\pi}$  V and 0  
(B) 0 and  $\frac{120 \times 2\sqrt{2}}{\pi}$  V      (D) 0 and  $\frac{120\sqrt{2}}{\pi}$  V
- 

3) In a single phase full wave controlled bridge rectifier, minimum output voltage and maximum output voltage are obtained at which conduction angles ?

- (A)**  $0^\circ, 180^\circ$  respectively      (C)  $0^\circ, 0^\circ$  respectively  
(B)  $180^\circ, 0^\circ$  respectively      (D)  $180^\circ, 180^\circ$  respectively

## Question 11      Fill in the Following Blanks with the Correct Word (s)

- 1) The controlled AC-DC converters are used to convert an ..... **AC** .....voltage of variable...**Amplitude**..... and frequency to a variable ...**DC**..... voltage.
- 2) Single phase half wave controlled rectifier is constructed using one ..... **SCR**.....
- 3) ...  **$\alpha$**  ...is the number of degrees from the beginning of the cycle until the SCR is gated ON.
- 4) .....  **$180 - \alpha$**  .....is the number of degrees that the SCR remains conducting.
- 5) .....  **$\alpha$**  ....is the degree at which the SCR is turning off in full wave controlled rectifier.
- 6) A fully-controlled rectifier circuit contains only..... **SCR**.....rectifiers, whereas a ..... **semi-controlled rectifier** .....circuit is made up of both diodes and SCRs.



# **Chapter 7**

## **DC-DC Convertors (DC Choppers)**


# DC Choppers

## (DC to DC Convertors)

- Chopper is a static device and known as DC-to-DC converter.
- A variable DC voltage is obtained from a constant DC source.
- Widely used for motor control.
- Also used in regenerative braking.
- Thyristor converter offers greater efficiency, faster response, lower maintenance, smaller size and smooth control.
- Choppers are of two types:
  - ❑ *Step-Down Choppers:* output voltage is less than the input.
  - ❑ *Step-Up Choppers:* output voltage is more than the input.



# Principle of Step-Down Chopper

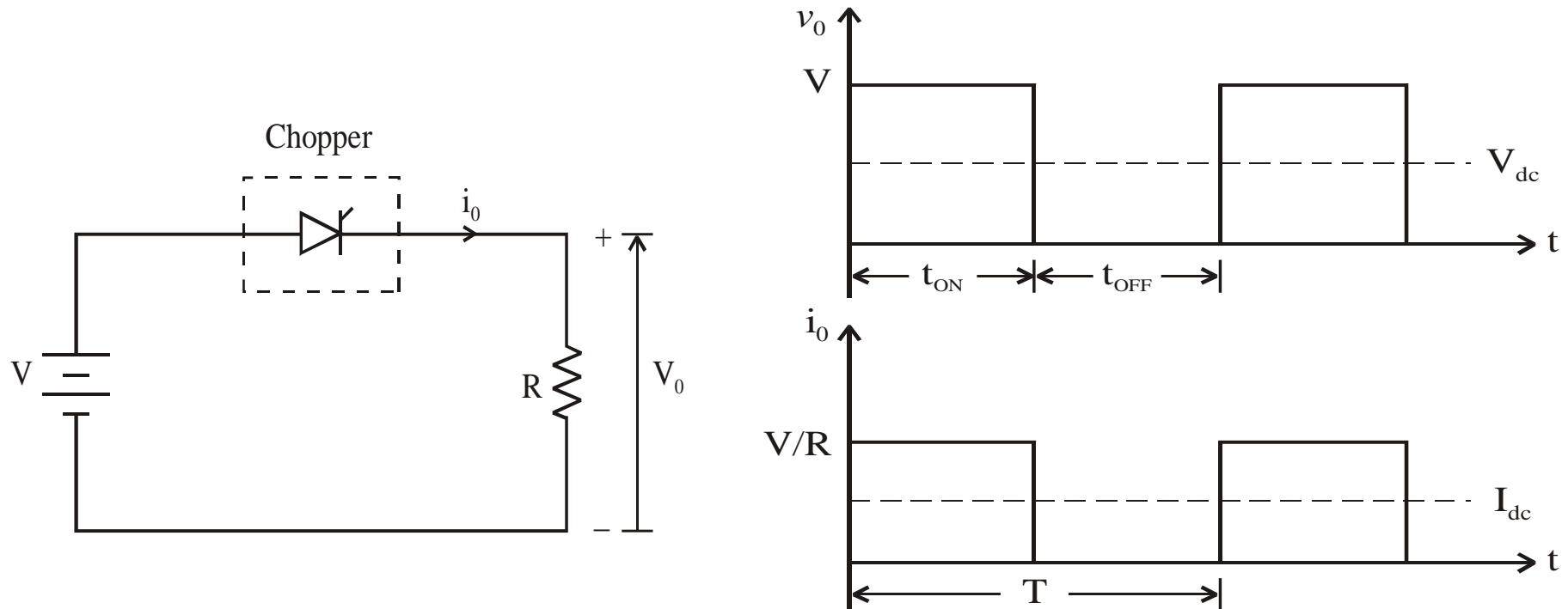

## A step-down chopper with resistive load

- The thyristor acts as a switch.
- When thyristor is ON, the supply voltage appears across the load.
- When thyristor is OFF, the voltage across the load will be zero.

$V_{dc}$  = Average value of load voltage.

$I_{dc}$  = Average value of load current.

$t_{ON}$  = Time interval for which SCR conducts.

$t_{OFF}$  = Time interval for which SCR is OFF.

$T = t_{ON} + t_{OFF}$  = Period of switching (chopping).

$f = 1/T$  = Freq. of chopper switching (chopping freq).

$$\text{Average Output Voltage: } V_{dc} = V \left( \frac{t_{ON}}{t_{ON} + t_{OFF}} \right) = V \left( \frac{t_{ON}}{T} \right) = Vd$$

where the duty cycle is:  $d = (t_{ON} / T)$

and during  $t_{ON}$ ,  $v_o = V \Rightarrow$  therefore RMS output voltage will be

$$V_o = \sqrt{\frac{1}{T} \int_0^{t_{ON}} V^2 dt} = \sqrt{\frac{V^2}{T} t_{ON}} = \sqrt{\frac{t_{ON}}{T}} V = \sqrt{d} V$$

Output power:  $P_o = V_o I_o = (V_o^2 / R) = (d^2 VR)$

Effective input resistance of chopper:  $R_i = (V / I_{dc}) = R / d$

The output voltage can be varied by varying the duty cycle

# Methods of Control


Output DC voltage can be varied by the following methods:

- ❑ Pulse Width Modulation (PWM) control or constant frequency operation.
- ❑ Variable frequency control.
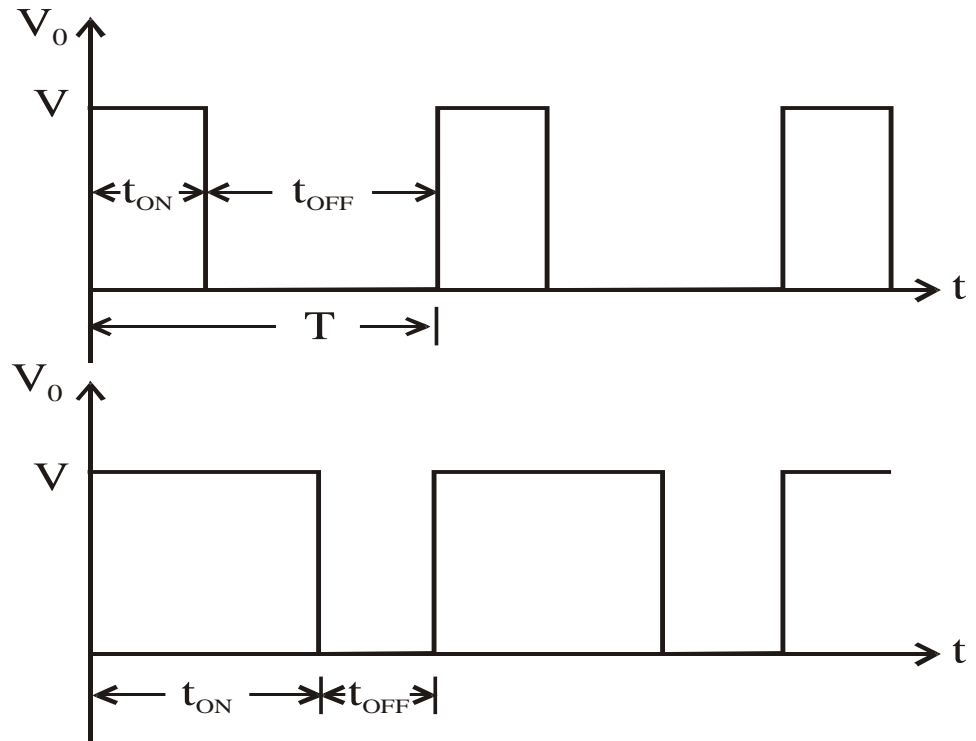
## *Pulse Width Modulation (PWM)*


➤  $t_{ON}$  is varied keeping chopping frequency  $f$  and chopping period  $T$  constant.

➤ Output voltage is varied by varying the ON time  $t_{ON}$




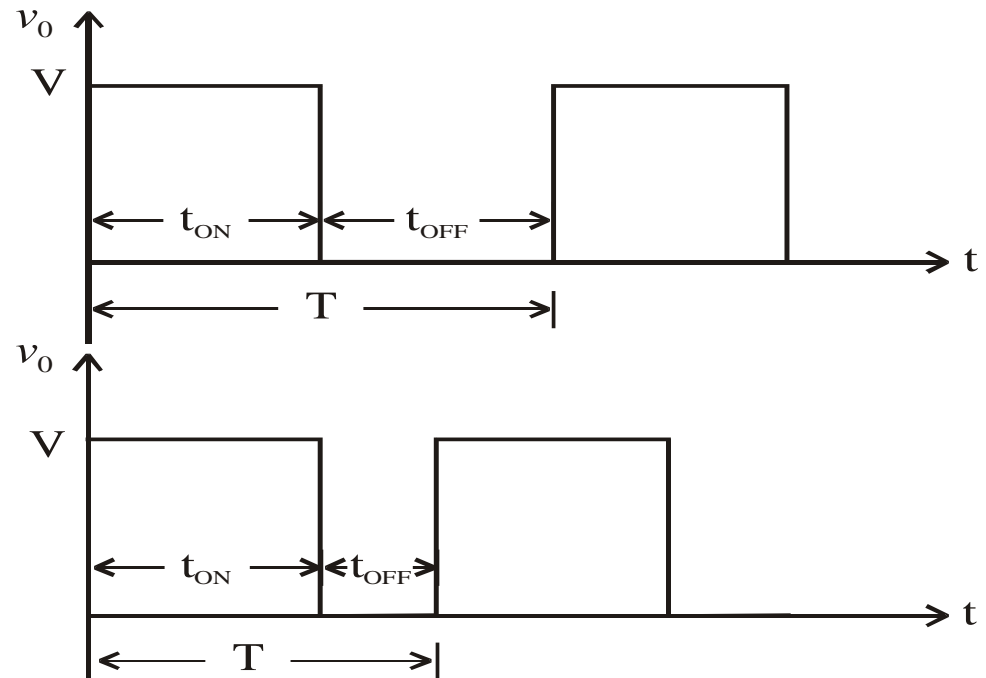
# Variable Frequency Control

- Chopping frequency  $f$  is varied keeping either  $t_{ON}$  or  $t_{OFF}$  constant.
- To obtain full output voltage range,  $f$  has to be varied over a wide range.
- This method produces harmonics in the output and for large  $t_{OFF}$ , load current may become discontinuous.



# Step-Down Chopper with $R$ - $L$ Load

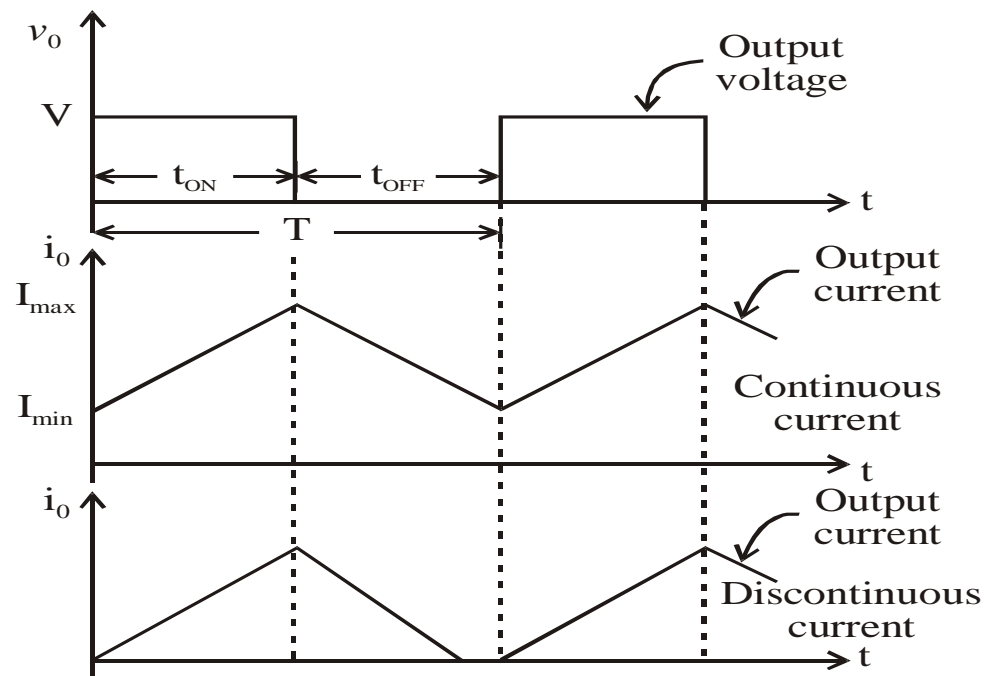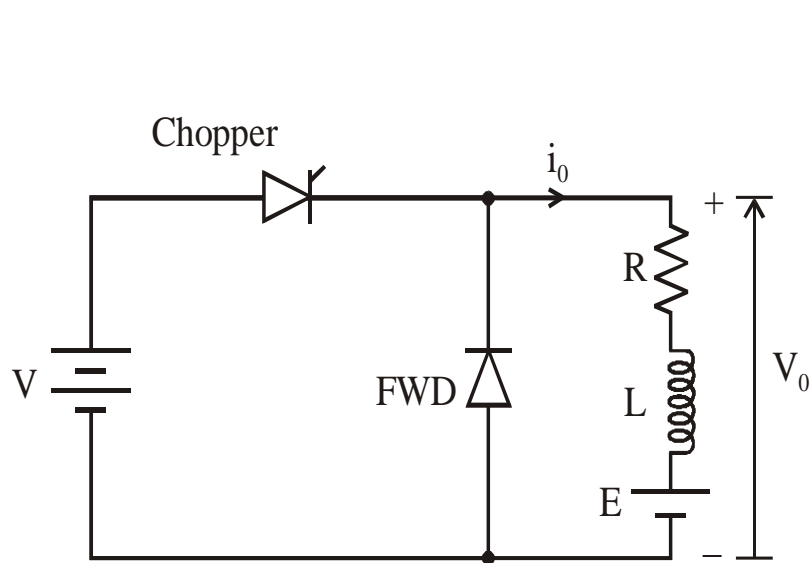

- When chopper is ON, the current flows from the supply  $V$  to load.
- When chopper is OFF, load current continues to flow in the same direction through FWD due to energy stored in the inductor  $L$ .
- Load current can be continuous or discontinuous depending on  $L$  and duty cycle  $d$ .
- For continuous current operation, load current varies between  $I_{max}$  and  $I_{min}$ .
- When current becomes equal to  $I_{max}$ , the chopper is turned-off, and it is turned-on when the current reduces to  $I_{min}$ .

$$I_{\min} = \left( I_{\max} e^{-\frac{(1-d)RT}{L}} \right) - \frac{E}{R} \left( 1 - e^{-\frac{(1-d)RT}{L}} \right)$$

$$I_{\max} = \frac{V - E}{R} \left( 1 - e^{-\frac{dRT}{L}} \right) + I_{\min} e^{-\frac{dRT}{L}}$$

From the above equations, we get:

$$I_{\max} = \frac{V}{R} \left( \frac{1 - e^{-\frac{dRT}{L}}}{1 - e^{-\frac{RT}{L}}} \right) - \frac{E}{R}$$

$$I_{\min} = \frac{V}{R} \left( \frac{e^{\frac{dRT}{L}} - 1}{e^{\frac{RT}{L}} - 1} \right) - \frac{E}{R}$$

Steady state ripple =  $I_{\max} - I_{\min}$

Peak-to-peak ripple current:  $\Delta I = I_{\max} - I_{\min}$

Average output voltage:  $V_{dc} = dV$

Average output current:  $I_{dc(approx)} = \frac{I_{\max} + I_{\min}}{2}$

**Example 1** A Chopper circuit is operating on TRC at a frequency of 2 kHz on a 460 V supply. If the load voltage is 350 volts, calculate the conduction period of the thyristor in each cycle.

**Solution:**

$$\text{Total time period of chopper} \Rightarrow T = \frac{1}{f} = \frac{1}{2 \times 10^3} = 0.5 \text{ msec}$$

$$V_{dc} = Vd = V \left( \frac{t_{ON}}{T} \right)$$

$$\therefore \text{Conduction period} \Rightarrow t_{ON} = \frac{T \times V_{dc}}{V} = \frac{0.5 \times 10^{-3} \times 350}{460} = 0.38 \text{ msec}$$

**Example 2** A dc chopper has a resistive load of  $20\Omega$  and input voltage  $V_s = 220\text{V}$ . When the chopper is ON, its voltage drop is 1.5 volts and chopping frequency is 10 kHz. If the duty cycle is 80%, determine the average output voltage and the chopper ON time.

**Solution:**

$$V_s = 220\text{V}, R = 20\Omega, f = 10 \text{ kHz}, d = \frac{t_{ON}}{T} = 0.80$$

$$\text{Voltage drop across chopper} \Rightarrow V_{ch} = 1.5 \text{ V}$$

$$\text{Average output voltage} \Rightarrow V_{dc} = \left( \frac{t_{ON}}{T} \right) (V_s - V_{ch}) = 0.80(220 - 1.5) = 174.8 \text{ V}$$

$$\text{Chopping period} \Rightarrow T_{\text{usec}} = \frac{1}{f} = \frac{1}{10 \times 10^3} = 100$$

$$\text{Chopper ON time} \Rightarrow t_{ON} = dT = 0.80 \times 100 \times 10^{-6} = 80 \text{ usec}$$

**Example 3** A battery powered vehicle uses dc motor drive controlled by DC chopper working at 10 kHz. The battery voltage is 220 V, the min. turn ON and OFF times of the chopper switch are 2μsec and 25μsec, respectively. Determine the min. and max. dc voltage that the chopper can deliver to the motor.

**Solution:**

$$\text{Total time period of chopper} \Rightarrow T = \frac{1}{f} = \frac{1}{10 \times 10^3} = 100 \mu \text{ sec}$$

$$\text{Min. ON time} = 2 \mu \text{ sec}$$

$$\text{Min. duty cycle } d_{\min} = \frac{t_{ON(\min)}}{T} = \frac{2 \mu \text{ sec}}{100 \mu \text{ sec}} = 0.02$$

$$\therefore V_{dc(\min)} = d_{\min} \times V_S = 0.02 \times 220 = 4.4 \text{ V}$$

$$\text{Max. ON time} = T - t_{OFF} = 100 \mu \text{ sec} - 25 \mu \text{ sec} = 75 \mu \text{ sec}$$


$$d_{\max} = \frac{t_{ON(\max)}}{T} = \frac{75 \mu \text{ sec}}{100 \mu \text{ sec}} = 0.75$$

$$\therefore V_{dc(\max)} = d_{\max} \times V_S = 0.75 \times 220 = 165 \text{ V}$$

$$\text{The output range of control is: } 4.4 \text{ V} \leq V_{dc} \leq 165 \text{ V}$$



# Principle of Step-Up Chopper

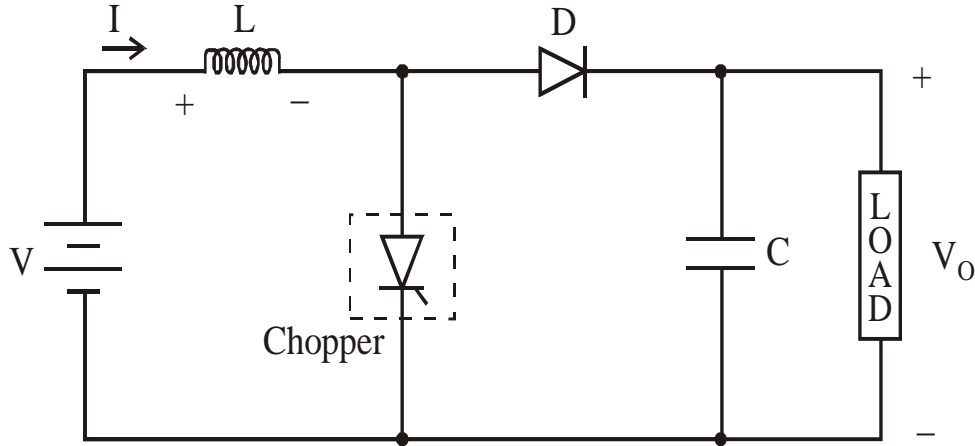

- ❑ A large  $C$  connected across the load to provide continuous  $V_o$ .
- ❑  $D$  prevents any current flow from  $C$  to the source.
- ❑ Step-Up choppers are used for regenerative braking of DC motors.

- Step-up chopper is used to obtain a load voltage  $V_o$  higher than the input voltage  $V$ .
- $L$  and  $C$  are chosen depending upon the requirement of output voltage and current.
- When the chopper is ON, the inductor  $L$  is connected across the supply and its current  $I$  rises.  $L$  stores energy during the ON time of the chopper  $t_{ON}$ .
- When the chopper is OFF, inductor current  $I$  is forced to flow through  $D$  and load for a period,  $t_{OFF}$ .
- The current tends to decrease resulting in reversing the polarity of induced EMF in  $L$ . Therefore voltage across load is given by:

$$\boxed{V_o = V + L \frac{dI}{dt}} \Rightarrow \text{which means that } V_o > V$$

# Expression for Output Voltage

Assume average current of  $L$  is  $I$  during ON and OFF time of chopper.

When the chopper is ON:

Voltage across  $L = V \Rightarrow$  Energy stored in  $L = VIt_{ON}$

When the chopper is OFF: (energy is supplied by  $L$  to the load)

Voltage across  $L = V_o - V \Rightarrow$  Energy supplied by  $L = (V_o - V)It_{OFF}$

Neglecting losses,

Energy stored in  $L =$  Energy supplied by  $L$

$$\therefore VIt_{ON} = (V_o - V)It_{OFF} \Rightarrow V_o = \frac{V(t_{ON} + t_{OFF})}{t_{OFF}} \Rightarrow V_o = V \left( \frac{T}{T - t_{ON}} \right)$$

where  $T = t_{ON} + t_{OFF}$  is the chopping (switching) period.

$$\therefore V_o = V \left( \frac{1}{1 - (t_{ON}/T)} \right) \Rightarrow V_o = V \left( \frac{1}{1 - d} \right)$$

where  $d = t_{ON}/T =$  duty cycle

For  $0 < d < 1 \Rightarrow$  the output voltage will vary in the range  $V < V_o < \infty$

**Example 4** For step-up chopper, the input is 200V and the required output is 600V. If the conducting time of the thyristor is 200  $\mu$ sec, 1) compute the chopping frequency. 2) If the pulse width is halved for constant frequency of operation, find the new output voltage.

**Solution:**

$$V = 200 \text{ V}, t_{ON} = 200 \mu s, V_{dc} = 600 \text{ V}$$

$$1) \quad V_{dc} = V \left( \frac{T}{T - t_{ON}} \right) \Rightarrow 600 = 200 \left( \frac{T}{T - 200 \times 10^{-6}} \right) \Rightarrow T = 300 \mu s$$

$$2) \quad \text{Chopping frequency } f = \frac{1}{T} = \frac{1}{300 \times 10^{-6}} = 3.33 \text{ KHz}$$

$$\text{Pulse width is halved} \Rightarrow t_{ON} = \frac{200 \times 10^{-6}}{2} = 100 \mu s$$

$$\therefore \text{Output voltage} = V \left( \frac{T}{T - t_{ON}} \right) = 200 \left( \frac{300 \times 10^{-6}}{(300 - 100) \times 10^{-6}} \right) = 300 \text{ V}$$

---


## Classification of Choppers

- ☐ Class A chopper.
- ☐ Class B chopper.
- ☐ Class C chopper.
- ☐ Class D chopper.
- ☐ Class E chopper.
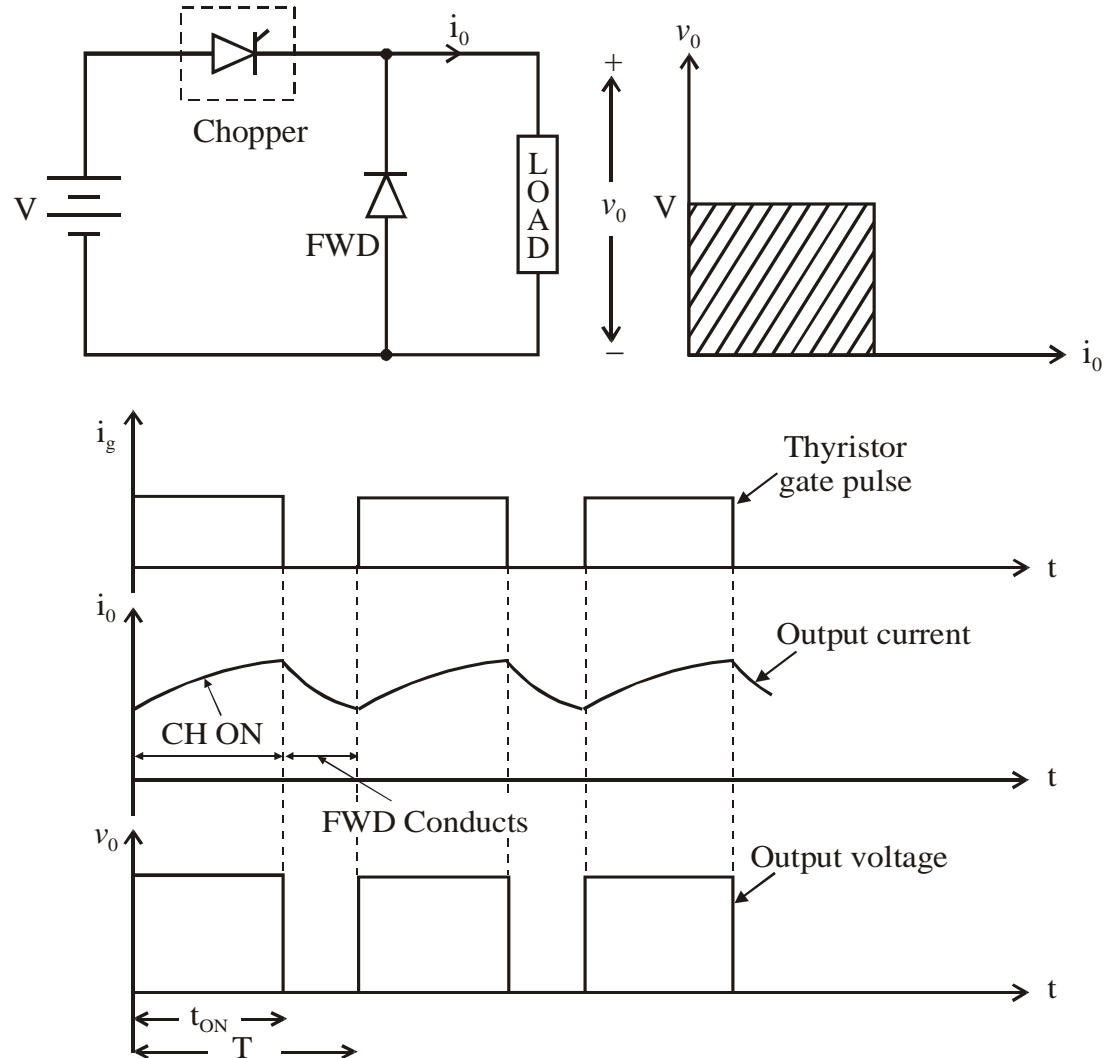
# Class A chopper

It is a step-down (first quadrant) chopper in which the power flows from the source to the load, and used DC motor speed control.


- When chopper is ON, supply voltage  $V$  is connected across the load.
- When chopper is OFF,  $V_o = 0$  and the load current continues to flow in the same direction through the FWD.
- The average values of output voltage and current are always positive.
- The output current equations obtained in step-down chopper with  $RL$  load can be used to study the performance of Class A Chopper.


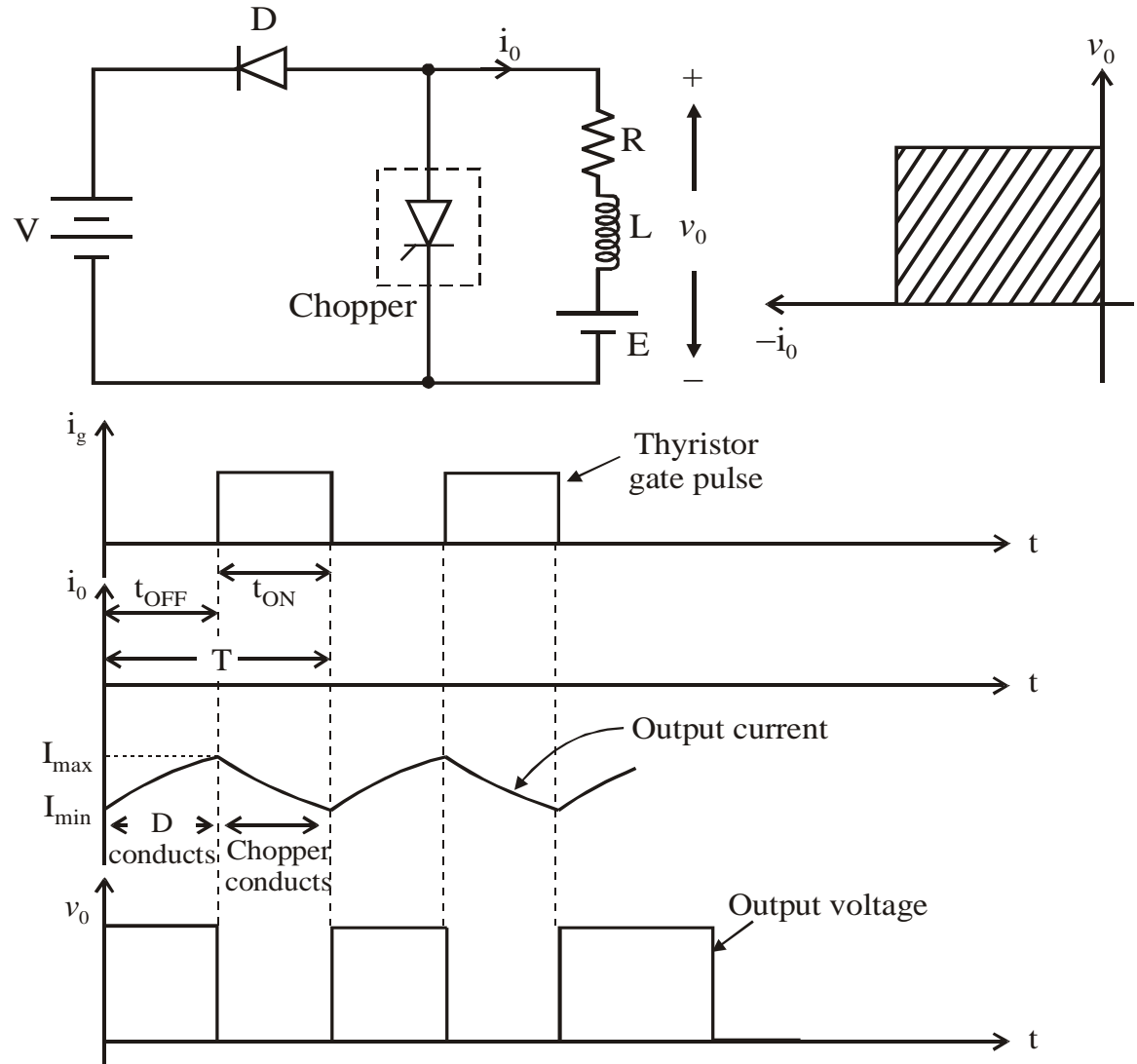
## Class B chopper

It is a step-up (second quadrant) chopper in which the power flows from the load to the source, and used for regenerative braking of DC motors.


- When chopper is ON,  $E$  drives current through  $L$  and  $R$  in a direction opposite to that shown in figure.
- During the ON period,  $L$  stores energy.
- When chopper is OFF,  $D$  conducts and part of the energy stored in  $L$  is returned to the supply.
- Average output voltage is positive.
- Average output current is negative.


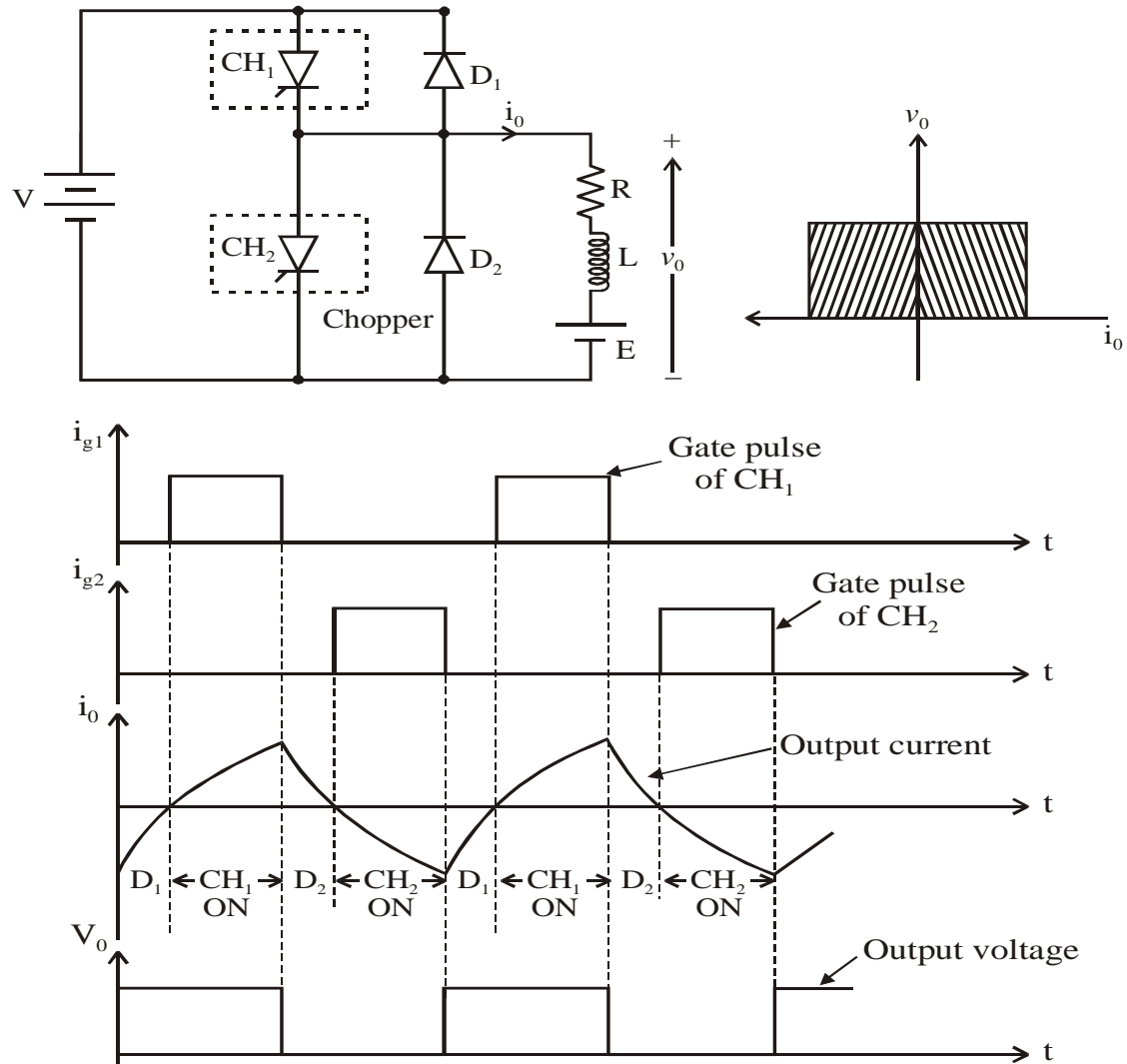
# Class C chopper




It is a combination of class A and B choppers (step-up/step-down) and used for DC motors speed control and regenerative braking.

- For first quadrant operation,  $CH_1$  is ON or  $D_2$  conducts.
- For second quadrant operation,  $CH_2$  is ON or  $D_1$  conducts.
- When  $CH_1$  is ON, load current is positive, output voltage equals  $V$ , and the load receives power from the source.
- When  $CH_1$  is OFF, energy stored in  $L$  forces current to flow through  $D_2$ , output voltage is zero, and load current is positive.
- When  $CH_2$  is triggered,  $E$  forces current to flow in opposite direction through  $L$  and  $CH_2$ . The output voltage is zero.
- On turning OFF  $CH_2$ , the energy stored in  $L$  drives current through  $D_1$  and the supply. Output voltage is  $V$ , the input current becomes negative, and power flows from the load to the source.
- Average output voltage is positive.
- Average output current can take both positive and negative values.
- Choppers  $CH_1$  &  $CH_2$  should not be turned ON simultaneously as it would result in short circuiting the supply.



**Class D chopper** It is a two quadrant operation chopper where the current is always positive but the load voltage can be positive or negative.



- When both  $CH_1$  and  $CH_2$  are triggered simultaneously, the output voltage  $v_o = V$  and output current flows through the load.
- When  $CH_1$  and  $CH_2$  are OFF, load current continues to flow in same direction through load,  $D_1$  and  $D_2$ , due to the energy stored  $L$ . Output voltage  $v_o = -V$ .
- Average load voltage is positive if  $t_{ON} > t_{OFF}$
- Average output voltage becomes negative if  $t_{ON} < t_{OFF}$ .

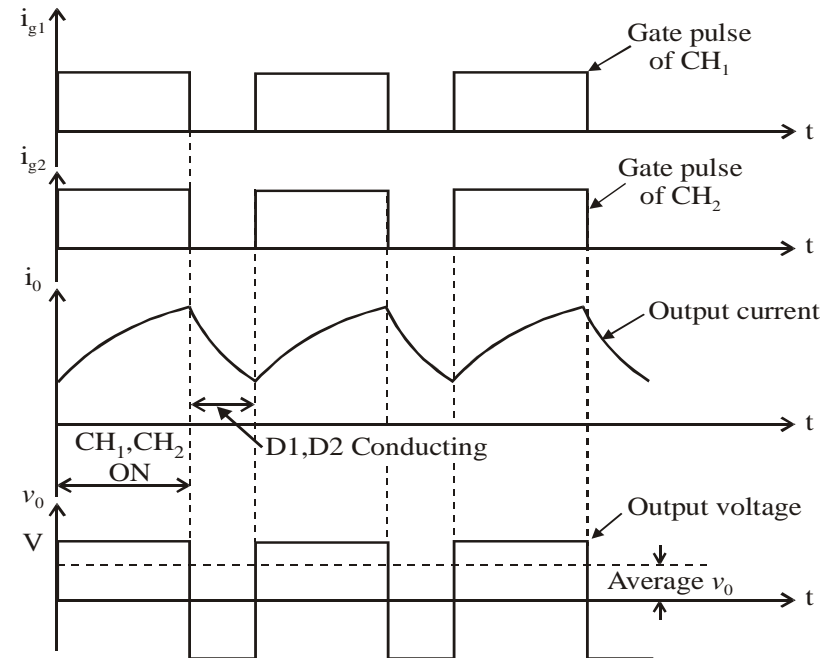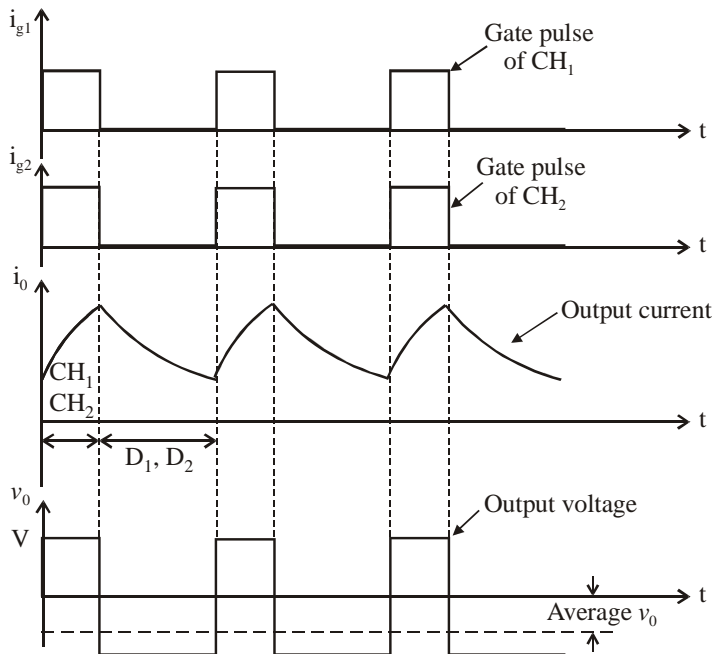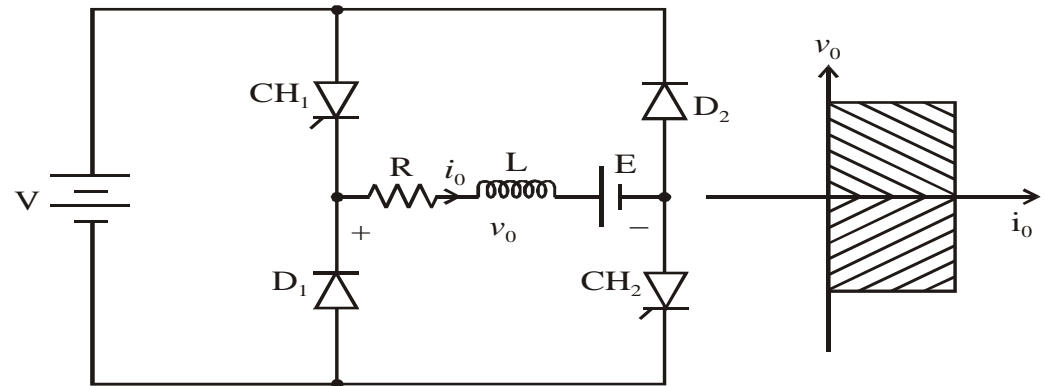
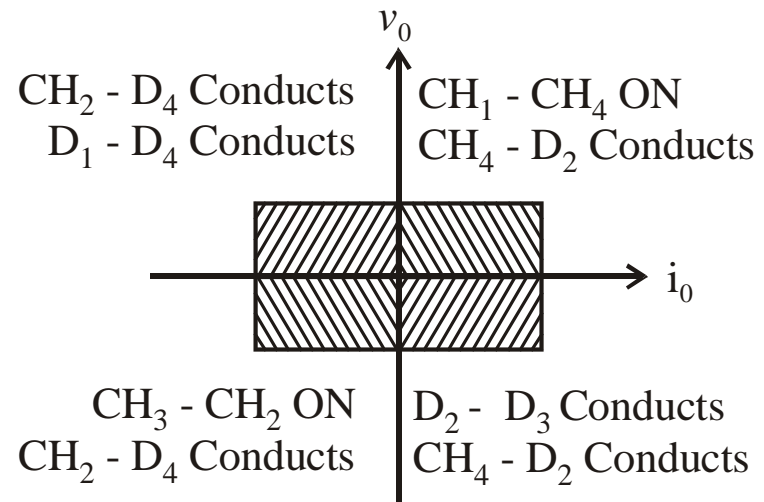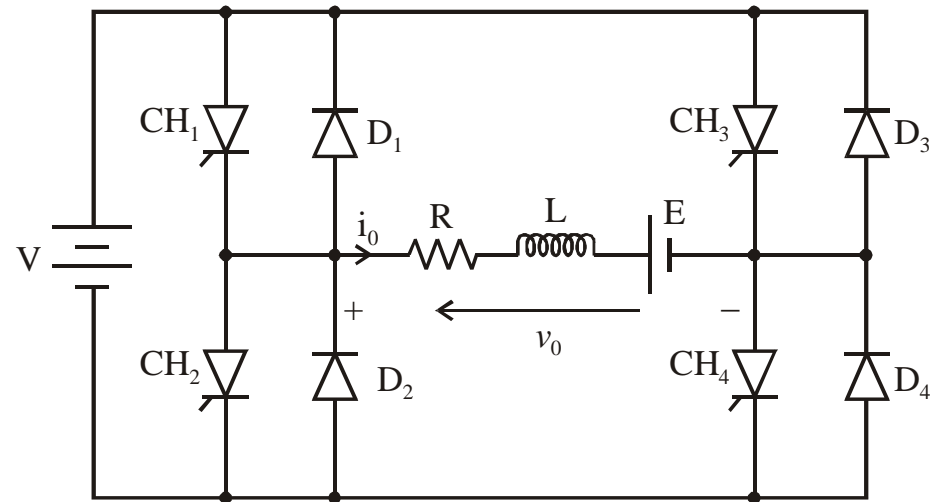
## Class E chopper

It is a four quadrant operation chopper where the load current and voltage can be positive or negative.

- When  $CH_1$  and  $CH_4$  are triggered, output current  $i_o$  flows in positive direction through  $CH_1$  and  $CH_4$ , with output voltage  $v_o = V$ . This gives the first quadrant operation.
- When both  $CH_1$  and  $CH_4$  are OFF, the energy stored in  $L$  drives  $i_o$  through  $D_2$  and  $D_3$  in the same direction, but output voltage  $v_o = -V$ . Therefore the chopper operates in the fourth quadrant.
- When  $CH_2$  and  $CH_3$  are triggered, the load current  $i_o$  flows in opposite direction and output voltage  $v_o = -V$ . Since both  $i_o$  and  $v_o$  are negative, the chopper operates in third quadrant.
- When both  $CH_2$  and  $CH_3$  are OFF, the load current  $i_o$  continues to flow in the same direction  $D_1$  and  $D_4$  and the output voltage  $v_o = V$ . Therefore the chopper operates in second quadrant as  $v_o$  is positive but  $i_o$  is negative.






# Problems and Solutions

## Question 1

For the given dc chopper with resistive load  $R = 10\Omega$  and input voltage  $V = 200$  V. When the chopper is ON, its voltage drop is 2 V and chopping frequency is 1 kHz. If the duty cycle is 60%, determine 1) average output voltage, 2) RMS value of output voltage, 3) effective input resistance of the chopper, and 4) chopper efficiency.

### Solution:

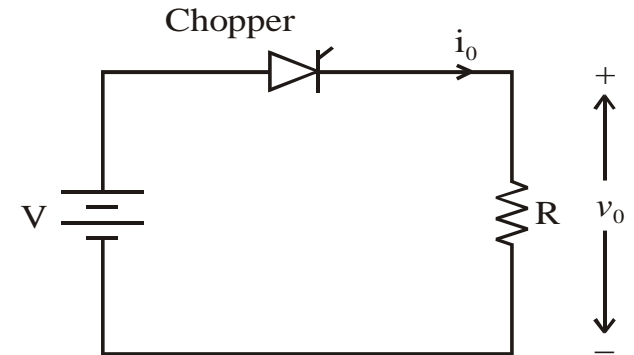

$$1) \quad V_{dc} = d(V - V_{ch}) = 0.60(200 - 2) = 118.8 \text{ V}$$

$$2) \quad \text{RMS of } V_o = \sqrt{d} (V - V_{ch}) = \sqrt{0.6} (200 - 2) = 153.3 \text{ V}$$

$$3) \quad I_{dc} = \frac{V_{dc}}{R} = \frac{118.8}{10} = 11.88 \text{ A} \Rightarrow R_i = \frac{V}{I_{dc}} = \frac{200}{11.88} = 16.83\Omega$$

$$4) \quad P_o = \frac{1}{T} \int_0^T \frac{v_o^2}{R} dt = \frac{1}{T} \int_0^T \frac{(V - V_{ch})^2}{R} dt = \frac{d(V - V_{ch})^2}{R} = \frac{0.6(200 - 2)^2}{10} = 2352 \text{ W}$$

$$P_i = \frac{1}{T} \int_0^T V i_o dt = \frac{1}{T} \int_0^T \frac{V(V - V_{ch})}{R} dt = \frac{dV(V - V_{ch})}{R} = \frac{0.6 \times 200(200 - 2)}{10} = 2376 \text{ W}$$

$$\text{Chopper efficiency} \Rightarrow \eta = \frac{P_o}{P_i} \times 100 = \frac{2352}{2376} \times 100 = 99\%$$

### Question 2

In a dc chopper, the average load current is 30 A, chopping frequency is 250 Hz, supply voltage is 110 V. Calculate the ON and OFF periods of the chopper if the load resistance is  $2\Omega$ .

#### Solution:

$$T = 1/f = 1/250 = 4 \times 10^{-3} = 4 \text{ msec}$$

$$I_{dc} = \frac{V_{dc}}{R} = \frac{dV}{R} \Rightarrow d = \frac{I_{dc}R}{V} = \frac{30 \times 2}{110} = 0.545$$

$$\text{Chopper ON period} \Rightarrow t_{ON} = dT = 0.545 \times 4 \times 10^{-3} = 2.18 \text{ msec}$$

$$\text{Chopper OFF period} \Rightarrow t_{OFF} = T - t_{ON} = 4 \times 10^{-3} - 2.18 \times 10^{-3} = 1.82 \text{ msec}$$

### Question 3

A chopper is supplying an inductive load with a free-wheeling diode. The load inductance is 5 H and resistance is  $10\Omega$ . The input voltage to the chopper is 200 volts and the chopper is operating at  $f=1\text{kHz}$ . If the ON/OFF time ratio is 2:3. Calculate:

- 1) Maximum and Minimum values of load current in one cycle of the chopper.
- 2) Average load current.

#### Solution:

$$1) \quad L = 5 \text{ H}, \quad R = 10\Omega, \quad f = 1 \text{ kHz}, \quad V = 200\text{V}, \quad t_{ON} : t_{OFF} = 2 : 3$$

$$\text{Chopping period} \Rightarrow T = 1/f = 1/1000 = 1 \text{ msec}$$

$$\frac{t_{ON}}{t_{OFF}} = \frac{2}{3} \Rightarrow t_{ON} = \frac{2}{3}t_{OFF}$$

$$T = t_{ON} + t_{OFF} = \frac{2}{3}t_{OFF} + t_{OFF} = \frac{5}{3}t_{OFF} \Rightarrow t_{OFF} = \frac{3}{5}T = \frac{3}{5} \times 1 \times 10^{-3} = 0.6 \text{ msec}$$

$$t_{ON} = T - t_{OFF} = (1 - 0.6) \times 10^{-3} = 0.4 \text{ msec}$$

$$\text{Duty cycle} \Rightarrow d = \frac{t_{ON}}{T} = \frac{0.4 \times 10^{-3}}{1 \times 10^{-3}} = 0.4$$

$$\text{Maximum load current:} \Rightarrow I_{\max} = \frac{V}{R} \left( \frac{1 - e^{-\frac{dRT}{L}}}{1 - e^{-\frac{RT}{L}}} \right) - \frac{E}{R}$$

Since there is no voltage source in the load circuit ( $E = 0$ ),

$$\therefore I_{\max} = \frac{200}{10} \left( \frac{1 - e^{-(0.4 \times 10 \times 1 \times 10^{-3})/5}}{1 - e^{-(10 \times 1 \times 10^{-3})/5}} \right) - \frac{0}{10} = 8.0047 \text{ A}$$

$$\text{Minimum load current with } E = 0 : \Rightarrow I_{\min} = \frac{V}{R} \left( \frac{e^{\frac{dRT}{L}} - 1}{e^{\frac{RT}{L}} - 1} \right)$$

$$\therefore I_{\min} = \frac{200}{10} \left( \frac{e^{(0.4 \times 10 \times 1 \times 10^{-3})/5} - 1}{e^{(10 \times 1 \times 10^{-3})/5} - 1} \right) = 7.995 \text{ A}$$

$$2) \quad \text{Average load current} \Rightarrow I_{dc} = \frac{I_{\max} + I_{\min}}{2} = \frac{8.0047 + 7.995}{2} \approx 8 \text{ A}$$

### Question 4

A chopper feeding on  $RL$  load is shown with  $V = 200$  V,  $R = 5\Omega$ ,  $L = 5$  mH,  $f = 1$  kHz,  $d = 0.5$  and  $E = 0$  V. Calculate : 1) Maximum and Minimum load currents, 2) average load current, and 3) effective input resistance.

### Solution:

1) Chopping period:  $T = \frac{1}{f} = \frac{1}{1 \times 10^3} = 1$  msec


Max. load current:  $I_{\max} = \frac{V}{R} \left( \frac{1 - e^{-\frac{dRT}{L}}}{1 - e^{-\frac{RT}{L}}} \right) - \frac{E}{R}$

$$I_{\max} = \frac{200}{5} \left( \frac{1 - e^{-(0.5 \times 5 \times 1 \times 10^3)/5 \times 10^{-3}}}{1 - e^{-(5 \times 1 \times 10^3)/5 \times 10^{-3}}} \right) - \frac{0}{5} = 24.9 \text{ A}$$

$$\text{Min. load current: } I_{\min} = \frac{V}{R} \left( \frac{e^{\frac{dRT}{L}} - 1}{e^{\frac{RT}{L}} - 1} \right) - \frac{E}{R} = \frac{200}{5} \left( \frac{e^{\frac{0.5 \times 5 \times 1 \times 10^3}{5 \times 10^{-3}}} - 1}{e^{\frac{5 \times 1 \times 10^3}{5 \times 10^{-3}}} - 1} \right) - \frac{0}{5} = 15.1 \text{ A}$$

2) Average load current:  $I_{dc} = \frac{I_{\max} + I_{\min}}{2} = \frac{24.9 + 15.1}{2} = 20 \text{ A}$

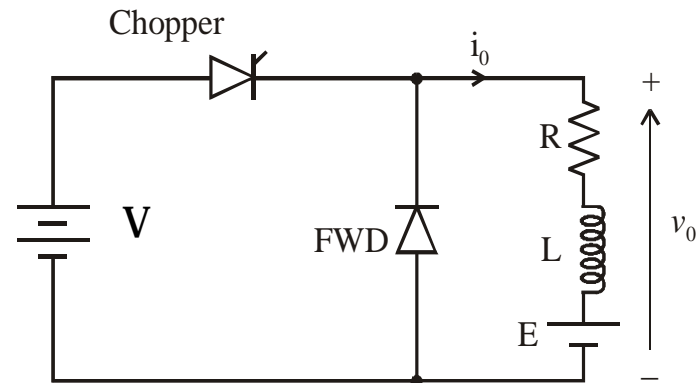3) Effective input resistance:  $R_i = \frac{V}{I_s} = \frac{V}{dI_{dc}} = \frac{200}{0.5 \times 20} = 20\Omega$



**Question 5** For the given first quadrant chopper, express the following variables as functions of  $V$ ,  $R$  and duty cycle  $d$  in case of resistive load:

- 1) Average output voltage and current, 2) Output current at the instant of commutation,
- 3) Average and RMS free wheeling diode current, 4) RMS value of output voltage, and
- 5) RMS and average thyristor currents.

**Solution:**

- 1) Average output voltage:

$$V_{dc} = \left( \frac{t_{ON}}{T} \right) V = dV$$


$$\text{Average output current: } I_{dc} = \frac{V_{dc}}{R} = \frac{dV}{R}$$

- 2) The thyristor is commutated at the instant  $t = t_{ON}$  and the output voltage is  $V$   
 $\therefore$  output current at the instant of commutation is  $\Rightarrow V / R$

- 3) Free wheeling diode (FWD) will never conduct in a resistive load.  
 $\therefore$  Average & RMS free wheeling diode currents are zero.

$$4) V_{O(RMS)} = \sqrt{\frac{1}{T} \int_0^{t_{ON}} v_o^2 dt} = \sqrt{\frac{1}{T} \int_0^{t_{ON}} V^2 dt} = \sqrt{V^2 \left( \frac{t_{ON}}{T} \right)} = \sqrt{dV}$$

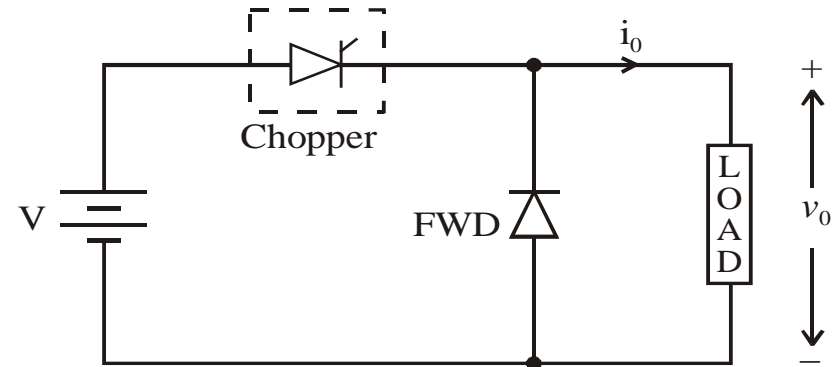- 5) RMS current of thyristor = RMS current of load  $= V_{O(RMS)} / R = \sqrt{dV} / R$   
 Average current of thyristor = Average current of load  $= dV / R$



**Question 6** In a 100V dc chopper drive, the max. value of accelerating current is 425A, the lower limit of current pulsation is 180 A , the length of ON and OFF period is 14msec and 11msec, respectively . Determine: 1) the limit of current pulsation, 2) the chopping frequency, 3) the duty cycle ratio, and 4) the output voltage.

**Solution:**

- 1) Limit of current pulsation = Max. current – Min. current =  $425 - 180 = 245 \text{ A}$
  - 2)  $T = (14 + 11) \text{ msec} = 25 \text{ msec} \Rightarrow f = 1/T = 1/(25 \times 10^{-3}) = 40 \text{ Hz}$
  - 3)  $d = t_{ON} / T = 14 \text{ msec} / 25 \text{ msec} = 0.56$
  - 4) Output voltage =  $dV = 0.56 \times 100 = 56 \text{ V}$
- 

**Question 7** Step-down dc chopper with  $100\Omega$  load. For 220V dc supply, calculate the average load current if the OFF period = 6msec and the chopping frequency is 100Hz.

**Solution:**

$$T = \frac{1}{f} = \frac{1}{100} = 10 \text{ msec}$$

$$t_{ON} = T - t_{OFF} = 10 \text{ msec} - 6 \text{ msec} = 4 \text{ msec}$$

$$d = t_{ON} / T = 4 \text{ msec} / 10 \text{ msec} = 0.4$$

$$I_{dc} = \frac{dV}{R} = \frac{0.4 \times 220}{100} = 0.88 \text{ A}$$

**Question 8**

A thyristor step-up chopper has the following data:  $V = 50\text{V}$ , chopping frequency =  $250\text{Hz}$ , and  $t_{\text{OFF}} = 2\text{msec}$ . Calculate  $V_o$ .

**Solution:**

$$T = 1/f = 1/250 = 4 \text{ msec}$$

$$V_o = V \frac{T}{T - t_{\text{ON}}} = V \frac{T}{t_{\text{OFF}}} = 50 \times \frac{4 \times 10^{-3}}{2 \times 10^{-3}} = 100\text{V}$$


---

**Question 9**

A step-down chopper is connected to  $60\text{V}$  dc supply and  $10\Omega$  resistive load. If the load voltage waveform has width of  $2\text{msec}$  from  $5\text{msec}$  periodic time, calculate :

1)  $I_{\text{dc}}$ , 2)  $R_{\text{in}}$ , and 3) Chopping frequency  $f$ .

**Solution:**

$$1) \quad I_{\text{dc}} = Vd/R = V (t_{\text{ON}}/T)/R = 60 \times (2 \times 10^{-3}/5 \times 10^{-3})/10 = 0.24\text{A}$$

$$2) \quad R_{\text{in}} = R/d = R/(t_{\text{ON}}/T) = 10/(2 \times 10^{-3}/5 \times 10^{-3}) = 25\Omega$$

$$3) \quad f = 1/T = 1/5 \times 10^{-3} = 200\text{Hz}$$


---

**Question 10**

A chopper circuit is operation on Time Ratio Control (TRC) principle at frequency  $f = 1\text{kHz}$  on a  $220\text{V}$  dc supply. If the load voltage is  $180\text{V}$ , calculate the conducting and blocking periods of the power device in each cycle.

**Solution:**

$$V_{\text{dc}} = Vd \Rightarrow 180 = 220 \times d \Rightarrow d = 0.8$$

$$t_{\text{ON}} = dT = d/f = 0.8/1 \times 10^3 = 0.8\text{msec}$$

$$t_{\text{OFF}} = T - t_{\text{ON}} = 1\text{msec} - 0.8\text{msec} = 0.2\text{msec}$$

## Question 11

Choose the correct answer for the following Questions

- 1) The average value of output voltage for step-up chopper is .....
- A.  $dV / (1-d)$     **B.  $V / (1-d)$**     C.  $dV$     D.  $(1-d)V$
- 
- 2) The duty ratio  $d$  is between .....
- A. 1 and  $\infty$     B.  $-1$  and  $+1$     **C. 0 and 1**    D.  $-1$  and 0
- 
- 3) DC to DC chopper operates from a 48V battery source into a resistive load of  $24\Omega$ . The frequency of the chopper is set to 250Hz. When chopper on-time is 1ms, the load power is .....
- A. 6W    B. 12W    **C. 24W**    D. 48W
- 
- 4) DC to DC chopper operates from a 48V source with a resistive load of  $24\Omega$ . The frequency of the chopper is 250Hz. When chopper on-time is 3ms, the RMS current is .....
- A. 1.5A    B. 15mA    **C. 1.73A**    D. 173mA



- 5) An ideal chopper is operating at a frequency of 500 Hz from a 60 V battery input. It is supplying a load having  $3\ \Omega$  resistance and 9 mH inductance. Assuming the load is shunted by a perfect commutating diode and assuming battery is low less, what is the mean load current at an on/off ratio of 1/1 ?
- (A) 10 A      (C) 20 A  
(B) 15 A      (D) None of the above
- 

- 6) A two-quadrant d.c. to d.c. chopper can operate with which of the following load conditions ?
1. +ve voltage, +ve current
  2. -ve voltage, +ve current
  3. -ve voltage, -ve current
- A. 1 only      B. 1 and 2      (C) 1 and 4      D. 3 and 4
- 

- 7) For a step up d.c.-d.c. chopper with an input d.c. voltage of 220 volts, if the output voltage required is 330 volts and the non-conducting time of thyristor-chopper is  $100\ \mu\text{s}$ , the ON time of thyristor-chopper would be
- A.  $66.6\ \mu\text{sec}$       B.  $100\ \mu\text{sec}$       (C)  $50\ \mu\text{sec}$       D.  $200\ \mu\text{sec}$




# Chapter 8

## DC-AC Inverters

# Inverters
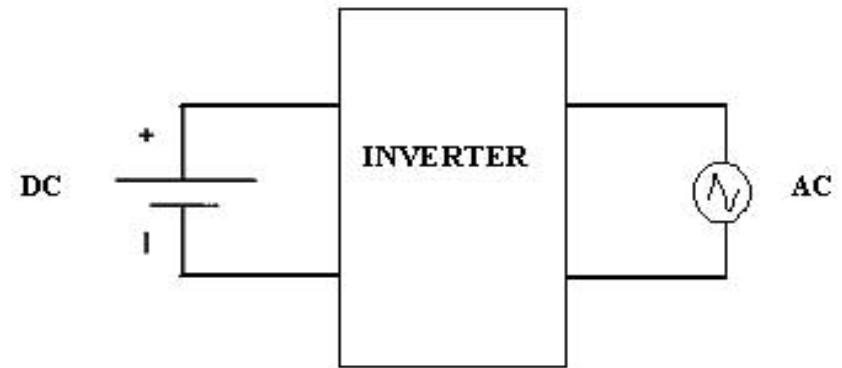
## (DC to AC Inverters)

- The converter that changes a DC to AC is called an inverter.
- Earlier inverters were built with SCR semiconductor devices.
- Since the circuitry to turn the SCR off is complex, other power devices such as BJT, MOSFETs, IGBT and MCTs.
- Currently SCRs are used in high power inverters (such as 500 kW or higher).
- Inverters are used in:
  - ❑ *Emergency lighting systems.*
  - ❑ *AC variable speed drives.*
  - ❑ *Uninterrupted power supplies UPS.*
  - ❑ *Frequency converters.*



# Types of Inverters

## ➤ Single Phase Inverters:


- ✓ Mini inverters.
- ✓ Parallel inverters.
- ✓ Series inverters.
- ✓ Bridge inverters.

## ➤ Three Phase Inverters:


- ✓ SCR bridge inverters.
- ✓ IGBT bridge inverters.

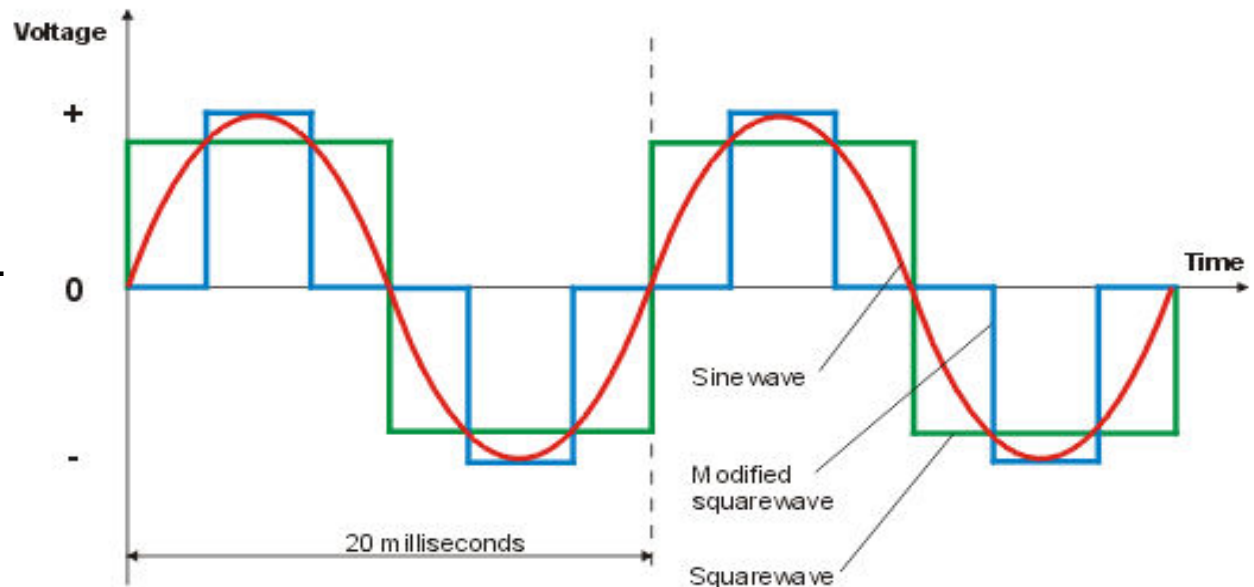**Not all inverters outputs are the same:**

- Square Wave.
- Modified Square Wave.
- Stepped Sine Wave.
- Pure Sine Wave.




## Mini Inverters

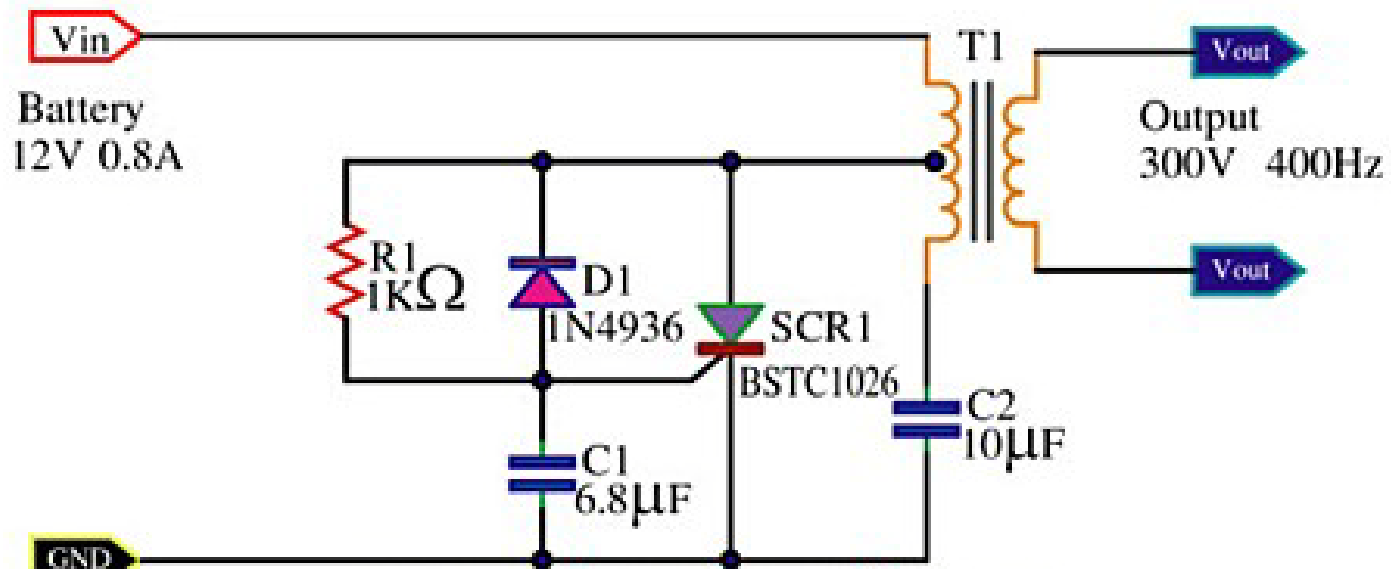

- The SCR provides 300 V of 400Hz from input voltage of 12V, 0.8A source.
- Drawback: it might latch in the conducting state if the load is too heavy or if there is a short circuit at the output. This requires some kind of protection.
- The transformer used is a 10W mains type with 6V+6V windings on the SCR side and a 110V+110V windings, in series, at the output.
- The efficiency is 50% and the ideal load is equivalent to a 22k resistor, 5W.
- The output waveform is vaguely sinusoidal at a frequency of 400Hz.

# Parallel Inverters

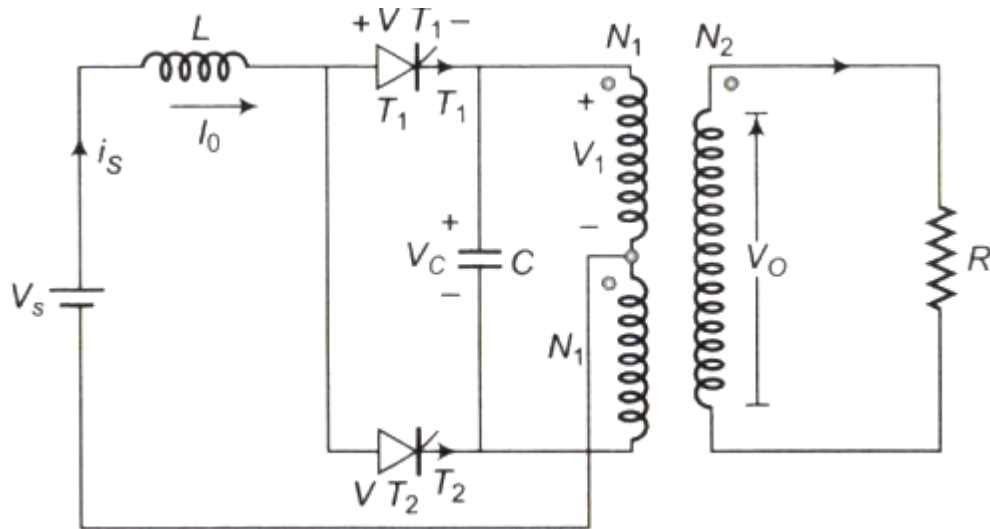

$$f_{\max} = \frac{n^2}{48CR}$$

$$\text{Transformer ratio: } n = \frac{N_2}{N_1} = \frac{V_o}{V_s}$$

$$t_{ON} = \frac{4CR}{n^2}; \quad t_{OFF} = \frac{Ln^2}{R}$$

$$0.25 < \frac{t_{ON}}{t_{OFF}} < 3.34$$

- The basic single phase parallel inverter circuit consists of two SCRs **T1** and **T2**, an inductor **L**, an output transformer and a commutating capacitor **C**.
- The function of **L** is to make the source current constant.
- During the work of this inverter, capacitor **C** comes in parallel with the load via the transformer (so it is called as a parallel inverter).


**Example 1** Design a single phase parallel inverter of maximum frequency  $f_{\max} = 400\text{Hz}$  using 12V battery to supply an AC load of [ 120W, 240V] .

**Solution:**

$$n = \frac{V_o}{V_s} = \frac{240}{12} = 20$$

$$P = \frac{(V_o)^2}{R} \Rightarrow 120 = \frac{240^2}{R}$$

$$\therefore R = 480\Omega$$

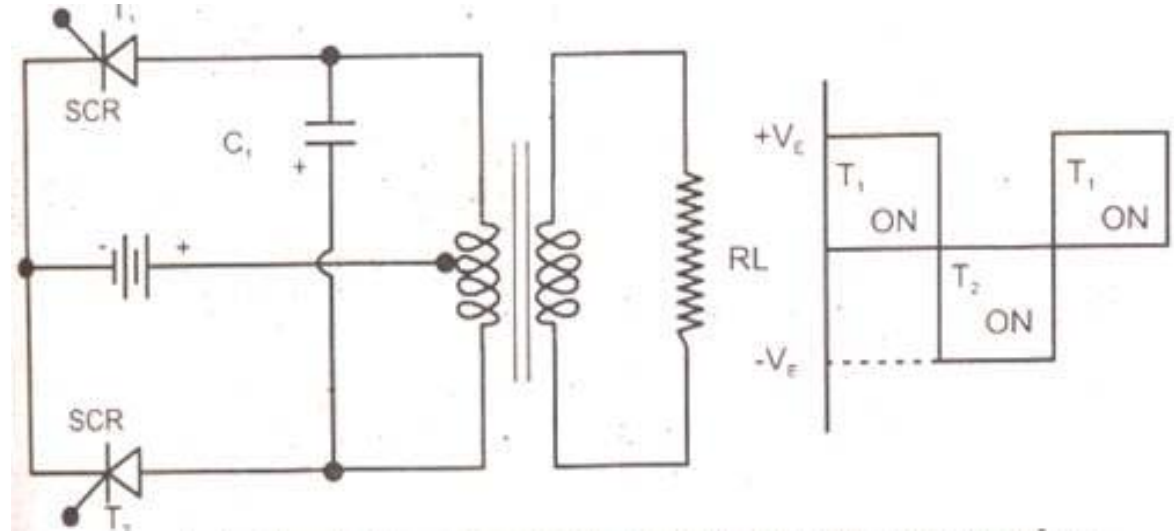

$$f_{\max} = \frac{n^2}{48CR} \Rightarrow 400 = \frac{20^2}{48 \times C \times 480} \Rightarrow C = 43\mu F$$

$$\text{Let: } \frac{t_{ON}}{t_{OFF}} = 3 \Rightarrow t_{ON} = 3t_{OFF}$$

$$\frac{4CR}{n^2} = 3 \frac{Ln^2}{R} \Rightarrow \frac{4 \times 43 \times 10^{-6} \times 480}{20^2} = 3 \frac{L \times 20^2}{480}$$

$$\therefore L = 90\mu H$$




# Series Inverters


$$f_r = \sqrt{\frac{1}{LC} - \frac{R^2}{4L}} \approx \sqrt{\frac{1}{LC}}$$

$$f_{out} = \frac{1}{(T/2) + t_{off}}$$

$$T = \frac{\pi}{f_r}$$

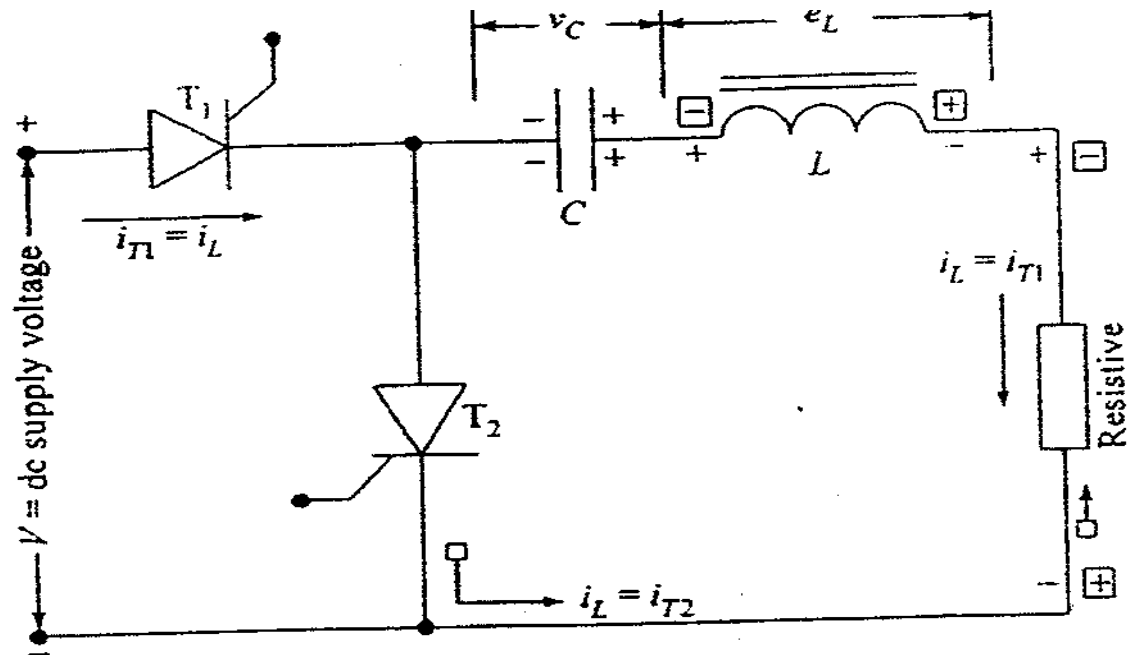

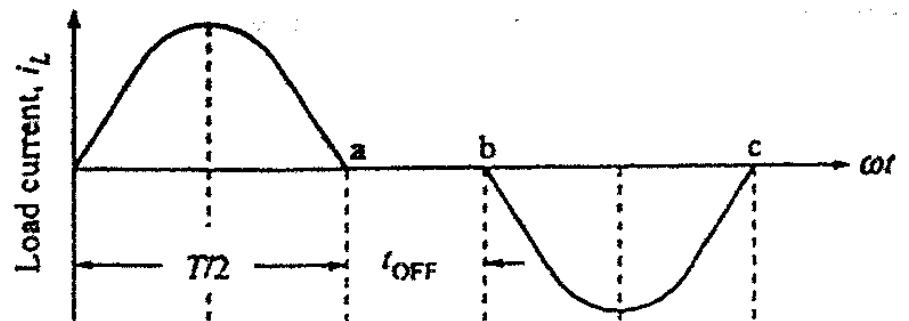+ , - polarities correspond to the load current  $i_L = i_{T1}$   
 ⊞ , ⊞ polarities correspond to the load current  $i_L = i_{T2}$   
 —→ Direction of the load current when  $T_1$  conducts  
 ⊞ —→ Direction of the load current when  $T_2$  conducts



### Example 2

For a series inverter of output frequency  $f_{\text{out}} = 50\text{Hz}$ , the time period between turn-off of one SCR and the turn-on of the other SCR is 0.012 sec. Find the resonant frequency ( $f_r$ ) and time period of oscillation ( $T$ ).

### Solution:

$$f_{\text{out}} = \frac{1}{(T/2) + t_{\text{off}}} \Rightarrow 50 = \frac{1}{(T/2) + 0.012} \Rightarrow T = 0.016\text{sec}$$

$$T = \frac{\pi}{f_r} \Rightarrow f_r = \frac{\pi}{T} = \frac{\pi}{0.016} = 196.3\text{ Hz}$$

---

### Example 3

For a series inverter operating under resonant frequency of  $f_r = 2\text{kHz}$ . Calculate the required capacitor value if the used inductance is 6 mH.


### Solution:

$$f_r = \frac{1}{\sqrt{LC}}$$


$$2000 = \frac{1}{\sqrt{6 \times 10^{-3} \times C}} \Rightarrow C = 0.416\mu\text{F}$$
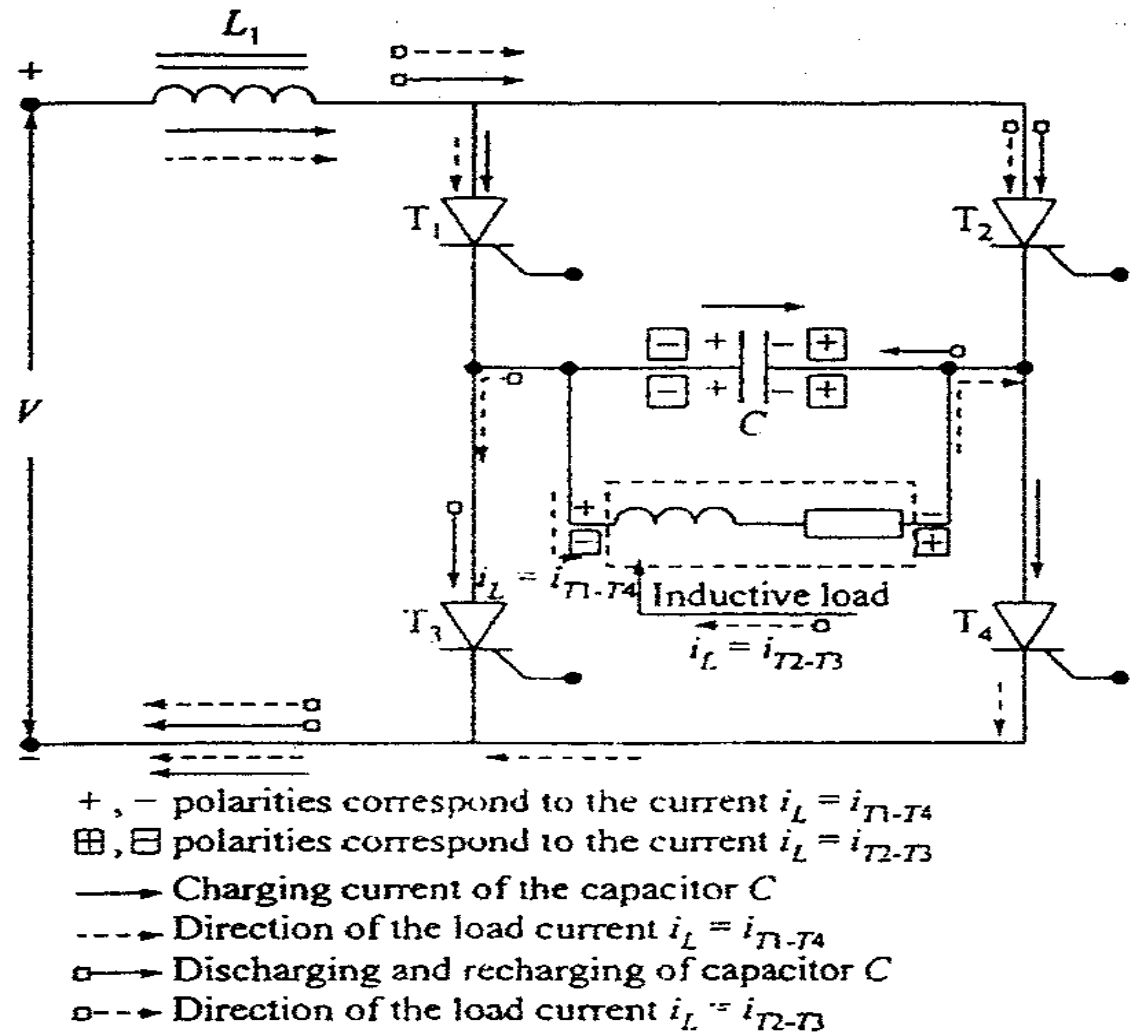
# Bridge Inverters

- The bridge inverters are current source inverters (**CSI**).
- Used in high frequency applications for induction heating and for solar cells power transfer.
- AC filters are required.



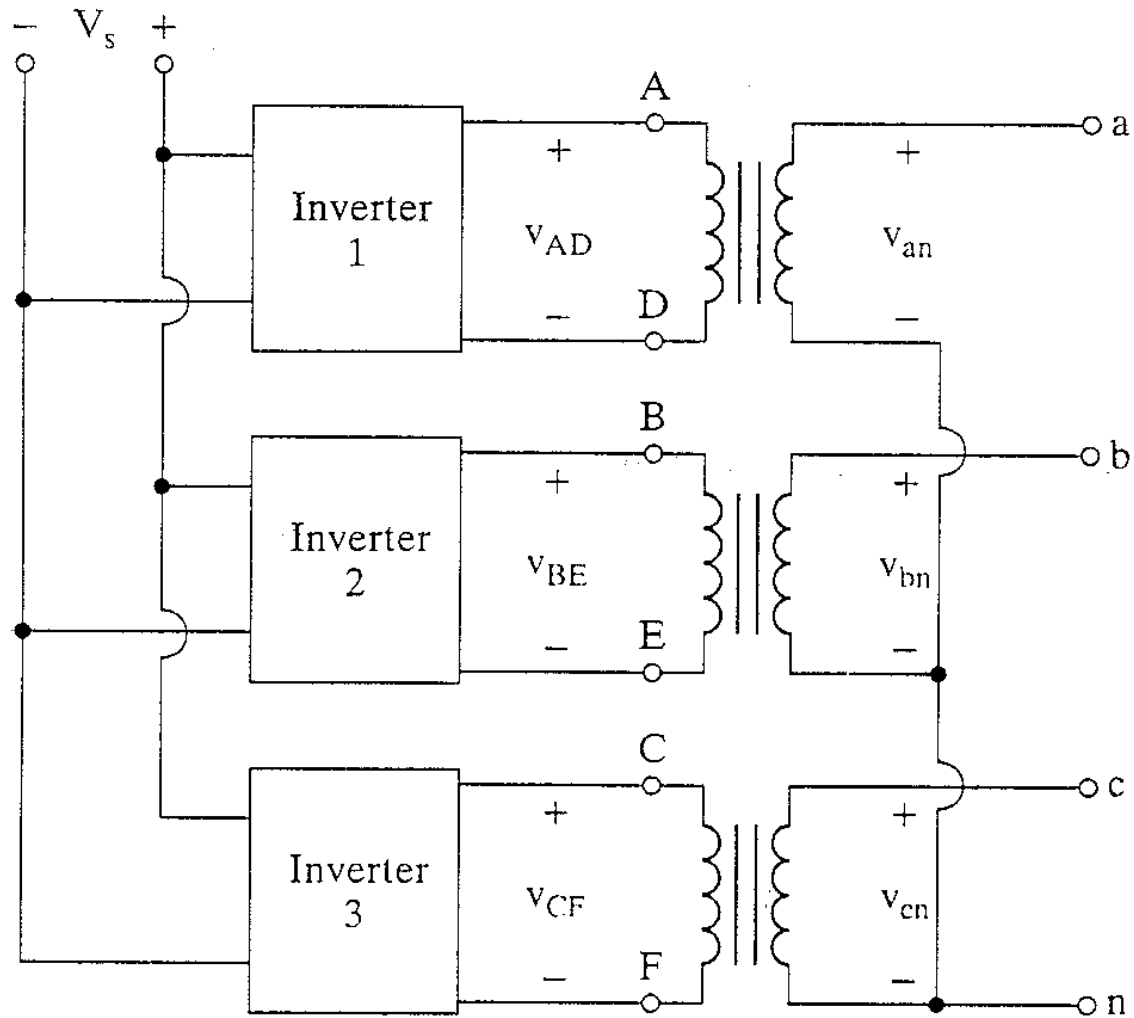
# Three Phase Voltage Source Inverters (VSI)




Three single-phase inverters in parallel, driven  $120^\circ$  apart

# ***Inverters Control***

## ➤ **Voltage Control:**

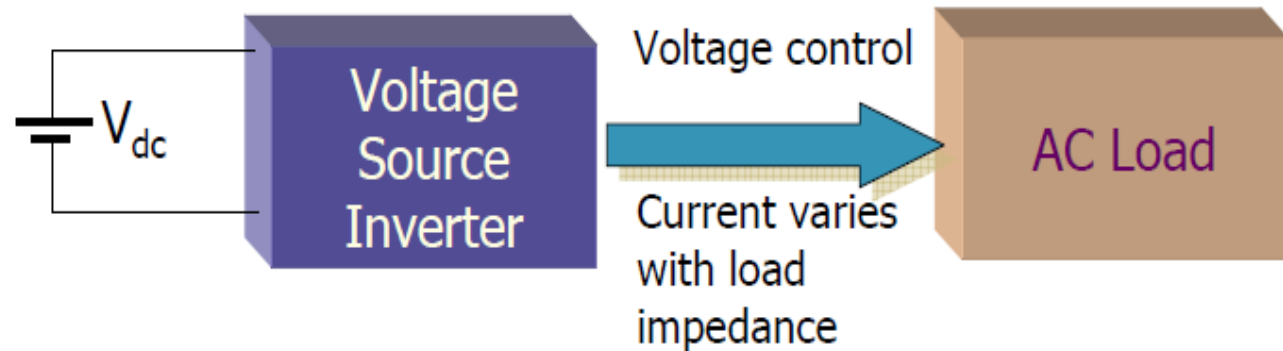

## ➤ **Current Control:**

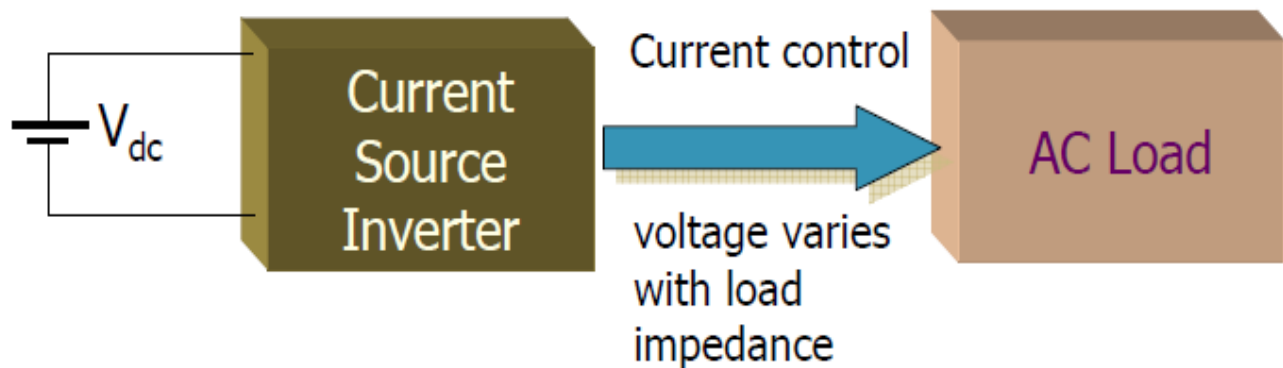

# ***Pulse Width Modulation (PWM) for VSI***


## ➤ **Objective of PWM:**

- ✓ Control of output voltage.
- ✓ Reduce harmonics.

## ➤ **Disadvantages of PWM:**


- ✓ Increase of switching losses due to high PWM frequency.
- ✓ Reduction of available voltage.
- ✓ EMI problems due to high order harmonics.

# AC Filters for Inverters

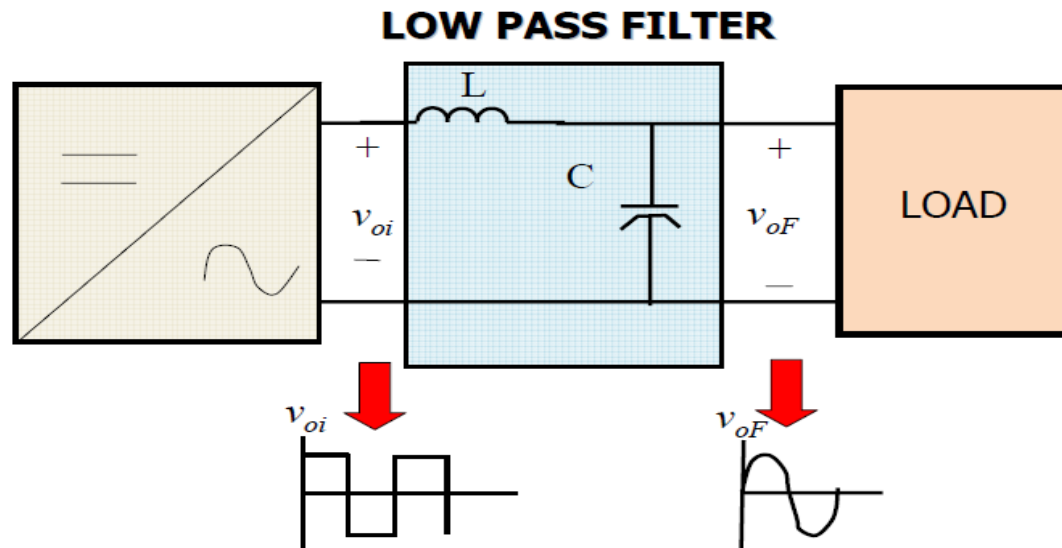


- ❑ Output of the inverter is “chopped AC voltage with zero DC component”. In some applications such as UPS, “*high purity*” sine wave output is required.
- ❑ An LC section low-pass filter is normally fitted at the inverter output to reduce the high frequency harmonics.
- ❑ In some applications such as AC motor drive, filtering is not required.


## ***Types of AC Filters***

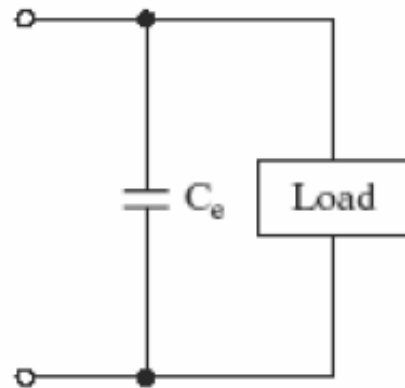

(a) C filter

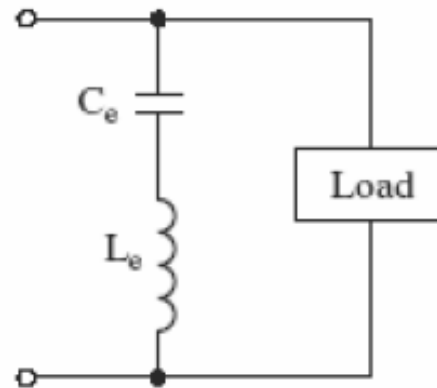

(b) CL filter

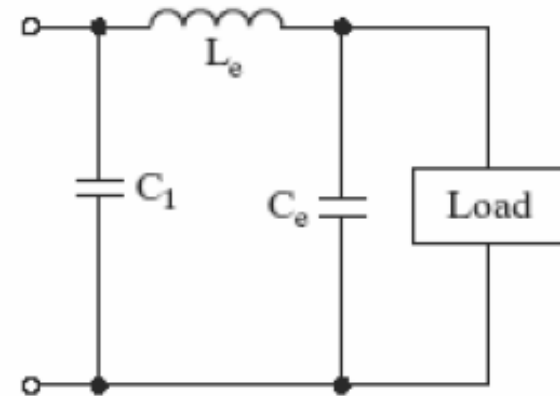

(c) CLC filter

C filter is very simple but draws more reactive power.

LC tuned filter can eliminate only one frequency.

CLC filter is more effective in reducing harmonics of wide bandwidth and draws less reactive power.




# Problems and Solutions

## Question 1

A single Phase parallel inverter has  $0.68\mu\text{F}$  commutation capacitor and  $500\Omega$  resistive load. If  $t_{\text{ON}}/t_{\text{OFF}} = 3$  and the centre-tap transformer has a turn ratio of  $n=12$ , calculate: 1) the maximum output frequency  $f_{\text{max}}$ , 2) find the value of  $L$  and draw the circuit diagram.

## Solution:

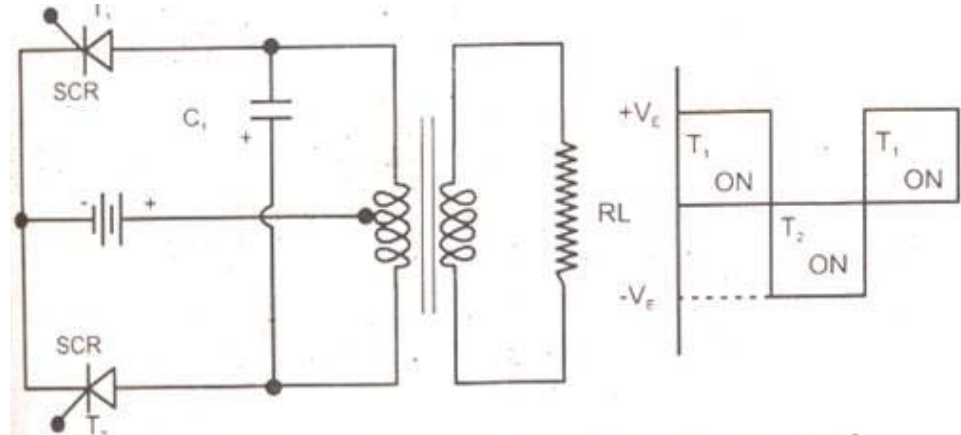

$$1) \quad f_{\text{max}} = \frac{n^2}{48RC} = \frac{12^2}{48 \times 500 \times 0.68 \times 10^{-6}} = 8.8\text{kHz}$$

$$2) \quad \frac{t_{\text{ON}}}{t_{\text{OFF}}} = 3 \Rightarrow t_{\text{ON}} = 3t_{\text{OFF}}$$

$$\frac{4RC}{n^2} = 3 \frac{Ln^2}{R} \Rightarrow \frac{4 \times 500 \times 0.68 \times 10^{-6}}{12^2} = 3 \frac{L \times 12^2}{500}$$

$$\therefore L = 11\mu\text{H}$$

**Question 2** Calculate the output frequency ( $f_{out}$ ) of a series inverter in which  $L=10\text{mH}$ ,  $C=2\mu\text{f}$ , and  $R=100\Omega$ . The time period between  $t_{OFF}$  of one SCR and  $t_{ON}$  of the other SCR is  $0.25\text{ms}$ . If the load resistance varies between  $100\Omega$  and  $75\Omega$ , find the output frequency range.

**Solution:**

$$f_r = \sqrt{\frac{1}{LC} - \frac{R^2}{4L}} = \sqrt{\frac{1}{10 \times 10^{-3} \times 2 \times 10^{-6}} - \frac{100^2}{4 \times 10 \times 10^{-3}}} = 500\text{Hz}$$

$$T = \frac{\pi}{f_r} = \frac{\pi}{500} = 6.28\text{m sec}$$

$$f_{out} = \frac{1}{(T/2) + t_{off}} = \frac{1}{(6.28 \times 10^{-3} / 2) + 0.25 \times 10^{-3}} = 290\text{Hz}$$

For  $R = 75\Omega$  we have:

$$f_r = \sqrt{\frac{1}{LC} - \frac{R^2}{4L}} = \sqrt{\frac{1}{10 \times 10^{-3} \times 2 \times 10^{-6}} - \frac{75^2}{4 \times 10 \times 10^{-3}}} = 600\text{Hz}$$

$$T = \frac{\pi}{f_r} = \frac{\pi}{600} = 5.23\text{m sec}$$

$$f_{out} = \frac{1}{(T/2) + t_{off}} = \frac{1}{(5.23 \times 10^{-3} / 2) + 0.25 \times 10^{-3}} = 350\text{Hz}$$

$\therefore$  The frequency range is:  $290\text{Hz} \leq f_{out} \leq 350\text{Hz}$

### Question 3 Choose the correct answer for the following Questions

1) An inverter is an electrical device that converts ..... currents.

- A. AC-DC    ☒ B. DC-AC    C. DC-DC    D. AC-AC
- 

2) The inverter performs the opposite function of the .....

- A. regulators    B. transformers    ☒ C. rectifiers    D. filters
- 

3) Static inverters are used in .....

- A. Induction heaters    B. Solar panels    C. UPS    ☒ D. All the above
- 

4) Inverters are classified according to their connections as .....

- A. Series inverters    B. Parallel inverters    C. Bridge inverters  
☒ D. All the above



# Chapter 9

## AC-AC Converters

# AC - AC Converters

- Used to convert the AC voltage to another AC voltage with waveforms of different amplitude, frequency, or phase.
- They can be single or three phase circuits.
- The AC-AC converters are classified as:
  - ❑ **AC Controllers (AC Regulators ):**
    - ✓ Two SCRs or TRIACs are used under natural commutation.
    - ✓ Output voltage has variable rms value with fixed or variable frequencies.
    - ✓ Used in light-dimmers and speed control of induction motors.
  - ❑ **Cycloconverters:**
    - ✓ Converts input power at one frequency to output power at different frequency with one-stage of conversion.
    - ✓ Cycloconverters are naturally commutated and no DC link is required.
    - ✓ Maximum output frequency is a fraction of the source frequency (up to  $f/3$ ).
    - ✓ Used in low speed ac motor drives for ranges of frequencies from 0 to 20 Hz.
    - ✓ Called also frequency changers (step-up or step-down).

# Types of AC Voltage Controllers

## ➤ Integral Cycle Control (On-Off Control):



- ✓ Load power is controlled by connecting the source for few cycles then disconnecting for another number of cycles, periodically.
- ✓ Suitable for systems with large time constants.
- ✓ Average load power can be varied from 0% through 100%.
- ✓ Used for heating loads and speed control.

## ➤ Phase Control:

- ✓ The SCRs are fired once every cycle and the firing angle can be delayed from the zero crossing.
- ✓ Only part of the voltage appears across the load providing voltage control.
- ✓ Load current appears in pulses and its zero crossing is used to turn-off the SCRs.
- ✓ Suitable for loads with short time constants.
- ✓ Firing instants of the SCRs are  $180^\circ$  apart, each occurs in its respective half cycle.
- ✓ By controlling the firing instant, the effective load voltage can be varied.
- ✓ Since the two SCRs having firing pulses delayed by  $180^\circ$ , the AC current pulses are periodic and symmetrical without DC current component.
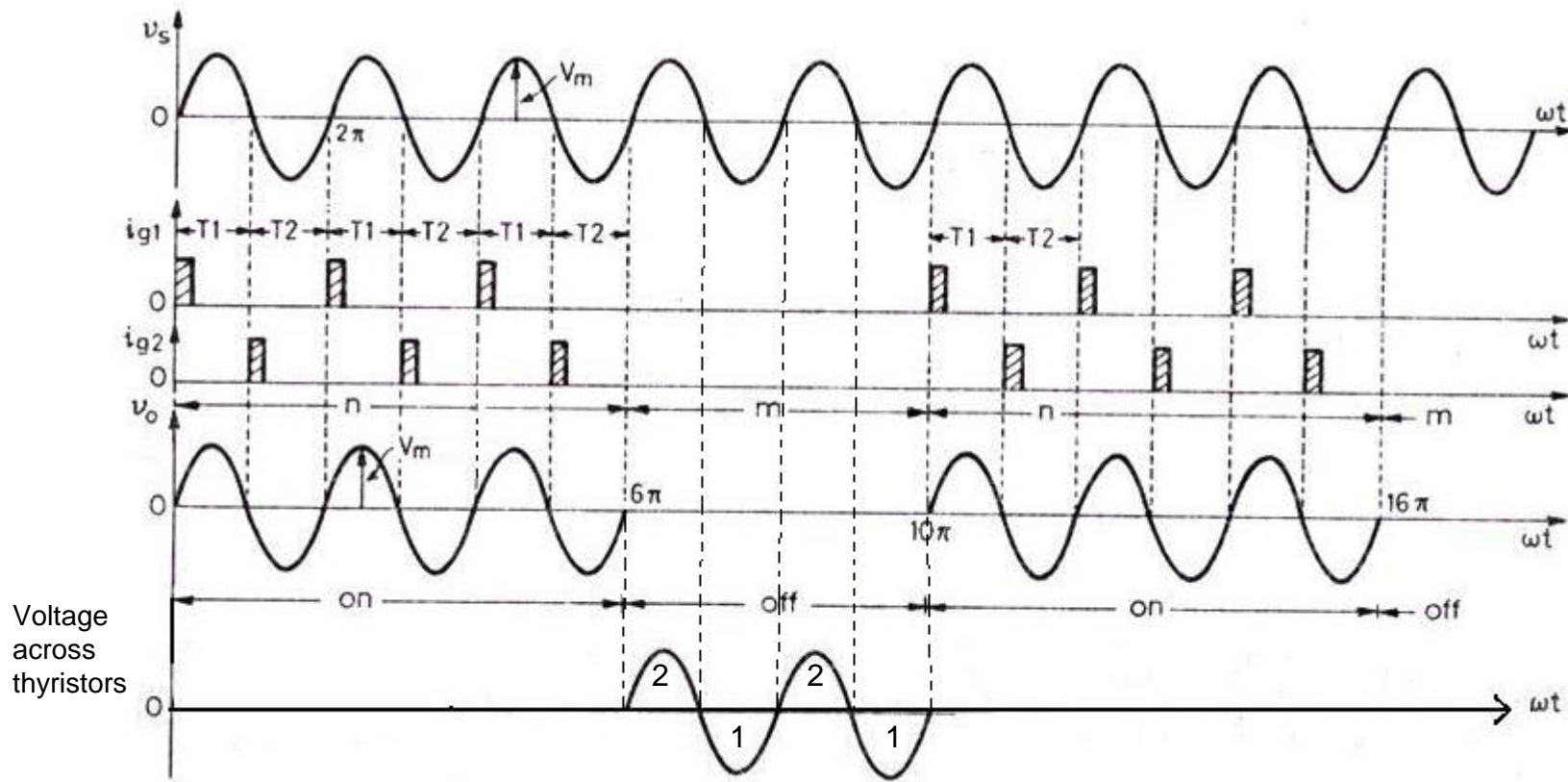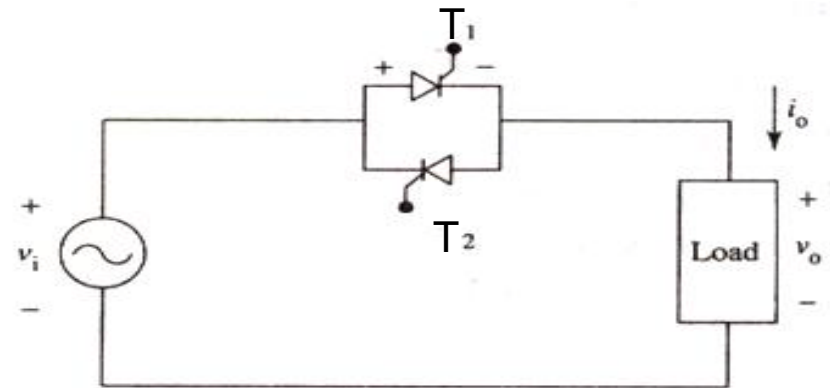
# Integral Cycle Control

Single Phase AC voltage  
Control with Resistive  
Load





The ratio of ON time to the total cycle time  $T$  controls the average load power as well as the rms output voltage.


$$\text{Duty cycle: } d = \frac{t_{ON}}{T}$$

$$\text{Average load power: } P_{O(avg)} = \frac{V_i^2 t_{ON}}{RT} = \frac{V_i^2 d}{R} = P_{O(max)} d$$

$$\text{RMS output voltage: } V_{O(rms)} = \frac{V_m}{\sqrt{2}} \sqrt{d} = V_i \sqrt{d}$$


$$\text{Power factor: } PF = \sqrt{d}$$

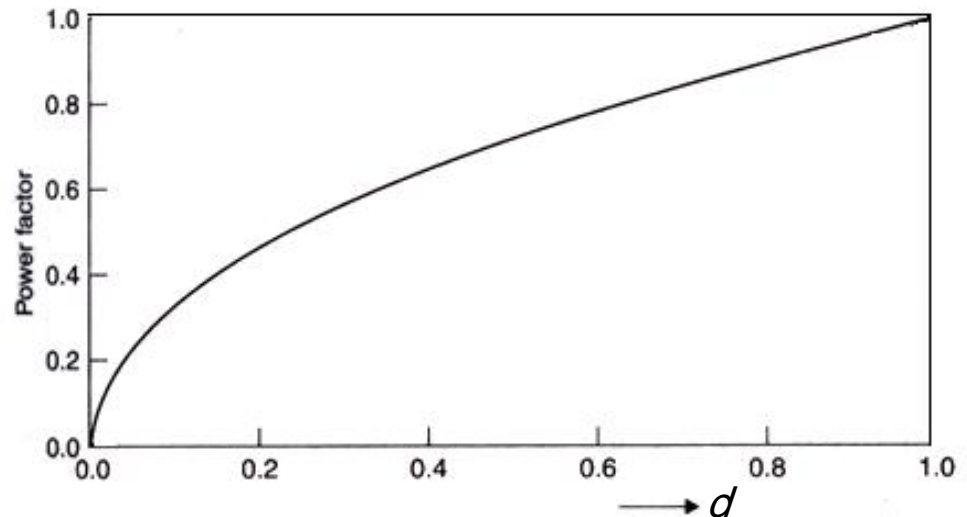- The Source current is always in time phase with source voltage.
- However, the integral cycle circuit does not operate at unity PF.
- For part of time, the source current is not present at all and therefore is not in phase with source voltage.



# Phase Control
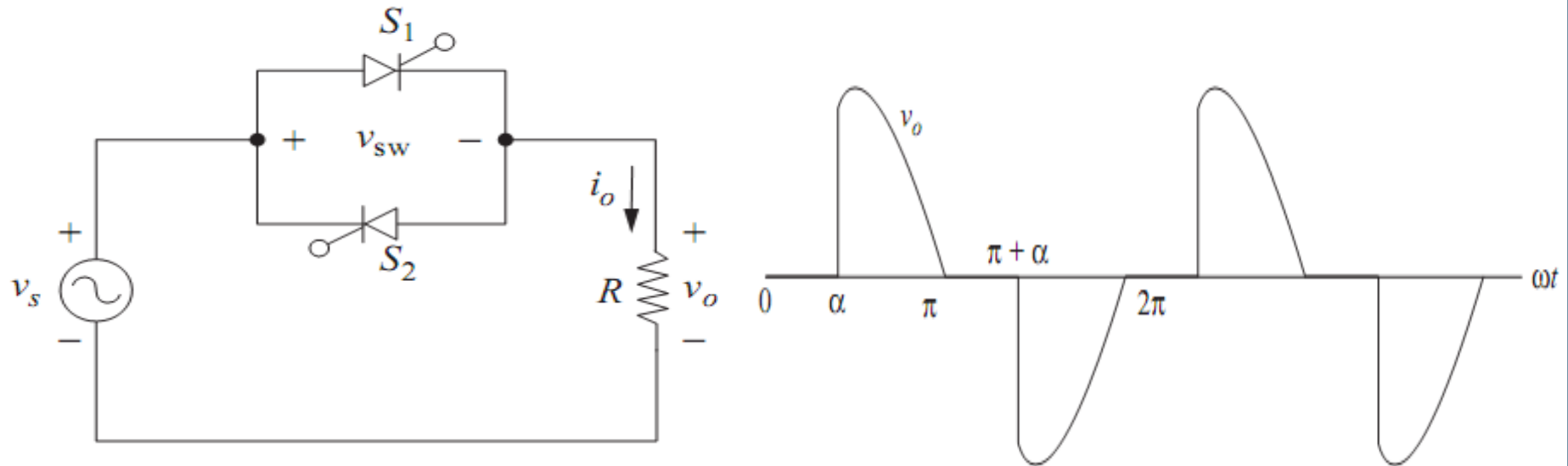
## Single Phase AC phase Control with Resistive Load



$$v_o(\omega t) = \begin{cases} V_m \sin \omega t & \text{for } \alpha < \omega t < \pi \text{ and } \alpha + \pi < \omega t < 2\pi \\ 0 & \text{otherwise} \end{cases}$$

$$V_{o,\text{rms}} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} [V_m \sin(\omega t)]^2 d(\omega t)} = \frac{V_m}{\sqrt{2}} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin(2\alpha)}{2\pi}}$$

$$I_{o,\text{rms}} = \frac{V_{o,\text{rms}}}{R}$$

$$I_{\text{SCR},\text{rms}} = \frac{I_{o,\text{rms}}}{\sqrt{2}}$$

$$\text{pf} = \frac{P}{S} = \frac{P}{V_{s,\text{rms}} I_{s,\text{rms}}} = \frac{V_{o,\text{rms}}^2 / R}{V_{s,\text{rms}} (V_{o,\text{rms}} / R)} = \frac{V_{o,\text{rms}}}{V_{s,\text{rms}}}$$

$$= \frac{\frac{V_m}{\sqrt{2}} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin(2\alpha)}{2\pi}}}{V_m / \sqrt{2}}$$

$$\text{pf} = \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin(2\alpha)}{2\pi}}$$

$$I_{\text{SCR},\text{avg}} = \frac{1}{2\pi} \int_{\alpha}^{\pi} \frac{V_m \sin(\omega t)}{R} d(\omega t) = \frac{V_m}{2\pi R} (1 + \cos \alpha)$$

### Example 1

TRIAC AC controller supplies an electrical furnace of  $8\Omega$  heating element with [240V , 50Hz] voltage supply and integral cycle control circuit that allows the current to flow for 2 cycles ON and one OFF cycle.

Calculate: 1) the average load power, and 2) the PF.

### Solution:

$$d = \frac{t_{ON}}{T} = \frac{t_{ON}}{t_{ON} + t_{OFF}} = \frac{2}{2+1} = \frac{2}{3}$$

$$1) \quad P_{O(avg)} = \frac{V_i^2 d}{R} = \frac{240^2 (2/3)}{8} = 4800 \text{ W}$$

$$2) \quad PF = \sqrt{d} = \sqrt{2/3} = 0.816$$

### Example 2

Thyristor AC Controllers with  $7\Omega$  resistive load is connected to ac voltage source  $V_{IN} = 350 \sin(315t)$ . If the conduction time of each thyristor is 2.5 msec, calculate the load power .

### Solution:

$$\theta_C = \omega t_C = 315 \times 2.5 \times 10^{-3} = 0.7875 \text{ rad} = 45^\circ$$

$$\alpha = 180 - \theta_C = 180^\circ - 45^\circ = 135^\circ; \quad V_m = 350 \text{ Volt}$$

$$V_{O(rms)} = \frac{V_m}{\sqrt{2}} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin(2\alpha)}{2\pi}} = 73.3 \text{ V} \Rightarrow P = \frac{[V_{O(rms)}]^2}{R} = \frac{[73.3]^2}{7} = 810 \text{ W}$$

# Cycloconverters

## ➤ Types of Cycloconverters :

- ✓ Single phase to single phase cycloconverter.
- ✓ Three phase to three phase cycloconverter.
- ✓ Single phase to three phase cycloconverter.



## *Single Phase Cycloconverter*



- First, two single-phase controlled converters are operated as bridge rectifiers.
- The delay angles are configured such that the output voltage of one converter is equal and opposite to that of other converter.


$$V_{dc} = \frac{2V_m}{\pi} \cos(\alpha) = 0.9V_{rms} \cos(\alpha)$$

- If  $\alpha_p$  is the delay angle of the positive converter, the delay angle of the negative converter is :

$$\alpha_n = \pi - \alpha_p$$

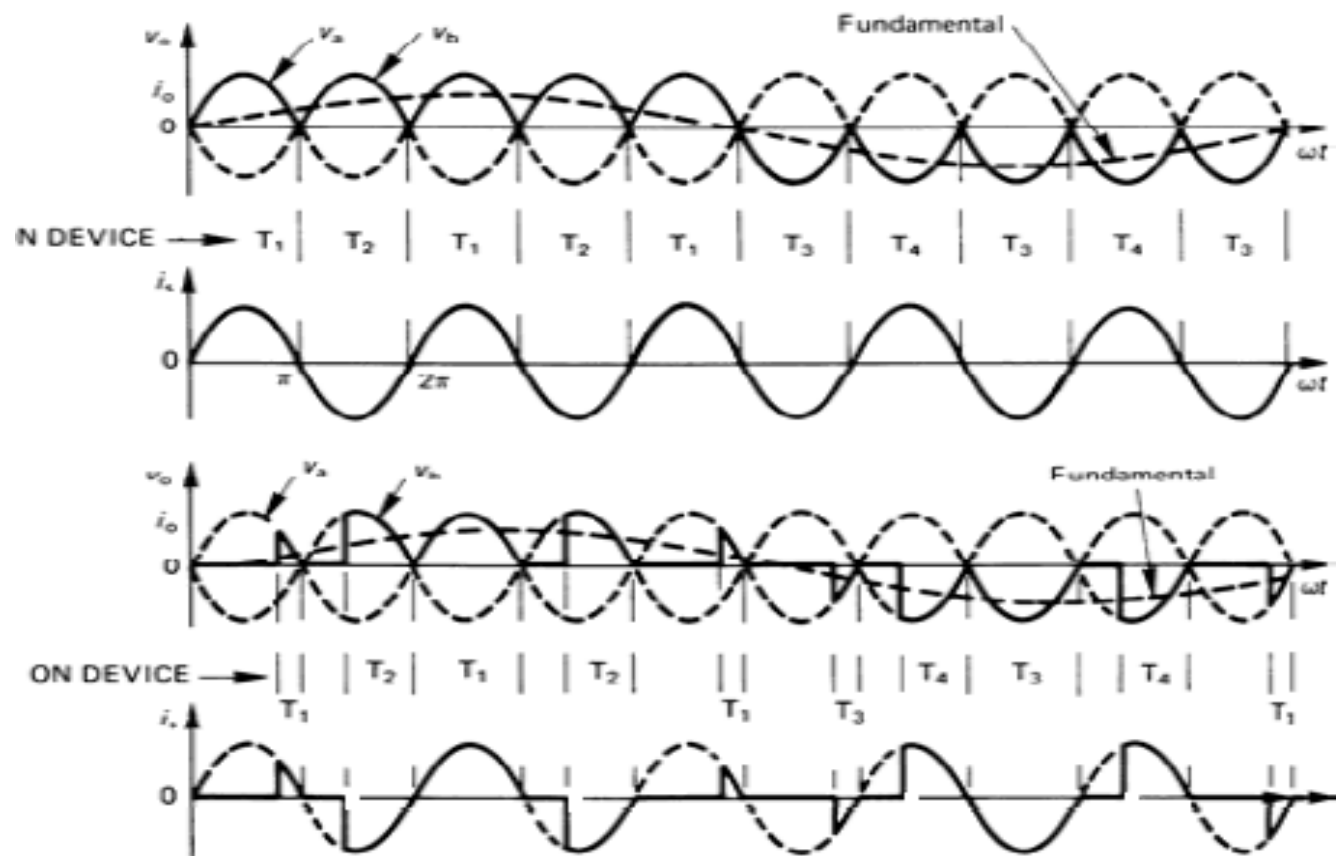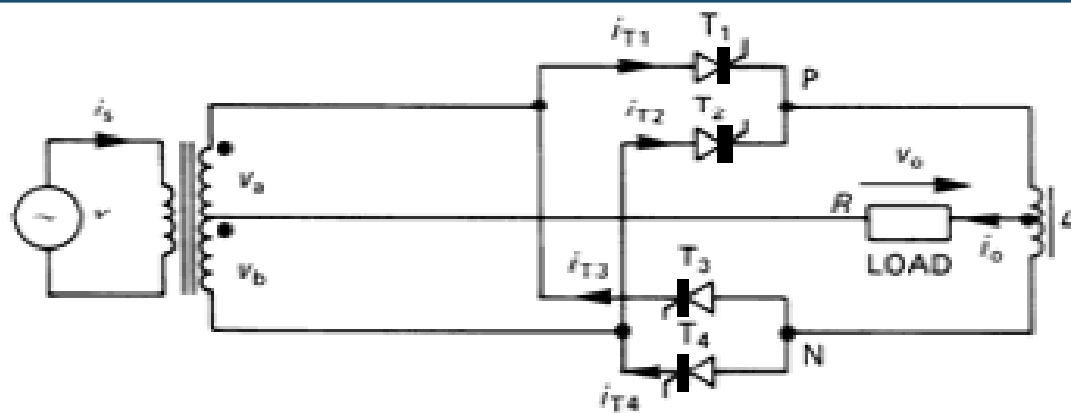

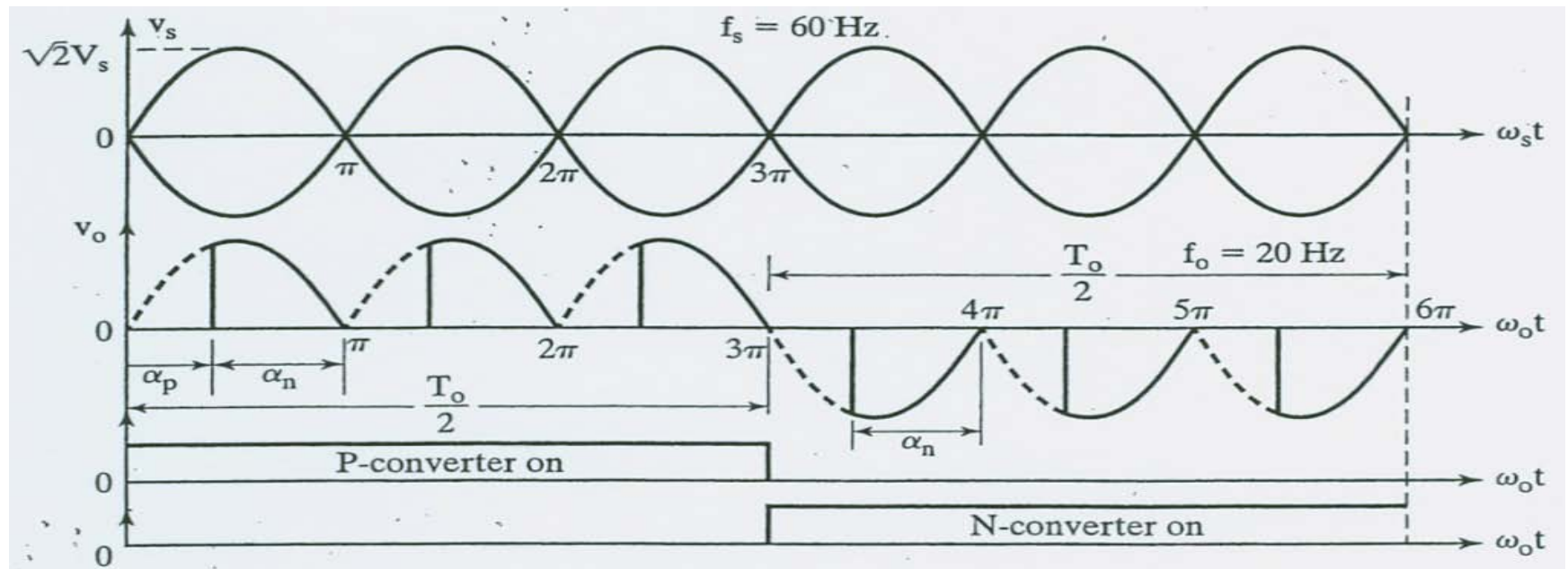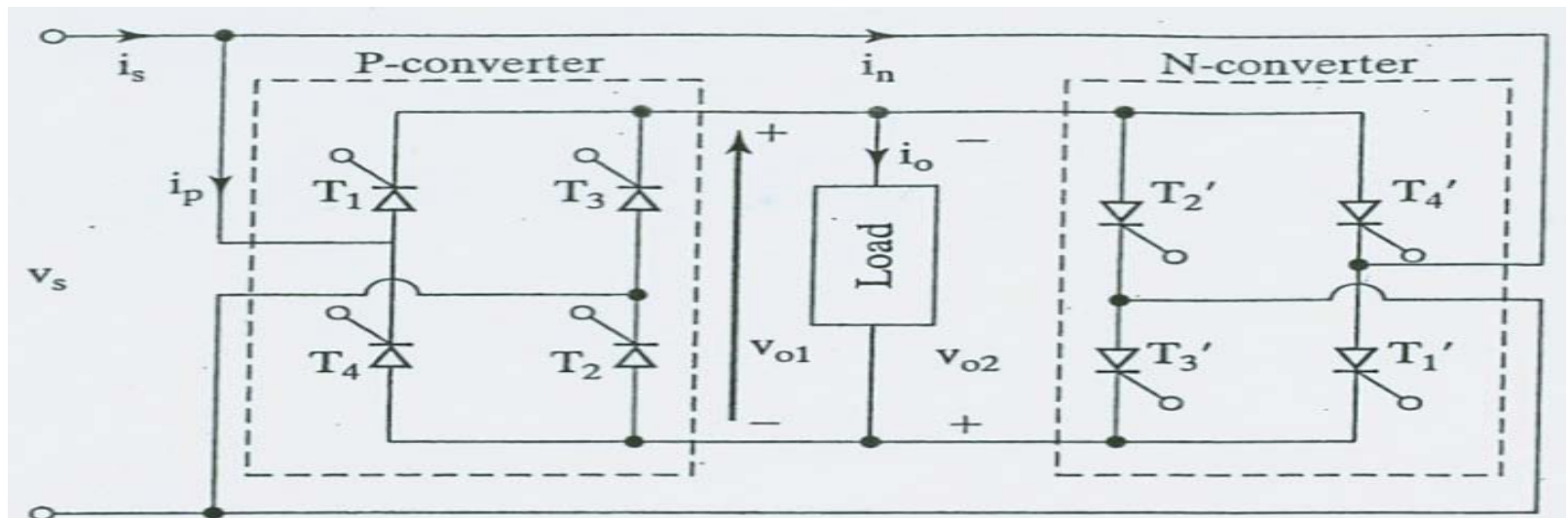

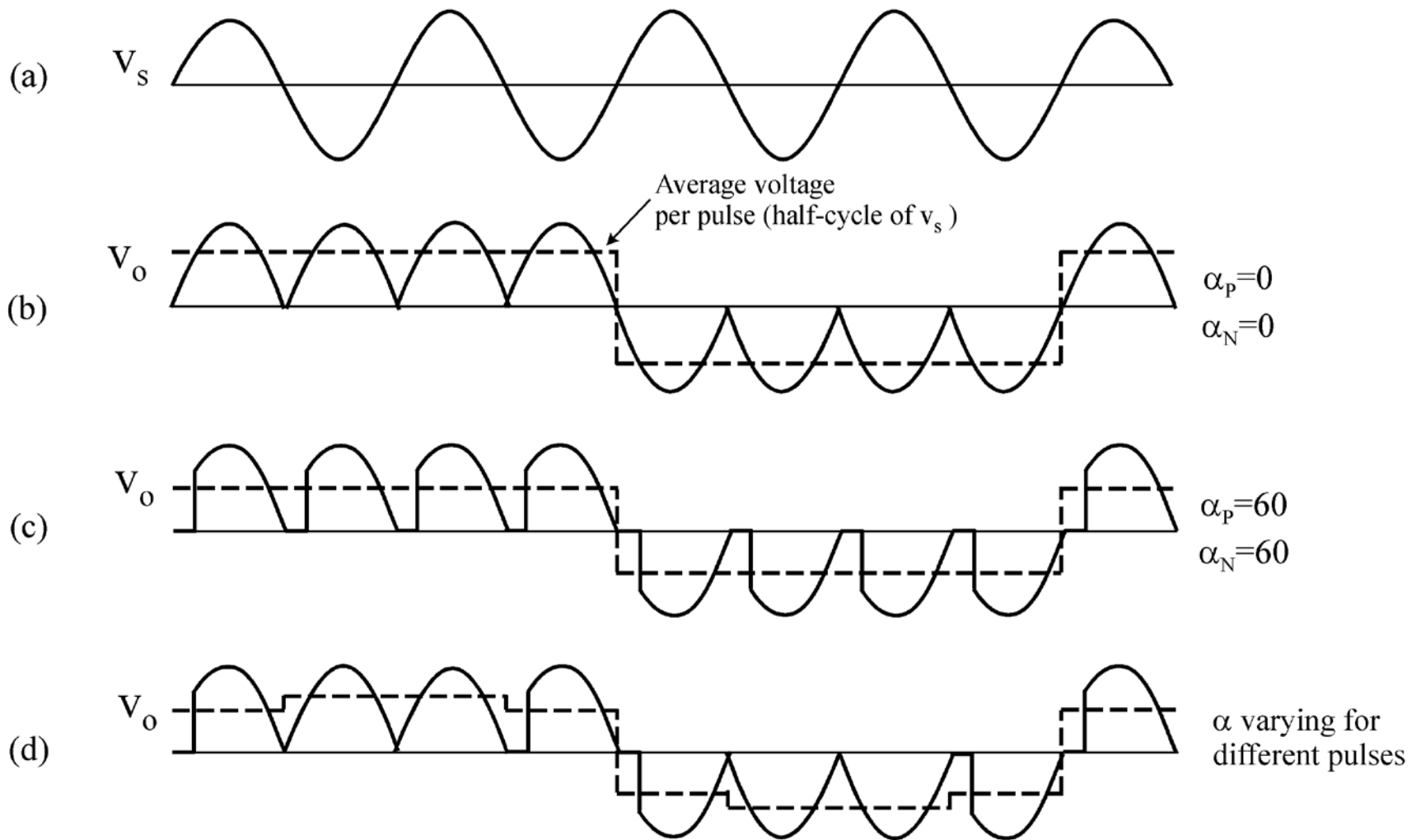

**a)** input voltage    **b)** output voltage for zero firing angle  
**c)** output voltage with firing angle  $\pi/3$  rad.    **d)** output voltage with varying firing angle.



# Problems and Solutions

## Question 1

1 $\Phi$  AC to AC Converter with 100 $\Omega$  resistive load . If the control mode is integral cycle of 4 ON cycles from 5 total cycles and the supply voltage is [240 V, 50Hz ], find 1) the average load power and 2) the supply power factor.

Solution:

$$d = \frac{t_{ON}}{T} = \frac{4}{5}$$

$$1) \quad P_{O(avg)} = \frac{V_i^2 d}{R} = \frac{240^2 (4/5)}{100} = 460.8 \text{ W}$$

$$2) \quad PF = \sqrt{d} = \sqrt{4/5} = 0.894$$

---

## Question 2

1 $\Phi$  AC voltage controller feeding a pure resistance load of rms voltage of 200V. If the rms voltage of the source is 250V, find the power factor of the controller.

Solution:

$$PF = \frac{P}{S} = \frac{V_{O(rms)} I_{O(rms)}}{V_{in(rms)} I_{O(rms)}} = \frac{V_{O(rms)}}{V_{in(rms)}} = \frac{200}{250} = 0.8$$

### Question 3

The voltage controller shown has 120 Vrms, 60Hz source and the load resistance is 15Ω. Determine: a) the delay angle required to deliver 500 W to the load, b) The rms source current , c) The rms and average current in SCRs, and d) The power factor.

#### Solution:

$$\text{a) } P = \frac{[V_{O(rms)}]^2}{R} \Rightarrow 500 = \frac{[V_{O(rms)}]^2}{15}$$

$$V_{O(rms)} = \sqrt{500 \times 15} = 86.6 \text{ V}$$

$$V_{O(rms)} = \frac{V_m}{\sqrt{2}} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin(2\alpha)}{2\pi}}$$


$$86.6 = (120) \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin(2\alpha)}{2\pi}} \Rightarrow \therefore \alpha = 1.54 \text{ rad} = 88.1^\circ$$

$$\text{b) } I_{O(rms)} = \frac{V_{O(rms)}}{R} = \frac{86.6}{15} = 5.77 \text{ A}$$

$$\text{c) } I_{SCR(rms)} = \frac{I_{O(rms)}}{\sqrt{2}} = \frac{5.77}{\sqrt{2}} = 4.08 \text{ A}$$

$$I_{SCR(avg)} = \frac{V_m}{2\pi R} (1 + \cos(\alpha)) = \frac{\sqrt{2} \times 120}{2\pi \times 15} (1 + \cos(88.1)) = 1.86 \text{ A}$$
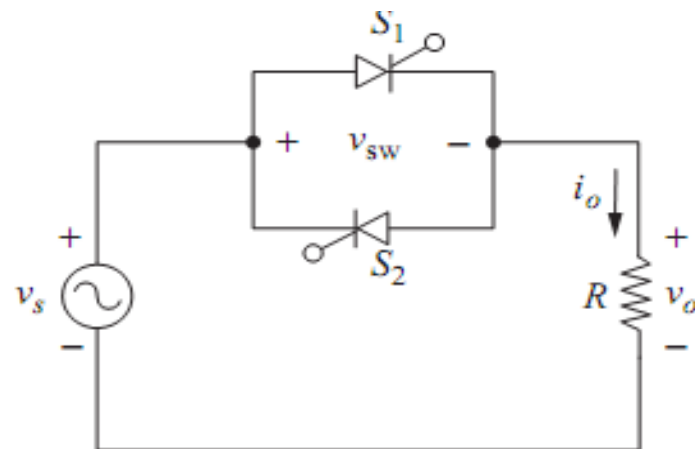
$$\text{d) } PF = \frac{P}{S} = \frac{500}{120 \times 5.77} = 0.72$$



### Question 4

For the given Triac regulator, if the rated power of the lamp is 1KW, find the approximate value of  $\alpha$  that reduces the wattage of the lamp to 500W with switch at position 2.

### Solution:

$$P = \frac{[V_{O(rms)}]^2}{R} ; V_{O(rms)} = \frac{V_m}{\sqrt{2}} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin(2\alpha)}{2\pi}}$$

$$P = \frac{\left(\frac{V_m}{\sqrt{2}}\right)^2}{R} \left(1 - \frac{\alpha}{\pi} + \frac{\sin(2\alpha)}{2\pi}\right)$$


$$500 = 1000 \times \left(1 - \frac{\alpha}{\pi} + \frac{\sin(2\alpha)}{2\pi}\right)$$

$$0.5 = 1 - \frac{\alpha}{\pi} + \frac{\sin(2\alpha)}{2\pi}$$

$$0.5\pi = \pi - \alpha + 0.5\sin(2\alpha)$$

$$\therefore \alpha - 0.5\sin(2\alpha) = \pi/2$$

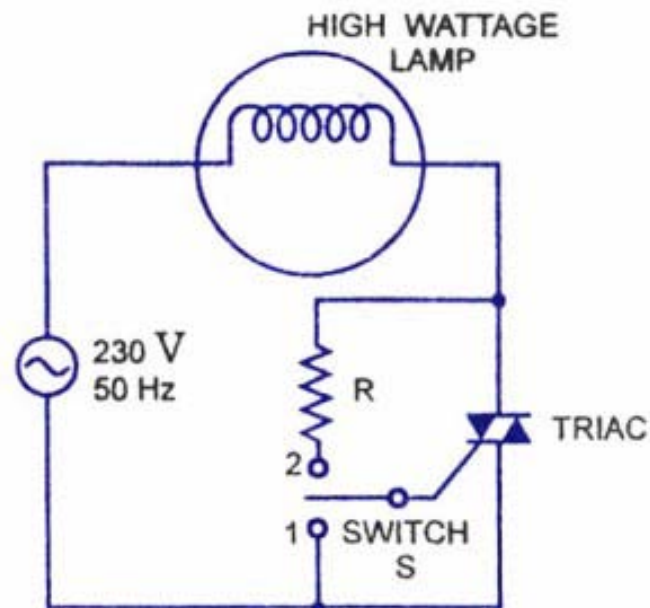By estimation, we can find that:  $\alpha = \pi/2$




### Question 5

For the shown 1 $\Phi$  AC controller, calculate the rms output voltage for  $\alpha = 45^\circ$  symmetrical trigger.
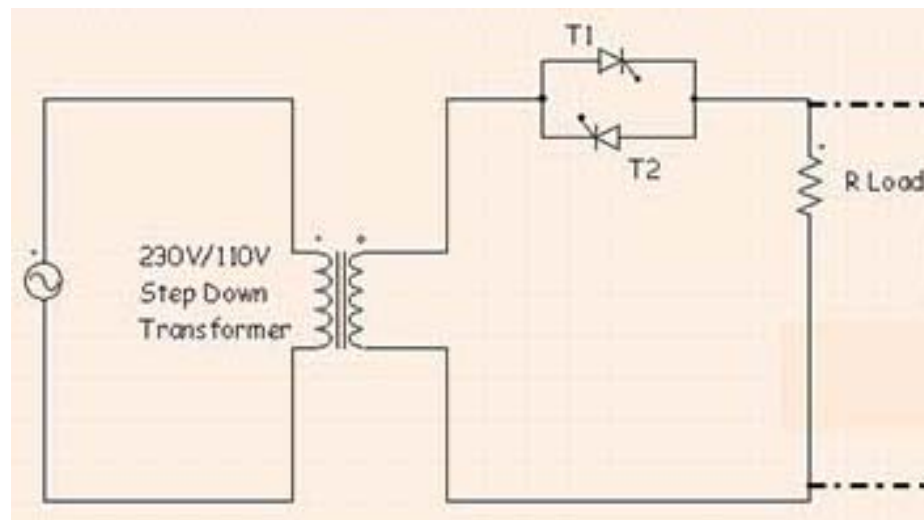
#### Solution:

$$V_{O(rms)} = \frac{V_m}{\sqrt{2}} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin(2\alpha)}{2\pi}}$$

$$V_{O(rms)} = 110 \sqrt{1 - \frac{45}{180} + \frac{\sin(2 \times 45)}{2 \times 3.14}} = 104.9 \text{ V}$$



### Question 6

1 $\Phi$  to 1 $\Phi$  step-down cycloconverter with the following data: [240V, 60Hz] supply, output frequency is 10Hz, the positive and negative converter groups are set to give  $V_{dc3} = 216\text{V}$ ,  $V_{dc2} = 187\text{V}$ , and  $V_{dc1} = 108\text{V}$ . Find the values of firing angles.

#### Solution:

$$V_{dc} = 0.9 V_{rms} \cos(\alpha)$$

$$V_{dc3} = 0.9 V_{rms} \cos(\alpha_3) \Rightarrow 216 = 0.9 \times 240 \times \cos(\alpha_3) \Rightarrow \alpha_3 = 0^\circ$$

$$V_{dc2} = 0.9 V_{rms} \cos(\alpha_2) \Rightarrow 187 = 0.9 \times 240 \times \cos(\alpha_2) \Rightarrow \alpha_2 = 30^\circ$$


$$V_{dc1} = 0.9 V_{rms} \cos(\alpha_1) \Rightarrow 108 = 0.9 \times 240 \times \cos(\alpha_1) \Rightarrow \alpha_1 = 60^\circ$$

### Question 7


Draw the voltage waveforms for an AC controller using On/Off and Phase control methods for the following outputs: 100%, 75% ,and 25% .

#### Solution:

On/ Off Control

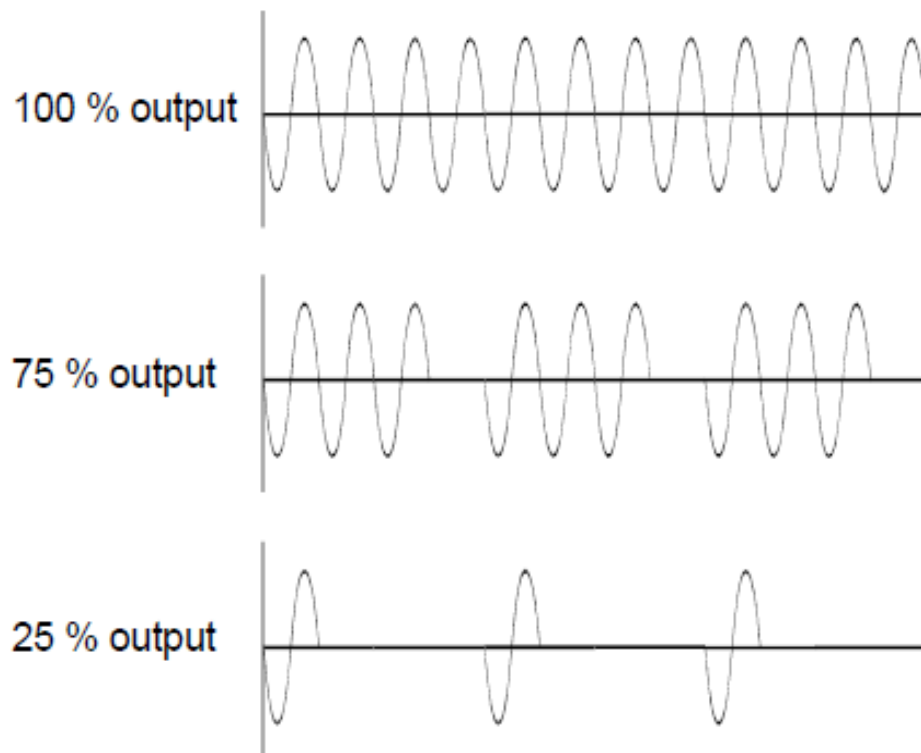

Phase Angle Control

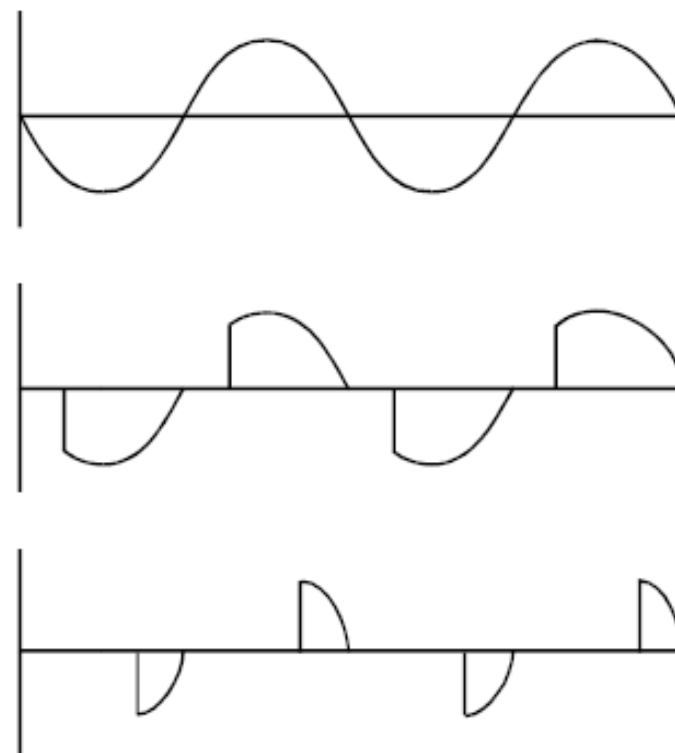

## **Question 8    Fill in the blanks with the appropriate word(s)**

- 1)**    Triac is the word derived by combining the capital letters from the words -----and -----.
- 2)**    AC Regulators are also called AC -----
- 3)**    ----- circuits are used to prevent premature triggering caused for example by voltage spikes in the AC supply or those produced by inductive loads such as motors.
- 4)**    Integral Cycle Control Method is applied to load with ----- element.
- 5)**    The ----- is fabricated by integrating two thyristors in an ----- parallel connection.

### **Answers:**

1) Triode, alternating current. 2) AC controllers. 3) Snubber. 4) heating. 5) Triac, anti

## Question 9 Choose the correct answer for the following Questions

1) A cycloconverter can be

(A) Step down.

(B) Step up.

☒ (C) Step down or Step up.

(D) Neither of above.

2) Match **List I** (Converters) with **List II** (Type of conversion) and select the correct answer :

### List I

A. Controlled Rectifier

B. Chopper

C. Inverter

D. Cycloconverter

### List II

1. Fixed DC to variable voltage and variable frequency AC

2. Fixed DC to variable DC

3. Fixed AC to variable DC

4. Fixed AC to variable frequency AC

Codes :


	A	B	C	D
(A)	2	3	1	4
(B)	3	2	4	1
(C)	2	3	4	1
<input checked="" type="checkbox"/> (D)	3	2	1	4

3)

1. Single phase fully controlled ac to dc converter
2. Voltage commutated dc to dc chopper with input dc voltage  $E$ .
3. Phase voltage of a three phase inverter with  $180^\circ$  conduction and input dc voltage  $E$ .
4. Line voltage of a three phase inverter with  $120^\circ$  conduction and input dc voltage  $E$ .
5. Three-phase diode bridge rectifier.


A.

3

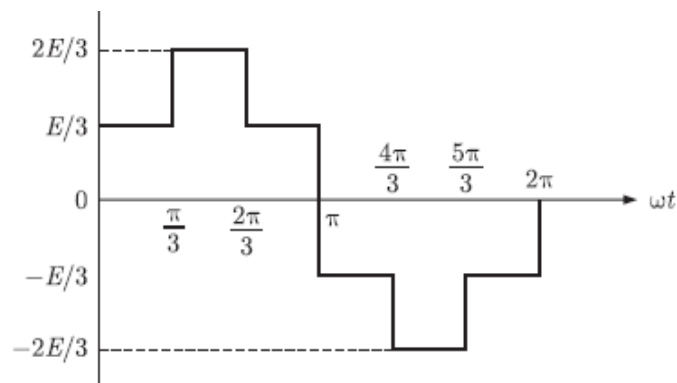


B.

4

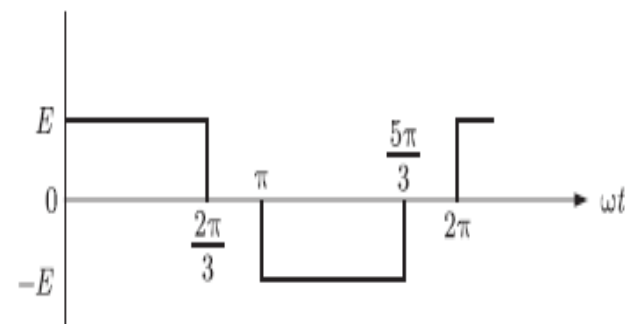

D.

5

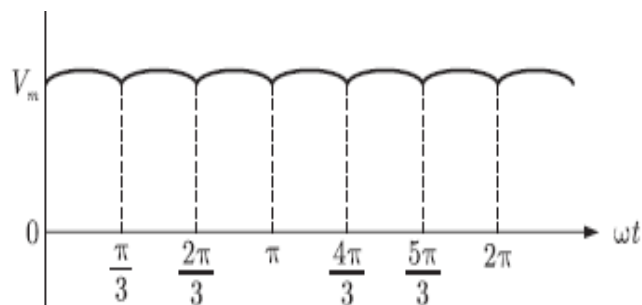

C.

1

